



# KTU **NOTES**


The learning companion.

**KTU STUDY MATERIALS | SYLLABUS | LIVE  
NOTIFICATIONS | SOLVED QUESTION PAPERS**

## MODULE - 5

19/11/2020

### Two port network parameters

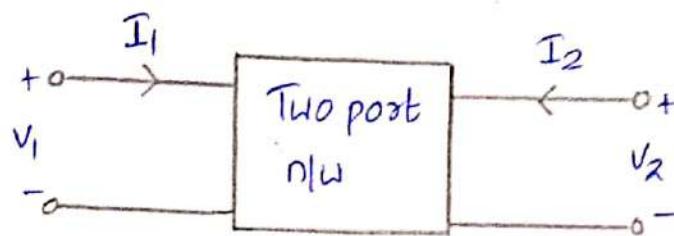

There are 4 variables associated with two port n/w  $V_1, V_2, I_1$  and  $I_2$ . Two of these variables can be represented in terms of the other two. There will be two dependent variables and two independent variables.

PARAMETERS	VARIABLES		EQUATION
	DEPENDENT	INDEPENDENT	
Impedance	$V_1, V_2$	$I_1, I_2$	$V_1 = Z_{11}I_1 + Z_{12}I_2$ $V_2 = Z_{21}I_1 + Z_{22}I_2$
Admittance	$I_1, I_2$	$V_1, V_2$	$I_1 = Y_{11}V_1 + Y_{12}V_2$ $I_2 = Y_{21}V_1 + Y_{22}V_2$
Transmission	$V_1, I_1$	$V_2, I_2$	$V_1 = AV_2 - BI_2$ $I_1 = CV_2 - DI_2$
Hybrid	$V_1, I_2$	$I_1, V_2$	$V_1 = h_{11}I_1 + h_{12}V_2$ $I_2 = h_{21}I_1 + h_{22}V_2$

### Open circuited Impedance Parameters ( $Z$ -parameters)

$$(V_1, V_2) = f(I_1, I_2)$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\text{In matrix form } \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[V] = [Z][I]$$

The individual  $Z$ -parameters can be found out by setting each of the port currents to zero.

Case-I:  $I_2=0$ , o/p port open circuited

$$V_{11} = Z_{11} \cdot I_1 \Big|_{I_2=0} \Rightarrow Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$Z_{11}$  is the driving point impedance with o/p open circuited. It is called open circuit input impedance.

$$V_2 = Z_{21} I_1 \Big|_{I_2=0} \Rightarrow Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$Z_{21}$  - transfer impedance with dp open circuited or open circuit forward transfer impedance.


Case-II:  $I_1=0$ , i/p open circuited.

$$V_1 = Z_{12} I_2 \Big|_{I_1=0} \Rightarrow Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$Z_{12}$  - transfer impedance with Input open circuited or open circuit reverse transfer impedance.

$$\text{Hence } Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

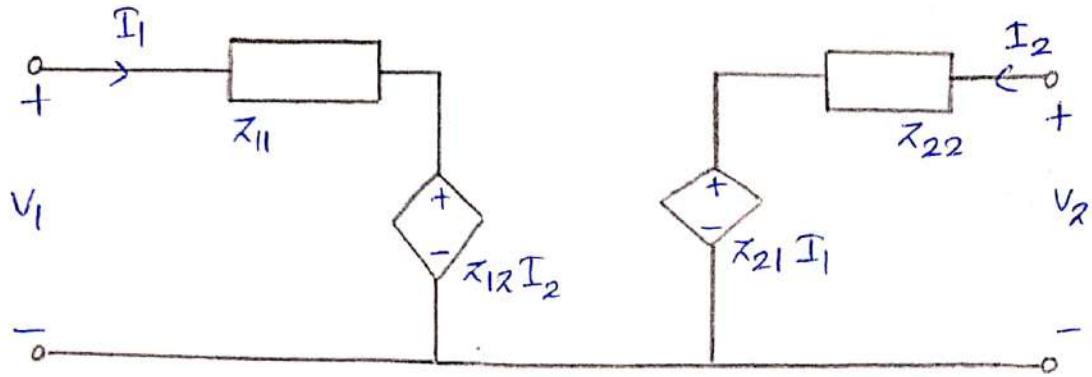$Z_{22}$  - Open circuit driving point impedance with the input open circuited.  
Also called open circuit o/p impedance.




Equivalent of two port N/H in terms of z-parameters.

→ The impedance parameters are measured with either input or o/p port open circuited, hence they are called **open circuit impedance parameters**.

### CONDITION FOR RECIPROCITY

A network is said to be reciprocal if the ratio of excitation at one port to response at the other port is same if excitation and response are interchanged.

a)

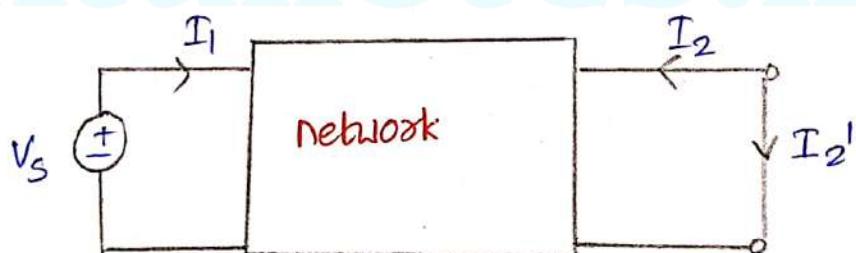

Network for driving condition for reciprocity.

Voltage  $V_s$  is applied at the input port with the o/p short circuited

$$V_1 = V_s, V_2 = 0, I_2 = -I_2'$$

From z parameter eqns,

$$V_s = Z_{11} I_1 - Z_{12} I_2' \quad \text{--- (1)}$$

$$0 = Z_{21} I_1 - Z_{22} I_2' \quad \text{--- (2)}$$


$$I_1 = \frac{Z_{22}}{Z_{21}} I_2' \quad \text{--- (3)}$$

$$\begin{cases} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \end{cases}$$

Substituting in ①,  $V_s = z_{11} \cdot \frac{z_{22}}{z_{21}} I_2' - z_{12} I_2'$

$$\cdot \frac{V_s}{I_2'} = \frac{z_{11} z_{22} - z_{12} z_{21}}{z_{21}}$$

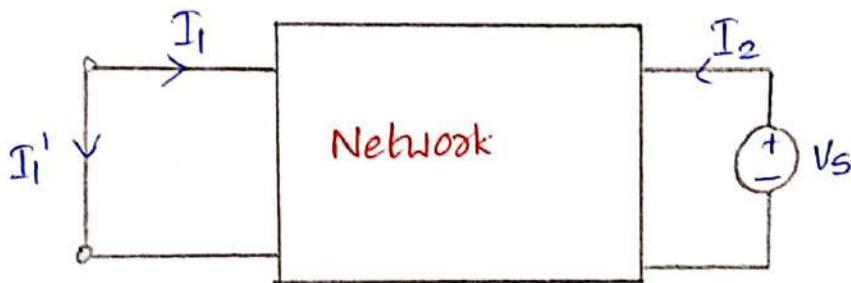(b) Interchanging the excitation and response.



$$U_2 = V_s, U_1 = 0, I_1 = -I_1'$$

From the  $\pi$  parameter equations,

$$0 = -z_{11} I_1' + z_{12} I_2 \quad \text{--- ①}$$

$$V_s = -z_{21} I_1' + z_{22} I_2 \quad \text{--- ②}$$

$$I_2 = \frac{z_{11}}{z_{12}} I_1' \quad \text{--- ③}$$

$$V_s = -z_{21} I_1' + z_{22} \cdot \frac{z_{11}}{z_{12}} I_1'$$

$$\frac{V_s}{I_1'} = \frac{z_{11} z_{22} - z_{12} z_{21}}{z_{12}}$$

For the  $n/w$  to be reciprocal,

$$\frac{V_s}{I_2'} = \frac{V_s}{I_1'} \Rightarrow \underline{\underline{z_{12} = z_{21}}}$$

23/11/20 CONDITION FOR SYMMETRY

For a network to be symmetrical, the voltage to current ratio at one port should be the same as the voltage to current ratio at the other port with one of the ports open circuited.

- a) When the output port is open circuited

$$I_2 = 0$$

From z-parameter equations,

$$V_S = Z_{11} I_1$$

$$Z_{11} = \frac{V_S}{I_1}$$

- b) When the input port is open,

$$I_1 = 0$$

$$V_S = Z_{22} I_2$$

$$\frac{V_S}{I_2} = Z_{22}$$

Hence for the n/w to be symmetrical,

$$\frac{V_S}{I_1} = \frac{V_S}{I_2}$$

$$\text{ie } \underline{Z_{11}} = \underline{Z_{22}}$$

PROBLEMS

1. Test results for a two port n/w are ①  $I_1 = 0.1 \angle 0^\circ A$ ,  $V_1 = 5.2 \angle 50^\circ V$ ,  $V_2 = 4.1 \angle -25^\circ V$  with port 2 open circuited. ②  $I_2 = 0.1 \angle 0^\circ A$ ,  $V_1 = 3.1 \angle -80^\circ V$ ,  $V_2 = 4.2 \angle 60^\circ V$  with port-1 open circuited. Find z-parameters.

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{5.2 \angle 50^\circ}{0.1 \angle 0^\circ} = 52 \angle 50^\circ \Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{4.1[-25]}{0.1[0]} = 41[-25^\circ] \Omega$$


$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{8.1[-80^\circ]}{0.1[0]} = 81[-80^\circ] \Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{4.2[60^\circ]}{0.1[0^\circ]} = 42[60^\circ] \Omega$$

Hence the  $\pi$ -parameters are

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 52[50^\circ] & 81[-80^\circ] \\ 41[-25^\circ] & 42[60^\circ] \end{bmatrix}$$

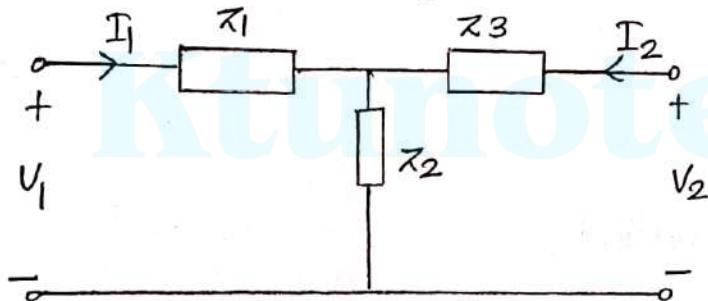2. Find the  $\pi$ -parameters for the network.



First method

Case-I: When the op is open circuited  $I_2=0$ .

Applying KVL to Mesh-1;

$$V_1 = (Z_1 + Z_2)I_1$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = Z_1 + Z_2$$

$$V_2 = Z_2 I_1$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = Z_2$$

Case 2: When  $v_p$  is open circuited,  $I_1 = 0$

$$V_2 = (Z_2 + Z_3)I_2$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = Z_2 + Z_3$$

$$V_1 = Z_2 I_2$$


$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = Z_2$$

Hence the z-parameters are,

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_1 + Z_2 & Z_2 \\ Z_2 & Z_2 + Z_3 \end{bmatrix}$$

2nd method

Redrawing the n/w,

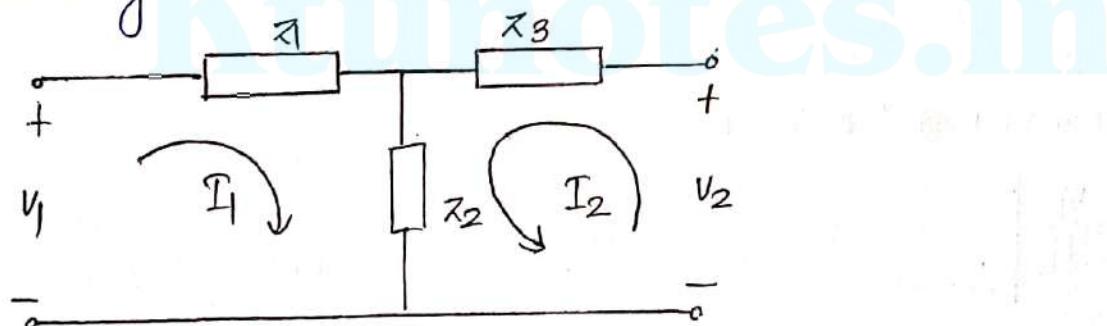


$$\begin{aligned} V_1 &= Z_1 I_1 + Z_2 (I_1 + I_2) \\ &= (Z_1 + Z_2) I_1 + Z_2 I_2 \quad \text{--- } \textcircled{1} \end{aligned}$$

$$\begin{aligned} V_2 &= Z_3 I_2 + Z_2 (I_1 + I_2) \\ &= Z_2 I_1 + (Z_2 + Z_3) I_2 \quad \text{--- } \textcircled{2} \end{aligned}$$


$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_1 + Z_2 & Z_2 \\ Z_2 & Z_2 + Z_3 \end{bmatrix}$$

---

3. Find  $\pi$ -parameters of the n/w.

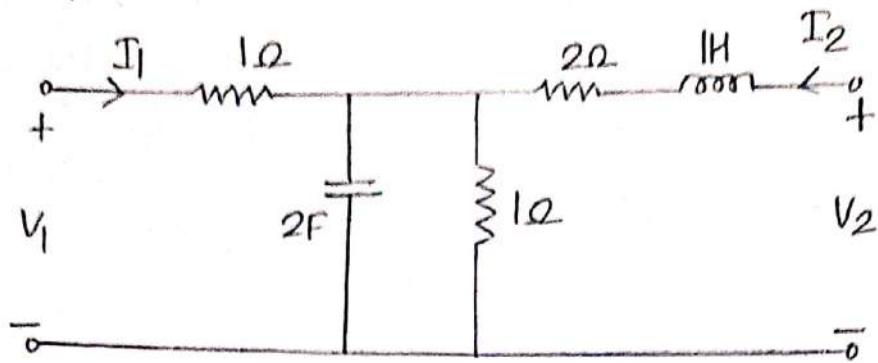

Transformed n/w

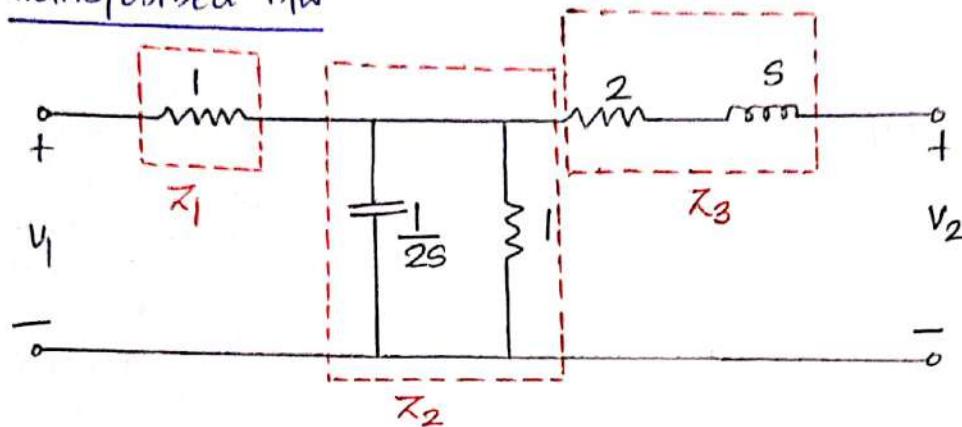

$$Z_1 = 1, Z_2 = \frac{1}{2s} \cdot 1 = \frac{1}{2s+1}, Z_3 = s+2$$

KTunotes.in

From  $\pi$ -parameter distribution,

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_1 + Z_2 = 1 + \frac{1}{2s+1} = \frac{2s+1+1}{2s+1} = \frac{2(s+1)}{2s+1}$$


$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \Rightarrow Z_2 = \frac{1}{2s+1}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = Z_2 = \frac{1}{2s+1}$$


$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_2 + Z_3 = \frac{1}{2s+1} + s+2 = \frac{1 + (2s+1)(s+2)}{2s+1}$$

$$= \frac{1 + 2s^2 + 5s + 2}{2s+1} = \underline{\underline{\frac{2s^2 + 5s + 2}{2s+1}}}$$

4. Find  $\pi$ -parameters of the n/w.

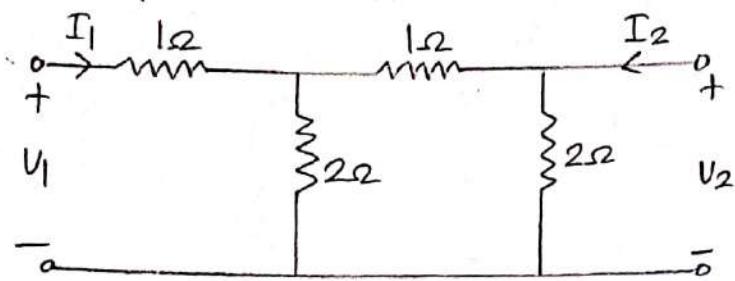

Redrawing the n/w

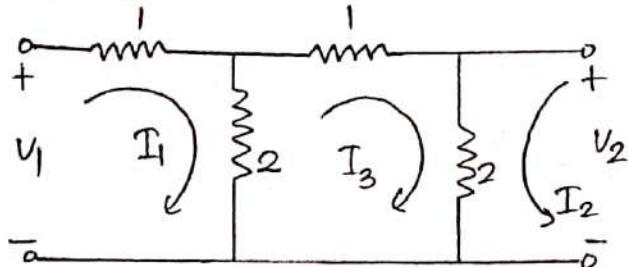

$$\text{Mesh-1: } -V_1 + 3I_1 - 2I_3 = 0 \Rightarrow V_1 = 3I_1 - 2I_3 \quad \textcircled{1}$$

$$\text{Mesh-3: } 2I_2 + 2I_3 - V_2 = 0 \Rightarrow V_2 = 2I_2 + 2I_3 \quad \textcircled{2}$$

$$\text{Mesh-2: } -2I_1 + 2I_2 + 5I_3 = 0$$

$$I_3 = \frac{2}{5}I_1 - \frac{2}{5}I_2 \quad \textcircled{3}$$

Substituting  $I_3$  in  $\textcircled{1}$  and  $\textcircled{2}$  to eliminate  $I_3$ .

$$\begin{aligned} V_1 &= 3I_1 - 2\left(\frac{2}{5}I_1 - \frac{2}{5}I_2\right) \\ &= 3I_1 - \frac{4}{5}I_1 + \frac{4}{5}I_2 \end{aligned}$$

$$V_1 = \frac{11}{5}I_1 + \frac{4}{5}I_2 \quad \textcircled{4}$$

$$V_2 = 2I_2 + 2\left(\frac{2}{5}I_1 - \frac{2}{5}I_2\right)$$

$$= 2I_2 + \frac{4}{5}I_1 - \frac{4}{5}I_2$$

$$V_2 = \frac{4}{5}I_1 + \frac{6}{5}I_2 \quad \textcircled{5}$$


$$\begin{cases} V_1 = Z_{11}I_1 + Z_{12}I_2 \\ V_2 = Z_{21}I_1 + Z_{22}I_2 \end{cases}$$

Comparing  $\textcircled{4}$  and  $\textcircled{5}$  with  $\pi$ -parameter eqns.


$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{11}{5} & \frac{4}{5} \\ \frac{4}{5} & \frac{6}{5} \end{bmatrix}$$

5. Find z-parameters of the following nlu.

24/11/20

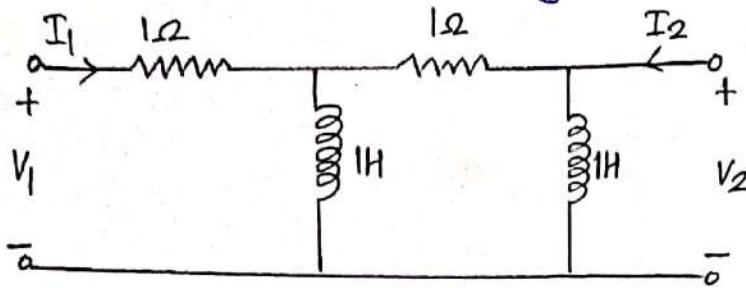

Transformed nlu

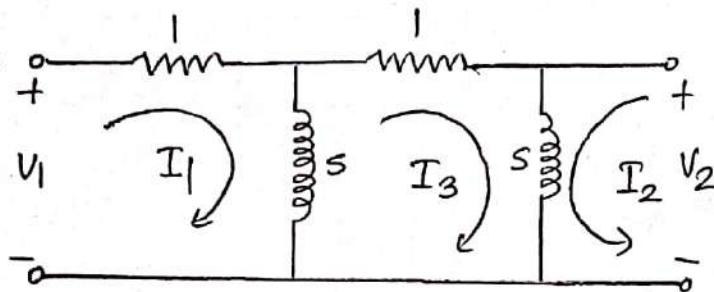

$$\text{Mesh-1: } V_1 = (s+1)I_1 - sI_3 \quad \text{--- (1)}$$

$$\text{Mesh-3: } V_2 = 3I_2 + sI_3 \quad \text{--- (2)}$$

$$\text{Mesh-2: } -6I_1 + 5I_2 + (2s+1)I_3 = 0$$

$$(2s+1)I_3 = sI_1 - sI_2$$

$$I_3 = \frac{s}{2s+1} I_1 - \frac{s}{2s+1} I_2 \quad \text{--- (3)}$$

Substituting in (1);

$$\begin{aligned} V_1 &= (s+1)I_1 - s \left[ \frac{s}{2s+1} I_1 - \frac{s}{2s+1} I_2 \right] \\ &= \left[ (s+1) - \frac{s^2}{2s+1} \right] I_1 + \frac{s^2}{2s+1} I_2 \\ &= \left[ \frac{(s+1)(2s+1) - s^2}{(2s+1)} \right] I_1 + \left( \frac{s^2}{2s+1} \right) I_2 \\ &= \left[ \frac{2s^2 + 3s + 1 - s^2}{2s+1} \right] I_1 + \left( \frac{s^2}{2s+1} \right) I_2 \end{aligned}$$

$$V_1 = \left( \frac{s^2 + 3s + 1}{2s+1} \right) I_1 + \left( \frac{s^2}{2s+1} \right) I_2 \quad \text{--- (4)}$$

Substituting ③ in ②,

$$\begin{aligned}
 V_2 &= SI_2 + S \left[ \frac{s}{2s+1} I_1 - \frac{s}{2s+1} I_2 \right] \\
 &= \frac{s^2}{2s+1} I_1 + \frac{2s^2+s-s^2}{2s+1} I_2 \\
 &= \frac{s^2}{2s+1} I_1 + \frac{s^2+s}{2s+1} I_2 \quad \longrightarrow \textcircled{5}
 \end{aligned}$$


$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$


Comparing ④, ⑤ with  $z$ -parameter eqns,

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} \frac{s^2+3s+1}{2s+1} & \frac{s^2}{2s+1} \\ \frac{s^2}{2s+1} & \frac{s^2+s}{2s+1} \end{bmatrix}$$

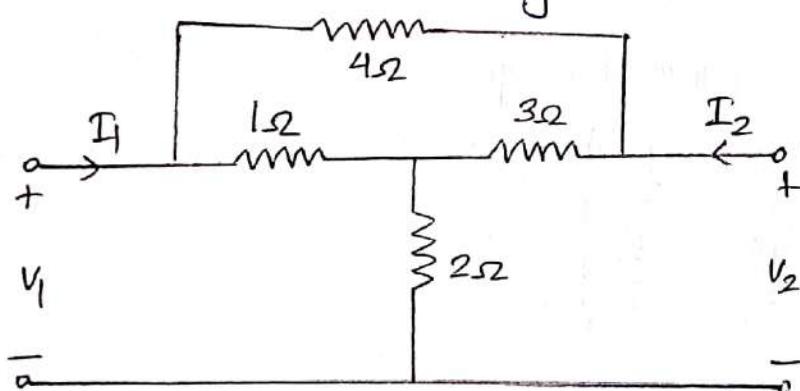6. Find the open circuit impedance parameters for the n/w shown below. Determine whether the n/w is symmetrical and reciprocal.



The n/w can be redrawn as shown below,

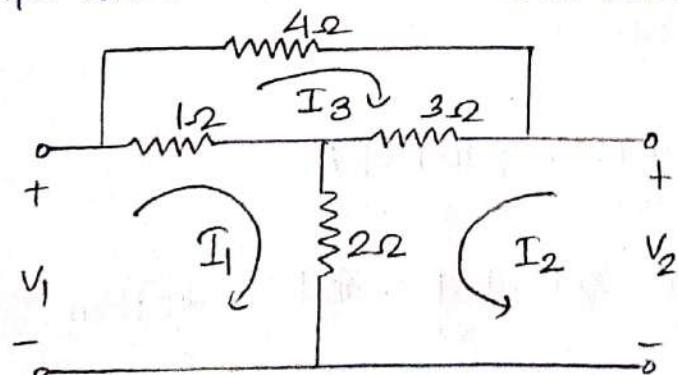

Applying KVL to mesh 1,

$$-V_1 + 3I_1 + 2I_2 - I_3 = 0$$

$$V_1 = 3I_1 + 2I_2 - I_3 \quad \textcircled{1}$$

Mesh - 2:

$$5I_2 + 2I_1 + 3I_3 - V_2 = 0$$

$$V_2 = 2I_1 + 5I_2 + 3I_3 \quad \text{--- (2)}$$

Mesh - 3:

$$8I_3 + 3I_2 - I_1 = 0$$

$$I_3 = \frac{1}{8}I_1 - \frac{3}{8}I_2 \quad \text{--- (3)}$$

Substituting  $I_3$  in (1);

$$V_1 = 8I_1 + 2I_2 - \left[ \frac{1}{8}I_1 - \frac{3}{8}I_2 \right]$$

$$= \frac{23}{8}I_1 + \frac{19}{8}I_2 \quad \text{--- (4)}$$

Substituting  $I_3$  in (2);

$$V_2 = 2I_1 + 5I_2 + 3\left[ \frac{1}{8}I_1 - \frac{3}{8}I_2 \right]$$

$$= \frac{19}{8}I_1 + \frac{31}{8}I_2 \quad \text{--- (5)}$$

Comparing (4) and (5) with  $\pi$ -parameter eqns,

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{23}{8} & \frac{19}{8} \\ \frac{19}{8} & \frac{31}{8} \end{bmatrix}$$

$Z_{11} \neq Z_{22}$ , the network is not symmetrical

$Z_{12} = Z_{21}$ ; hence the net is reciprocal

### Situation circuit admittance parameters (Y-parameters)

Y-parameters may be defined by expressing  $I_1$  and  $I_2$  in terms of  $V_1$  and  $V_2$

$$(I_1, I_2) = f(V_1, V_2)$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- } ①$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- } ②$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{In matrix form}$$

$$[I] = [Y][V]$$

Individual  $Y$ -parameters can be defined by setting each of the port voltages to zero.

### Case-I

When o/p port is short-circuited,  $V_2 = 0$

$$Y_{11} = \frac{I_1}{V_1} \quad \Big| \quad V_2 = 0$$

$Y_{11}$  - driving point admittance with the output port short circuited. It is also called short-circuit input admittance.

$$Y_{21} = \frac{I_2}{V_1} \quad \Big| \quad V_2 = 0$$

$Y_{21}$  - transfer admittance with o/p short circuited. Also called short-circuit forward transfer admittance.

### Case-II

When input port is short circuited,  $V_1 = 0$

$$Y_{12} = \frac{I_1}{V_2} \quad \Big| \quad V_1 = 0$$


$Y_{12}$  - transfer admittance with input port short circuited. It is also called short circuit reverse transfer admittance.

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$Y_{22}$  - Short circuit driving point admittance with input short circuited.  
It is also called short-circuit output admittance.

The admittance parameters are measured with either i/p or o/p port short circuited, hence they are called short-circuit admittance parameters.

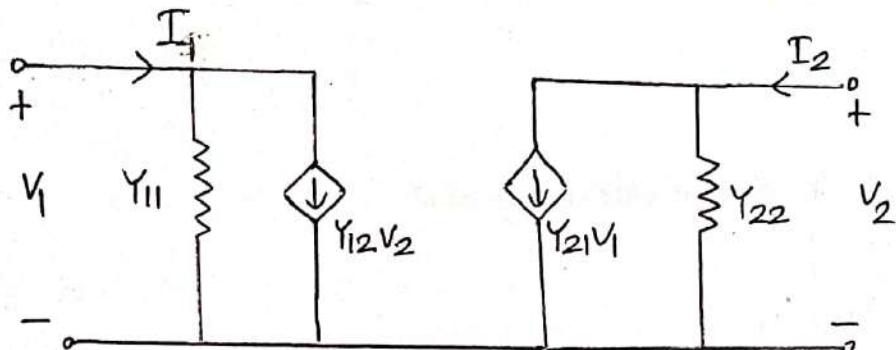Equivalent circuit of two port n/w in terms of Y-parameters is shown below



25/11/20 CONDITION FOR RECIPROCITY


① Vs applied at input port, o/p short circuited.

$$V_1 = V_s, V_2 = 0, I_2 = -I_2'$$

$$I_2 = Y_{21}V_1 \text{ From } ②$$

$$-I_2' = Y_{21}V_s$$


$$\frac{I_2'}{V_s} = -Y_{21}$$

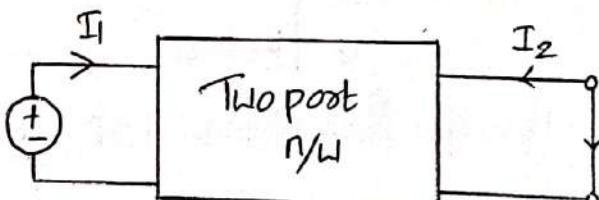

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad ①$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad ②$$

⑥ Interchanging excitation and response

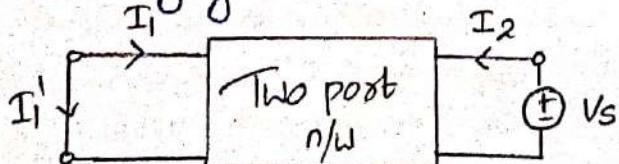

$$V_2 = V_s, V_1 = 0, I_1 = -I_1'$$

$$\text{From } ① \quad I_1 = Y_{12}V_2$$

$$-I_1' = Y_{12}V_s$$

$$\frac{I_1'}{V_s} = -Y_{12}$$

For the n/w to be reciprocal,

$$\frac{I_2'}{V_s} = \frac{I_1'}{V_s}$$

$$\underline{\underline{Y_{12} = Y_{21}}}$$

### CONDITION FOR SYMMETRY

(a) When the o/p post is short circuited,  $V_2 = 0$

From (1),

$$I_1 = Y_{11} V_s$$

$$\frac{V_s}{I_1} = \frac{1}{Y_{11}}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$

(b) When the i/p post is short circuited, ie  $V_1 = 0$

$$\text{From (2), } I_2 = Y_{22} V_s$$

$$\frac{V_s}{I_2} = \frac{1}{Y_{22}}$$

For the n/w to be symmetrical,

$$\frac{V_s}{I_1} = \frac{V_s}{I_2}$$

$$\underline{\underline{Y_{11} = Y_{12}}}$$

Note: For the n/w to be symmetrical, the voltage current ratio at one post should be the same as the voltage to current ratio of the other post with one of the other posts short circuited.

### PROBLEMS

1. Test results for a two port n/w are:

(a) Post - 2 short circuited ;  $V_1 = 50 \angle 0^\circ V$ ,  $I_1 = 2.1 \angle 30^\circ A$ ,  $I_2 = -1.1 \angle -20^\circ A$

⑥ Port-1 short circuited:  $V_2 = 50 \angle 0^\circ V$ ,  $I_2 = 3 \angle -15^\circ A$ ,  $I_1 = -1.1 \angle -20^\circ A$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{2.1 \angle -30^\circ}{50 \angle 0} = 0.042 \angle -30^\circ S$$


$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{-1.1 \angle 20^\circ}{50 \angle 0} = -0.022 \angle -20^\circ S.$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{3 \angle -15^\circ}{50 \angle 0} = 0.06 \angle -15^\circ S.$$

$Y$ -parameters are:

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.042 \angle -30^\circ & -0.022 \angle -20^\circ \\ -0.022 \angle -20^\circ & 0.06 \angle -15^\circ \end{bmatrix}$$

2. Find  $Y$ -parameters of the n/w.

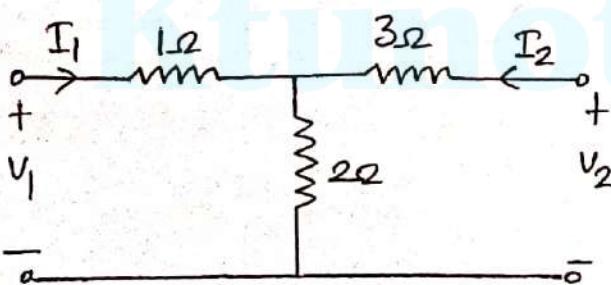


First Method

Case 1: When the op port is short circuited;  $V_2 = 0$

$$R_{eq} = 1 + \frac{2 \times 3}{2+3} = 1 + \frac{6}{5} = \frac{11}{5} \Omega$$

$$V_1 = \frac{11}{5} I_1$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{5}{11} S$$

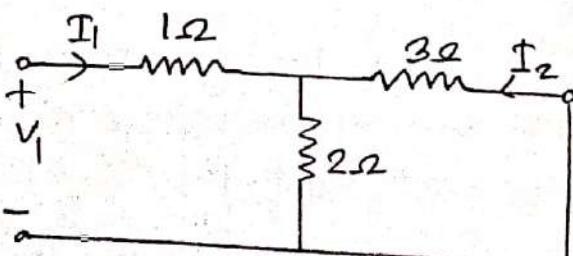

$$I_2 = -I_1 \times \frac{2}{2+3} = -\frac{2}{5} \cdot \frac{5V_1}{11} = -\frac{2}{11} V_1$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \underline{\underline{\frac{-2}{11} s}}$$


CASE 2:

When the input port is short circuited,  $V_1 = 0$

$$\text{Req.} = 3 + \frac{1 \times 2}{1+2} = \frac{11}{3} \Omega$$

$$V_2 = \frac{11}{3} I_2$$

$$\therefore Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \underline{\underline{\frac{3}{4} s}}$$

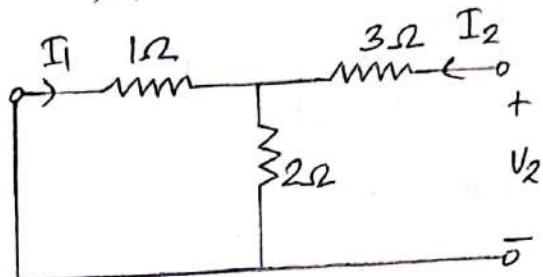


$$I_1 = -I_2 \times \frac{2}{3} = -\frac{2}{3} \cdot \frac{3V_2}{11} = -\frac{2}{11} V_2$$

$$\therefore Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = \underline{\underline{-\frac{2}{11} s}}$$

$Y$ -parameters are

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \underline{\underline{\begin{bmatrix} \frac{5}{11} & -\frac{2}{11} \\ -\frac{2}{11} & \frac{3}{11} \end{bmatrix}}}$$

2nd method

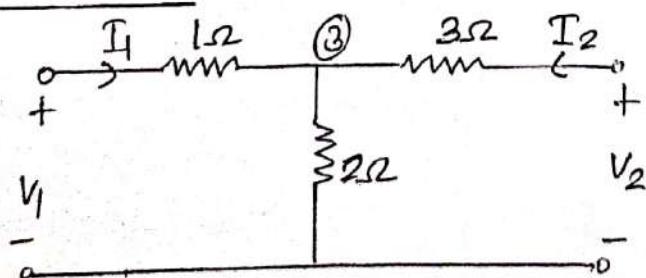

$$I_1 = \frac{V_1 - V_3}{1} = V_1 - V_3 \quad \text{--- } ①$$

$$I_2 = \frac{V_2 - V_3}{3} = \frac{V_2}{3} - \frac{V_3}{3} \quad \text{--- } ②$$

Applying KCL at node 3,

$$I_1 + I_2 = \frac{V_3}{2} \quad \text{--- } ③$$

Substituting ① and ② in ③,

$$V_1 - V_3 + \frac{V_2}{3} - \frac{V_3}{3} = \frac{V_3}{2}$$

$$V_3 \left[ \frac{1}{2} + 1 + \frac{1}{3} \right] = V_1 + \frac{V_2}{3}$$

$$V_3 \left[ \frac{3+6+2}{6} \right] = V_1 + \frac{V_2}{3}$$

$$V_3 \times \frac{11}{6} = V_1 + \frac{V_2}{3}$$

$$V_3 = \frac{6}{11} V_1 + \frac{2}{11} V_2 \quad \text{--- ④}$$

Substituting ④ in ①,

$$I_1 = V_1 - V_3 = V_1 - \frac{6}{11} V_1 - \frac{2}{11} V_2$$

$$= \frac{5}{11} V_1 - \frac{2}{11} V_2 \quad \text{--- ⑤}$$

$$I_2 = \frac{V_2}{3} - \frac{V_3}{3} = \frac{V_2}{3} - \frac{1}{3} \left[ \frac{6}{11} V_1 + \frac{2}{11} V_2 \right]$$

$$= \frac{V_2}{3} - \frac{2}{11} V_1 - \frac{2}{33} V_2$$

$$= -\frac{2}{11} V_1 + V_2 \left[ \frac{1}{3} - \frac{2}{33} \right]$$

$$= -\frac{2}{11} V_1 + V_2 \left[ \frac{11-2}{33} \right]$$


$$= -\frac{2}{11} V_1 + V_2 \times \frac{9}{33}$$

$$= -\frac{2}{11} V_1 + \frac{3}{11} V_2 \quad \text{--- ⑥}$$

Comparing ⑤ and ⑥ with Y-parameter eqns.

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{5}{11} & -\frac{2}{11} \\ -\frac{2}{11} & \frac{3}{11} \end{bmatrix}$$

3. Find Y-parameters of the network.

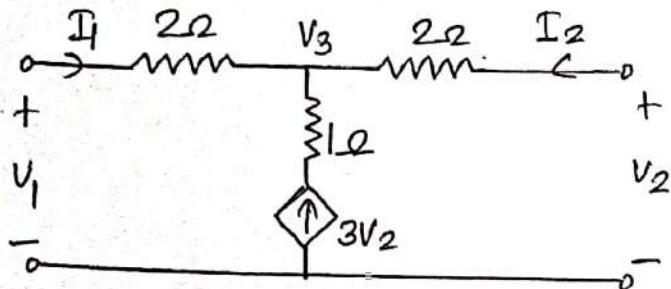

$$I_1 = \frac{V_1 - V_3}{2} = \frac{V_1}{2} - \frac{V_3}{2} \quad \text{--- (1)}$$

$$I_2 = \frac{V_2 - V_3}{2} = \frac{V_2}{2} - \frac{V_3}{2} \quad \text{--- (2)}$$

$$(1) - (2) \Rightarrow I_1 - I_2 = \frac{V_1}{2} - \frac{V_2}{2} \quad \text{--- (4)}$$

Applying KCL at node 3,

$$I_1 + I_2 = -3V_2 \quad \text{--- (3)}$$

$$I_1 - I_2 = \frac{V_1}{2} - \frac{V_2}{2} \quad \text{--- (4)}$$

$$(3) + (4) \Rightarrow 2I_1 = \frac{V_1}{2} - \frac{7}{2}V_2$$

$$\text{or } I_1 = \frac{V_1}{4} - \frac{7}{4}V_2 \quad \text{--- (5)}$$

$$\text{From (3), } I_2 = -3V_2 - I_1$$


$$= -3V_2 - \left( \frac{V_1}{4} - \frac{7}{4}V_2 \right)$$

$$= -\frac{V_1}{4} - \frac{5}{4}V_2 \quad \text{--- (6)}$$

Comparing (5) and (6) with y-parameter eqns,

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{4} & -\frac{7}{4} \\ -\frac{1}{4} & -\frac{5}{4} \end{bmatrix}$$

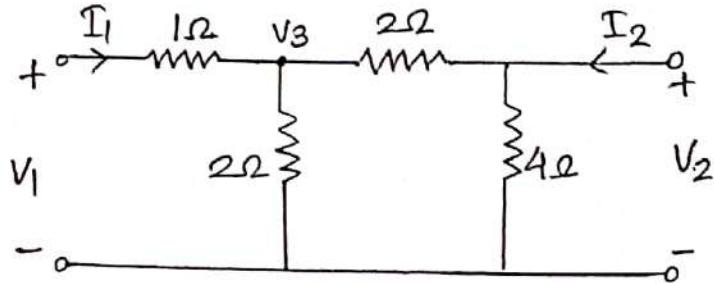1/12/2020 4) Determine Y-parameters of the n/w. Determine whether the n/w is symmetrical and reciprocal.



$$I_1 = \frac{V_1 - V_3}{1} = V_1 - V_3 \quad \text{--- (1)}$$

$$\begin{aligned} I_2 &= \frac{V_2 - V_3}{2} + \frac{V_2}{4} \\ &= \frac{3}{4}V_2 - \frac{V_3}{2} \quad \text{--- (2)} \end{aligned}$$

At node 3

$$\begin{aligned} I_1 &= \frac{V_3}{2} + \frac{V_3 - V_2}{2} \\ &= V_3 - \frac{V_2}{2} \quad \text{--- (3)} \end{aligned}$$

From (1) and (3),

$$V_1 - V_3 = V_3 - \frac{V_2}{2}$$

$$2V_3 = V_1 + \frac{V_2}{2}$$

$$V_3 = \frac{V_1}{2} + \frac{V_2}{4} \quad \text{--- (4)}$$

Substituting  $V_3$  into (1),

$$I_1 = V_1 - V_3 = V_1 - \left( \frac{V_1}{2} + \frac{V_2}{4} \right) = \frac{V_1}{2} - \frac{V_2}{4} \quad \text{--- (5)}$$

Substituting  $V_3$  in (2),

$$\begin{aligned} I_2 &= \frac{3}{4}V_2 - \frac{1}{2}V_3 \\ &= \frac{3}{4}V_2 - \frac{1}{2}\left(\frac{V_1}{2} + \frac{V_2}{4}\right) \\ &= -\frac{1}{4}V_1 + \frac{5}{8}V_2 \quad \text{--- (6)} \end{aligned}$$


Comparing ⑥ and ⑦ with y-parameter eqns.

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{2} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{5}{8} \end{bmatrix}$$


$Y_{11} \neq Y_{22}$   $\therefore$  N/w is not symmetrical.

$Y_{12} \neq Y_{21}$ , hence the n/w is reciprocal.

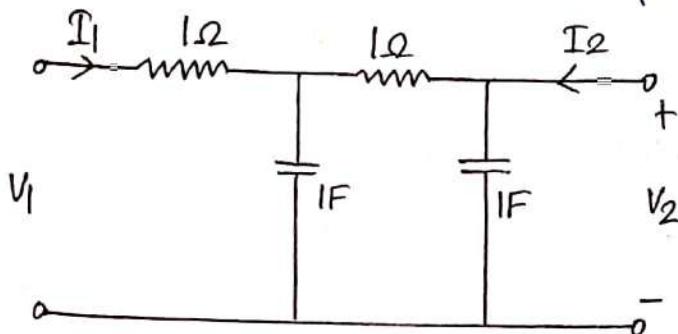5. Determine the short circuit admittance parameters for the n/w.



Transformed n/w

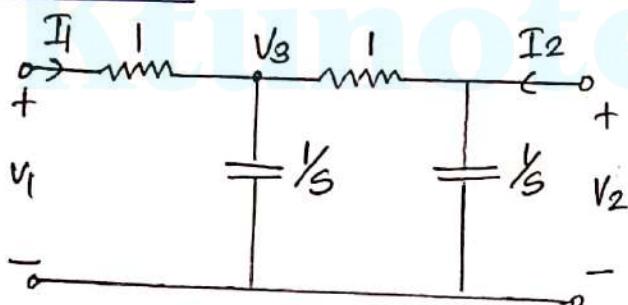

$$I_1 = \frac{V_1 - V_3}{Y_12} = V_1 - V_3 \quad \text{--- } ①$$

KCL at node 3,

$$I_1 = \frac{V_3}{Y_S} + \frac{V_3 - V_2}{Y_21} = (s+1)V_3 - V_2 \quad \text{--- } ②$$

$$I_2 = \frac{V_2}{Y_S} + \frac{V_2 - V_3}{Y_12} = (s+1)V_2 - V_3 \quad \text{--- } ③$$

From ① and ②,

$$V_1 - V_3 = (s+1)V_3 - V_2$$

$$(s+2)V_3 = V_1 + V_2$$

$$\therefore V_3 = \frac{1}{s+2}V_1 + \frac{1}{s+2}V_2 \quad \text{--- } ④$$

Substituting  $V_3$  in ①,

$$I_1 = V_1 - V_3 = V_1 - \frac{1}{s+2}V_1 - \frac{1}{s+2}V_2$$

$$I_1 = \frac{s+1}{s+2}V_1 - \frac{1}{s+2}V_2 \quad \text{--- ⑤}$$

Substituting  $V_3$  in ③,

$$I_2 = (s+1)V_2 - V_3 = (s+1)V_2 - \frac{1}{s+2}V_1 - \frac{1}{s+2}V_2$$


$$= -\frac{1}{s+2}V_1 + V_2 \left[ \frac{(s+1)(s+2) - 1}{s+2} \right]$$

$$= -\frac{1}{s+2}V_1 + \frac{s^2 + 3s + 1}{s+2}V_2 \quad \text{--- ⑥}$$

Comparing ⑤ and ⑥ with Y-parameter eqns.

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{s+1}{s+2} & -\frac{1}{s+2} \\ -\frac{1}{s+2} & \frac{s^2 + 3s + 1}{s+2} \end{bmatrix}$$

6. Determine Y-parameters of the nw.

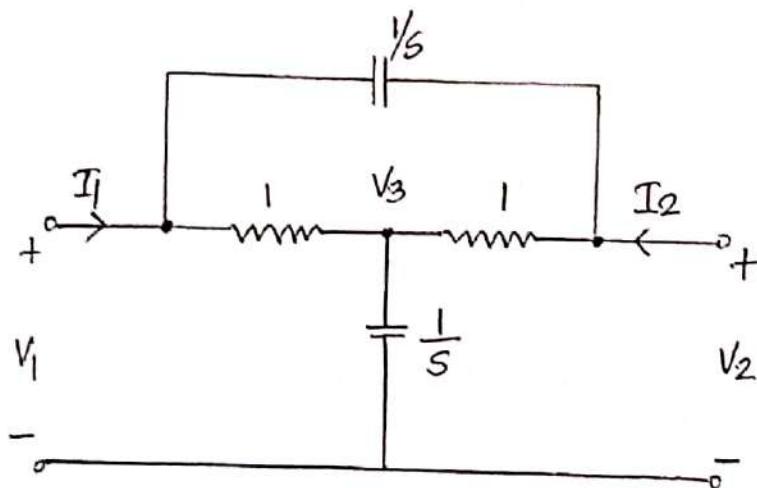

Applying KCL at Node 1.

$$I_1 = \frac{V_1 - V_3}{1} + \frac{V_1 - V_2}{\frac{1}{s}} = (s+1)V_1 - sV_2 - V_3 \quad \text{--- ①}$$

Applying KCL at node 2:

$$I_2 = \frac{V_2 - V_3}{1} + \frac{V_2 - V_1}{\frac{1}{s}}$$

$$= (s+1)V_2 - sV_1 - V_3 \quad \text{--- (2)}$$

Applying KCL at node 3

$$\frac{V_3}{Y_S} + \frac{V_3 - V_1}{1} + \frac{V_3 - V_2}{1} = 0$$

$$V_3(s+2) - V_1 - V_2 = 0$$

$$V_3 = \frac{1}{s+2}V_1 + \frac{1}{s+2}V_2 \quad \text{--- (3)}$$

Substituting  $V_3$  in (1),

$$\begin{aligned} I_1 &= (s+1)V_1 - sV_2 - \left[ \frac{1}{s+2}V_1 + \frac{1}{s+2}V_2 \right] \\ &= \left[ \frac{(s+1)(s+2)-1}{s+2} \right] V_1 - \left[ \frac{s(s+2)+1}{s+2} \right] V_2 \\ &= \left[ \frac{s^2+3s+1}{s+2} \right] V_1 - \left[ \frac{s^2+2s+1}{s+2} \right] V_2 \quad \text{--- (4)} \end{aligned}$$

Substituting  $V_3$  in (2),

$$\begin{aligned} I_2 &= (s+1)V_2 - sV_1 - \left[ \frac{1}{s+2}V_1 + \frac{1}{s+2}V_2 \right] \\ &= - \left[ \frac{s(s+2)+1}{s+2} \right] V_1 + \left[ \frac{(s+1)(s+2)-1}{s+2} \right] V_2 \\ &= - \left[ \frac{s^2+2s+1}{s+2} \right] V_1 + \left[ \frac{s^2+3s+1}{s+2} \right] V_2 \quad \text{--- (5)} \end{aligned}$$

Comparing (4) and (5) with Y-parameter eqns.

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{s^2+3s+1}{s+2} & -\frac{(s^2+2s+1)}{s+2} \\ -\frac{(s^2+2s+1)}{s+2} & \frac{s^2+3s+1}{s+2} \end{bmatrix}$$


## TRANSMISSION PARAMETERS

The transmission parameters or chain parameters or ABCD parameters relate the voltage and current at input port to voltage and current at o/p port.

$$(V_1, I_1) = f(V_2, -I_2)$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

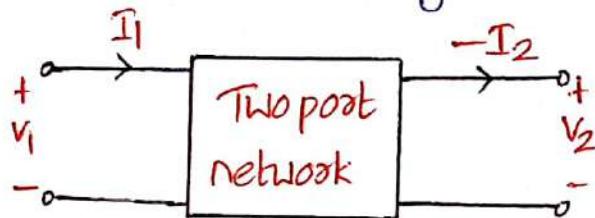

The negative sign is used with  $I_2$  and not for parameters B and D.

The reason for  $-I_2$  is that, in transmission feed, the o/p current is assumed to be coming out of output port and not going into the port.

In matrix form,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \text{ where } \begin{bmatrix} A & B \\ C & D \end{bmatrix} \text{ is called transmission matrix.}$$

CASE 1: When the o/p port is open circuited,  $I_2 = 0$ .

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \text{ - reverse voltage gain with o/p port open circuited.}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \text{ - transfer admittance with o/p open circuited.}$$

CASE 2: When o/p port is short circuited,  $V_2 = 0$ .

$$B = \left. -\frac{V_1}{I_2} \right|_{V_2=0} \text{ - transfer impedance with o/p port short circuited.}$$

$$D = \left. \frac{-I_1}{I_2} \right|_{V_2=0} \text{ - reverse current gain with o/p short circuited.}$$

CONDITION FOR RECIPROCITY

- (a)  $V_s$  applied at input port o/p short circuited.



$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$


$$V_1 = V_s, V_2 = 0, I_2' = -I_2$$

$$V_1 = -BI_2$$

$$V_s = -B \cdot I_2'$$

$$\frac{V_s}{I_2'} = B$$

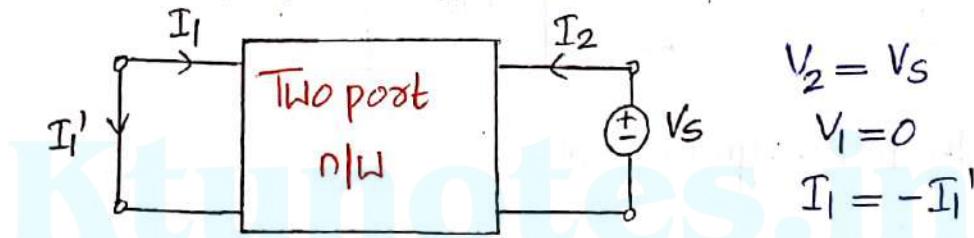- (b)  $V_s$  applied at o/p port with input port short circuited.



$$V_2 = V_s$$

$$V_1 = 0$$

$$I_1 = -I_1'$$

$$0 = AV_2 - BI_2$$

$$0 = AV_s - BI_2 \quad \Rightarrow I_2 = \frac{A}{B} V_s$$

$$-I_1' = CV_2 - DI_2$$

$$-I_1' = CV_s - DI_2$$

$$= CV_s - \frac{DA}{B} V_s$$

$$= V_s \left[ \frac{BC - AD}{B} \right]$$

$$\frac{V_s}{I_1'} = \frac{B}{AD - BC}$$

For the n/w to be reciprocal,  $\frac{V_s}{I_2} = \frac{V_s}{I_1'}$

$$B = \frac{B}{AD - BC}$$

$$\text{i.e. } \underline{\underline{AD - BC = 1}}$$

## CONDITION FOR SYMMETRY

① When the o/p port is open circuited,

$$I_2 = 0, V_1 = V_s$$

$$V_s = AV_2 \Rightarrow V_2 = \frac{V_s}{A}$$

$$I_1 = CV_2$$

$$= C \frac{V_s}{A}$$

$$\frac{V_s}{I_1} = \frac{A}{C}$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$




② When the input port is open circuited,  $I_1 = 0; V_2 = V_s$ .

$$0 = CV_s - DI_2$$

$$CV_s = DI_2$$

$$\frac{V_s}{I_2} = \frac{D}{C}$$

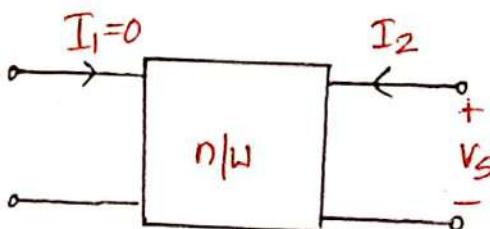


For the n/w to be symmetrical,

$$\frac{V_s}{I_1} = \frac{V_s}{I_2}$$

$$\frac{A}{C} = \frac{D}{C} \Rightarrow \underline{\underline{A=D}}$$

## PROBLEMS

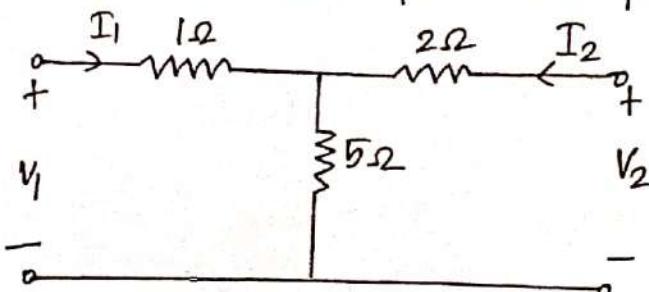1. Find the transmission parameters for the n/w shown in fig.



$$V_1 = AV_2 - BI_2$$


$$I_1 = CV_2 - DI_2$$

### First method

Case-I: o/p port open circuited,  $I_2 = 0$

From ckt,  $V_1 = 6I_1, V_2 = 5I_1$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{6I_1}{5I_1} = \underline{\underline{\frac{6}{5}}}$$

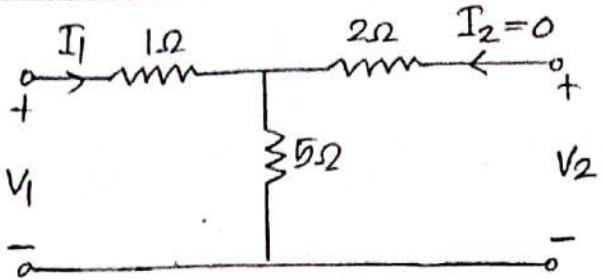


$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{I_1}{5I_1} = \underline{\underline{\frac{1}{5}}}$$

Case - 2: When o/p port is short circuited.  $V_2 = 0$

$$R_{eq} = 1 + (5||2)$$
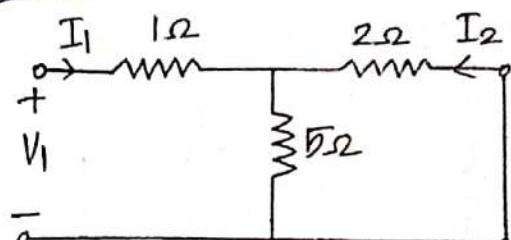
$$= 1 + \frac{5 \times 2}{5+2} = 1 + \frac{10}{7} = \frac{17}{7} \Omega$$



$$V_1 = R_{eq} \cdot I_1 = \frac{17}{7} I_1$$

$$I_2 = -I_1 \times \frac{5}{7} = -\frac{5}{7} I_1$$

$$B = -\frac{V_1}{I_2} \Big|_{V_2=0} = \frac{-\frac{17}{7} I_1}{-\frac{5}{7} I_1} = \underline{\underline{\frac{17}{5}}}$$

$$D = -\frac{I_1}{I_2} \Big|_{V_2=0} = \frac{-I_1}{-\frac{5}{7} I_1} = \underline{\underline{\frac{7}{5}}}$$

2nd method

$$V_1 = 6I_1 + 5I_2 \quad \textcircled{1}$$


$$V_2 = 5I_1 + 7I_2 \quad \textcircled{2}$$

$$5I_1 = V_2 - 7I_2$$

$$I_1 = \frac{1}{5}V_2 - \frac{7}{5}I_2 \quad \textcircled{3}$$

Substituting  $\textcircled{3}$  in  $\textcircled{1}$ ,
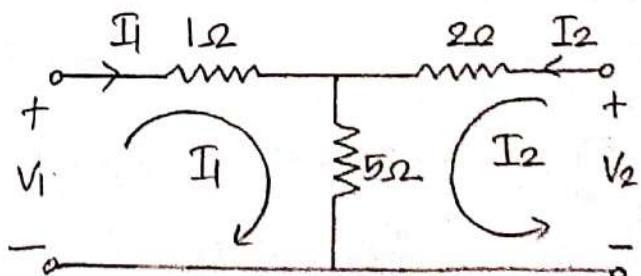
$$\begin{aligned} V_1 &= 6I_1 + 5I_2 = 6\left(\frac{1}{5}V_2 - \frac{7}{5}I_2\right) + 5I_2 \\ &= \frac{6}{5}V_2 - \frac{42}{5}I_2 + 5I_2 \end{aligned}$$




$$= \frac{6}{5}V_2 - \frac{17}{5}I_2 \quad \text{--- (4)}$$


Comparing (3) and (4) with transmission parameter eqns.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{6}{5} & \frac{17}{5} \\ \frac{1}{5} & \frac{7}{5} \end{bmatrix}$$

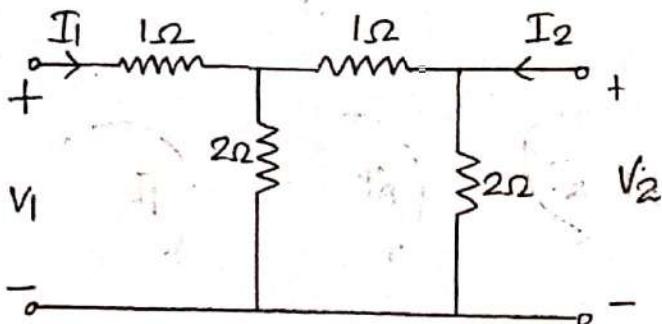2. Obtain the ABCD parameters for the nlu.



Redrawing the nlu

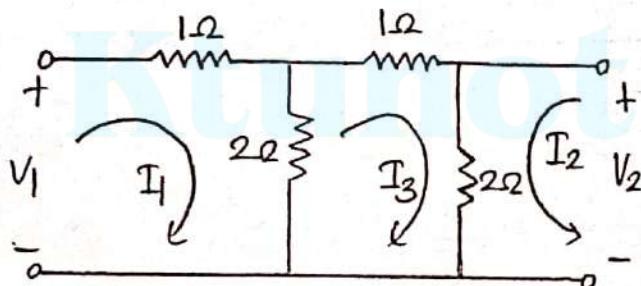

$$\text{Mesh-1: } V_1 = 3I_1 - 2I_3 \quad \text{--- (1)}$$

$$\text{Mesh-3: } V_2 = 2I_2 + 2I_3 \quad \text{--- (2)}$$

$$\text{Mesh-2: } 5I_3 - 2I_1 + 2I_2 = 0$$

$$I_3 = \frac{2}{5}I_1 - \frac{2}{5}I_2 \quad \text{--- (3)}$$

Substituting (3) in (1),

$$\begin{aligned} V_1 &= 3I_1 - 2I_3 = 3I_1 - 2\left(\frac{2}{5}I_1 - \frac{2}{5}I_2\right) = 3I_1 - \frac{4}{5}I_1 + \frac{4}{5}I_2 \\ &= \frac{11}{5}I_1 + \frac{4}{5}I_2 \quad \text{--- (4)} \end{aligned}$$

Substituting ③ in ②,

$$V_2 = 2I_2 + 2I_3 = 2I_2 + 2\left[\frac{2}{5}I_1 - \frac{2}{5}I_2\right] \\ = \frac{4}{5}I_1 + \frac{6}{5}I_2$$

$$\frac{4}{5}I_1 = V_2 - \frac{6}{5}I_2$$

$$I_1 = \frac{5}{4}V_2 - \frac{3}{2}I_2 \quad \text{--- ⑤}$$


Substituting ⑤ in ④,

$$V_1 = \frac{11}{5}I_1 + \frac{4}{5}I_2 = \frac{11}{5}\left[\frac{5}{4}V_2 - \frac{3}{2}I_2\right] + \frac{4}{5}I_2 \\ = \frac{11}{4}V_2 - \frac{33}{10}I_2 + \frac{4}{5}I_2 \\ = \frac{11}{4}V_2 - \frac{25}{10}I_2 \\ = \frac{11}{4}V_2 - \frac{5}{2}I_2 \quad \text{--- ⑥}$$

Comparing ⑥ and ⑤ with ABCD parameter eqns:

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{11}{4} & \frac{5}{2} \\ \frac{5}{4} & \frac{3}{2} \end{bmatrix}$$

3|2|2020 3) Determine transmission parameters for the n/w.

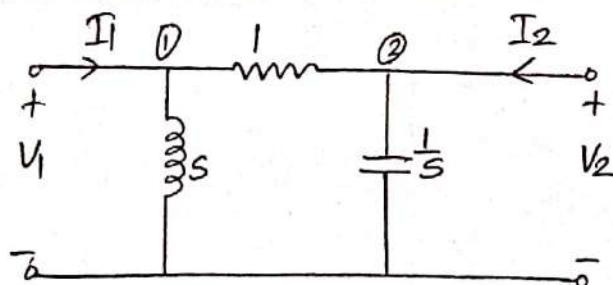

Applying KCL at node -1

$$I_1 = \frac{V_1}{s} + \frac{V_1 - V_2}{1} = V_1\left(\frac{1}{s} + 1\right) - V_2$$

$$= \frac{(s+1)}{s} V_1 - V_2 \quad \text{--- (1)}$$

KCL at node 2

$$I_2 = \frac{V_2}{1/s} + \frac{V_2 - V_1}{1} = sV_2 + V_2 - V_1 \\ = -V_1 + (s+1)V_2$$

$$V_1 = (s+1)V_2 - I_2 \quad \text{--- (2)}$$


Substituting (2) in (1),

$$I_1 = \frac{s+1}{s} [(s+1)V_2 - I_2] - V_2 \\ = \left[ \frac{(s+1)^2 - 1}{s} \right] V_2 - \frac{s+1}{s} I_2 \\ = \left( \frac{s^2 + 2s + 1 - s}{s} \right) V_2 - \frac{s+1}{s} I_2 \\ = \left( \frac{s^2 + s + 1}{s} \right) V_2 - \left( \frac{s+1}{s} \right) I_2 \quad \text{--- (3)}$$

Comparing (2) and (3) with ABCD parameter eqns.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} s+1 & -1 \\ \frac{s^2+s+1}{s} & \frac{s+1}{s} \end{bmatrix}$$

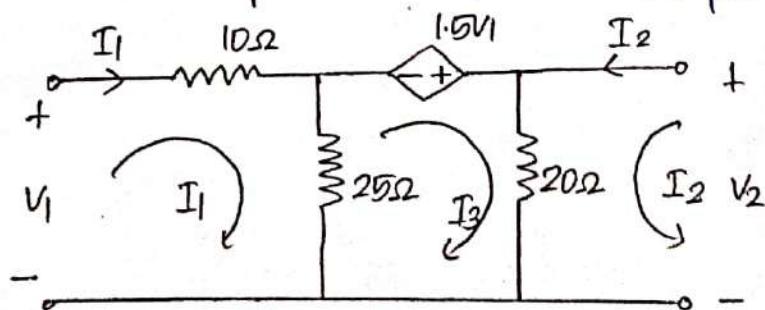4. Find transmission parameters for the two port nlu.



Applying KVL to mesh-1

$$V_1 = 35I_1 - 25I_3 \quad \text{--- (1)}$$

Mesh - 3

$$V_2 = 20I_2 + 20I_3 \quad \text{--- (2)}$$

Mesh - 2

$$45I_3 - 25I_1 + 20I_2 - 15V_1 = 0$$

$$45I_3 - 25I_1 + 20I_2 - 15(35I_1 - 25I_3) = 0$$

$$82.5I_3 - 77.5I_1 + 20I_2 = 0$$

$$I_3 = 0.94I_1 - 0.24I_2 \quad \text{--- (3)}$$

Subst. (3) in (1),

$$\begin{aligned} V_1 &= 35I_1 - 25I_3 = 35I_1 - 25(0.94I_1 - 0.24I_2) \\ &= 11.5I_1 + 6I_2 \quad \text{--- (4)} \end{aligned}$$

Subst. (3) in (2),

$$\begin{aligned} V_2 &= 20I_2 + 20I_3 \\ &= 20I_2 + 20(0.94I_1 - 0.24I_2) \\ &= 18.8I_1 + 15.2I_2 \quad \text{--- (5)} \end{aligned}$$

$$18.8I_1 = V_2 - 15.2I_2$$

$$I_1 = 0.053V_2 - 0.8I_2 \quad \text{--- (6)}$$

Subst. (6) in (4),

$$\begin{aligned} V_1 &= 11.5I_1 + 6I_2 \\ &= 11.5(0.053V_2 - 0.8I_2) + 6I_2 \\ &= 0.61V_2 - 3.32I_2 \quad \text{--- (7)} \end{aligned}$$

Comparing (7) and (6) with ABCD parameters eqns.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.61 & +3.32 \\ 0.053 & +0.81 \end{bmatrix}$$

## HYBRID PARAMETERS (h-parameters)

The hybrid parameters of a two port n/w may be defined by expressing  $V_1$  and  $I_2$  in terms of  $I_1$  and  $V_2$ .

$$(V_1, I_2) = f(I_1, V_2)$$

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

In matrix form,

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Individual h-parameters can be defined by setting  $I_1=0$  and  $V_2=0$ .

Case-1 :

When o/p port is short circuited,  $V_2=0$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} : h_{11} - \text{short circuit input impedance.}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} : h_{21} - \text{short circuit forward current gain.}$$

Case-2 :

When the input is open circuited,  $I_1=0$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$h_{12}$  - the open circuited reverse voltage gain


$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

$h_{22}$  - the open circuit o/p admittance

These four parameters are not dimensionally alike, hence they are called

hybrid parameters.

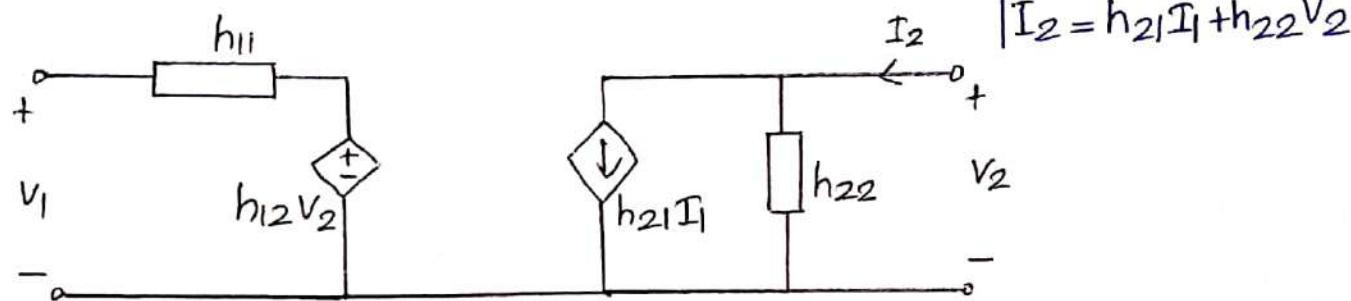
- The equivalent circuit of a two port n/w in terms of hybrid parameters is shown below.



Ktunotes.in


hybrid parameters.

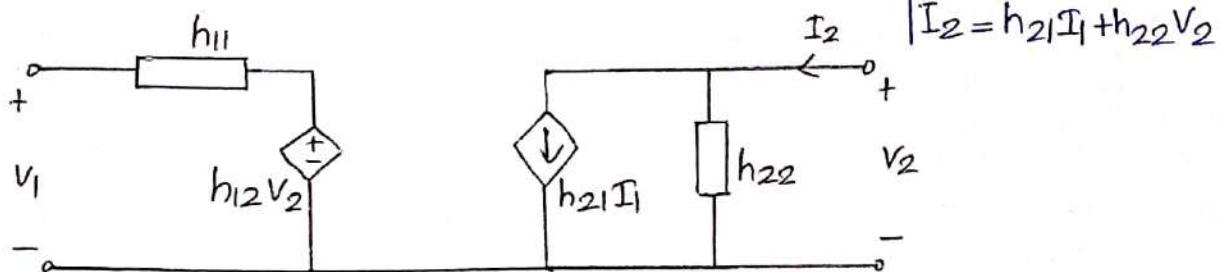- The equivalent circuit of a two port n/w in terms of hybrid parameters is shown below.


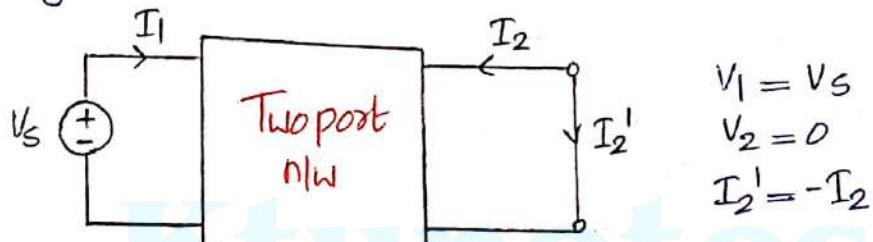
#### 14/12/20 CONDITION FOR RECIPROCITY

- ① Voltage  $V_s$  applied at input port and o/p port short circuited.



From h-parameter eqns.

$$V_s = h_{11}I_1$$

$$-I_2' = h_{21}I_1 \Rightarrow I_1 = \frac{-I_2'}{h_{21}}$$

$$\therefore V_s = h_{11} \times \frac{-I_2'}{h_{21}}$$

$$\frac{V_s}{I_2'} = -\frac{h_{11}}{h_{21}}$$

- ② Voltage  $V_s$  applied at the o/p port with the input port short circuited.



$$V_1 = 0, V_2 = V_s, I_1 = -I_1'$$

$$0 = h_{11}I_1 + h_{12}V_s$$

$$h_{12}V_6 = -h_{11}I_1 = h_{11}I_1'$$

$$\frac{V_s}{I_1'} = \frac{h_{11}}{h_{12}}$$

For the n/w to be reciprocal,

$$\frac{V_s}{I_2'} = \frac{V_s}{I_1'}$$

$$\underline{h_{21} = -h_{12}}$$

### CONDITION FOR SYMMETRY

Condition for symmetry is obtained from  $\pi$ -parameters

$$\begin{aligned}\pi_{11} &= \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{h_{11}I_1 + h_{12}V_2}{I_1} \\ &= h_{11} + h_{12} \frac{V_2}{I_1} \quad \text{--- (1)}\end{aligned}$$

$$\begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$$

$$\therefore I_2 = 0, 0 = h_{21}I_1 + h_{22}V_2$$

$$-h_{21}I_1 = h_{22}V_2$$

$$\frac{V_2}{I_1} = -\frac{h_{21}}{h_{22}} \quad \text{--- (2)}$$

Substituting (2) in (1),

$$\begin{aligned}\therefore \pi_{11} &= h_{11} + h_{12} \cdot -\frac{h_{21}}{h_{22}} \\ &= \frac{h_{11}h_{22} - h_{12}h_{21}}{h_{22}} \\ &= \frac{\Delta h}{h_{22}} \quad \text{where } \Delta h = h_{11}h_{22} - h_{12}h_{21}\end{aligned}$$

Similarly,

$$\pi_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{1}{h_{22}}$$

For a symmetrical nlu,  $z_{11} = z_{22}$

$$\frac{\Delta h}{h_{22}} = \frac{1}{h_{22}}$$

$$\Rightarrow \Delta h = 1$$

$$\underline{h_{11}h_{22} - h_{12}h_{21} = 1}$$

### PROBLEMS

1. Find out h-parameters from the following data.

(a) With the op post short circuited :  $V_1 = 25V, I_1 = 1A, I_2 = 2A$

(b) With the input post open circuited :  $V_1 = 10V, V_2 = 50V, I_2 = 2A$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{25}{1} = 25\Omega$$


$$\begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{10}{50} = 0.2$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{2}{1} = 2$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{2}{50} = 0.04$$

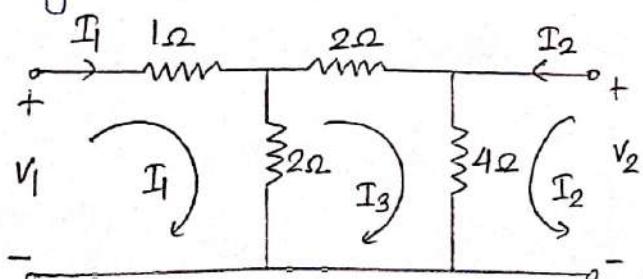2. Determine hybrid parameters of the nlu. Determine whether the nlu is reciprocal.




### First Method

CASE I: When port -2 is short circuited,  $V_2 = 0$

$$Req = 1 + 2 \parallel 2 = 2\Omega$$


$$V_1 = 2I_1$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = 2\Omega$$

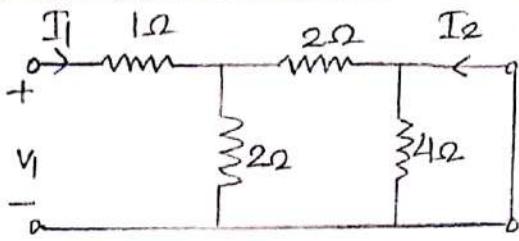

$$I_2 = -I_1 \times \frac{2}{2+2} = -\frac{I_1}{2}$$

$$h_{21} = \left. \frac{I_2}{V_2} \right|_{V_2=0} = -\frac{1}{2}$$

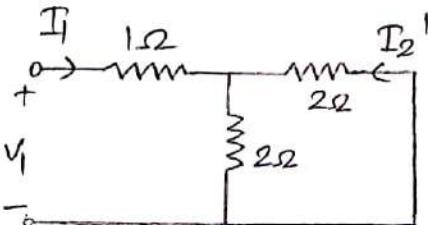

### Case - 2

When port-2 is open circuited,  $I_1 = 0$

$$Req = 4 \parallel 4 = 2\Omega$$

$$V_1 = 2I_y \quad I_y = I_x = \frac{I_2}{2}$$

$$I_y = \frac{I_2}{2}$$

$$V_2 = 4I_x$$

$$I_x = \frac{I_2}{2}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{2I_y}{4I_x} = \frac{1}{2}$$

$$h_{22} = \left. \frac{V_2}{V_2} \right|_{I_1=0} = \frac{2I_x}{4I_x} = \frac{1}{2}s$$

Hence h-parameters are,

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 2 & \frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

~~=====~~

## 2nd Method

Mesh - 1

$$V_1 = 3I_1 - 2I_3 \quad \text{--- (1)}$$

Mesh - 3

$$V_2 = 4I_2 + 4I_3 \quad \text{--- (2)}$$

Mesh - 2

$$8I_3 - 2I_1 + 4I_2 = 0$$

$$8I_3 = 2I_1 - 4I_2$$

$$I_3 = \frac{I_1}{4} - \frac{I_2}{2} \quad \text{--- (3)}$$

Subst. (3) in (1),

$$\begin{aligned} V_1 &= 3I_1 - 2I_3 = 3I_1 - 2\left(\frac{I_1}{4} - \frac{I_2}{2}\right) \\ &= \frac{5}{2}I_1 + I_2 \quad \text{--- (4)} \end{aligned}$$

Subs (3) in (2),

$$\begin{aligned} V_2 &= 4I_2 + 4I_3 = 4I_2 + 4\left(\frac{I_1}{4} - \frac{I_2}{2}\right) \\ &= 4I_2 + I_1 - 2I_2 \\ &= I_1 + 2I_2 \end{aligned}$$

$$2I_2 = -I_1 + V_2$$

$$\therefore I_2 = -\frac{1}{2}I_1 + \frac{1}{2}V_2 \quad \text{--- (5)}$$

Subs (5) in (4),

$$\begin{aligned} V_1 &= \frac{5}{2}I_1 + I_2 \\ &= \frac{5}{2}I_1 + \left(-\frac{1}{2}I_1 + \frac{1}{2}V_2\right) \\ &= 2I_1 + \frac{1}{2}V_2 \quad \text{--- (6)} \end{aligned}$$

Comparing ⑤ and ⑥ with h-parameter eqns.

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 2 & \frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

$\therefore h_{12} = -h_{21}$  the N/W is reciprocal

## 15/12/20 INTER-RELATIONSHIP AMONG PARAMETERS

When it is required to find out two or more parameters of a particular N/W, then finding each parameter will be tedious. But if we find a particular parameter then the other parameters can be found if the inter-relationship between them is known.

Z-parameters in terms of other parameters

1. Z-parameters in terms of Y-parameters

We know that,

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$\left| \begin{array}{l} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \end{array} \right.$$

By cramer's rule,

$$V_1 = \frac{\begin{vmatrix} I_1 & Y_{12} \\ I_2 & Y_{22} \end{vmatrix}}{\begin{vmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{vmatrix}} = \frac{Y_{22} I_1 - Y_{12} I_2}{Y_{11} Y_{22} - Y_{12} Y_{21}} = \frac{Y_{22} I_1}{\Delta Y} - \frac{Y_{12} I_2}{\Delta Y} \quad \text{--- ①}$$

Where  $\Delta Y = Y_{11} Y_{22} - Y_{12} Y_{21}$

$$V_2 = \frac{\begin{vmatrix} Y_{11} & I_1 \\ Y_{21} & I_2 \end{vmatrix}}{\Delta Y} = \frac{Y_{11} I_2}{\Delta Y} - \frac{Y_{21} I_1}{\Delta Y} = \frac{-Y_{21} I_1}{\Delta Y} + \frac{Y_{11} I_2}{\Delta Y} \quad \text{--- ②}$$

Comparing ① and ② with Z-parameter eqns.

$$Z_{11} = \frac{Y_{22}}{\Delta Y}, Z_{12} = \frac{-Y_{12}}{\Delta Y}$$

$$Z_{21} = \frac{-Y_{21}}{\Delta Y}, Z_{22} = \frac{Y_{11}}{\Delta Y}$$

2. Z-parameters in terms of ABCD parameters.

$$V_1 = AV_2 - BI_2 \quad \text{--- } ①$$

$$I_1 = CV_2 - DI_2 \quad \text{--- } ②$$

From ②,  $CV_2 = I_1 + DI_2$

$$V_2 = \frac{1}{C}I_1 + \frac{D}{C}I_2 \quad \text{--- } ③$$

Subs. ③ in ①,

$$\begin{aligned} V_1 &= A \left[ \frac{1}{C}I_1 + \frac{D}{C}I_2 \right] - BI_2 \\ &= \frac{A}{C}I_1 + \left( \frac{AD}{C} - B \right)I_2 \\ &= \frac{A}{C}I_1 + \left( \frac{AD - BC}{C} \right)I_2 \quad \text{--- } ④ \end{aligned}$$

Comparing ④ and ③ with Z-parameter eqns.

$$Z_{11} = \frac{A}{C}, Z_{12} = \frac{AD - BC}{C}$$

$$Z_{21} = \frac{1}{C}, Z_{22} = \frac{D}{C}$$

3. Z-parameters in terms of h-parameters

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad \text{--- } ①$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \text{--- } ②$$

From ②,  $h_{22}V_2 = I_2 - h_{21}I_1$

$$V_2 = -\frac{h_{21}}{h_{22}}I_1 + \frac{1}{h_{22}}I_2 \quad \text{--- } ③$$

Subst. ③ in ①,

$$\begin{aligned}
 V_1 &= h_{11} I_1 + h_{12} \left[ -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \right] \\
 &= I_1 \left[ h_{11} - \frac{h_{12} h_{21}}{h_{22}} \right] + \frac{h_{12}}{h_{22}} I_2 \\
 &= I_1 \left[ \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \right] + \frac{h_{12}}{h_{22}} I_2 \quad \text{--- ④}
 \end{aligned}$$

Comparing ④ and ③ with  $\pi$ -parameter eqns.

$$Z_{11} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} = \frac{\Delta h}{h_{22}} ; Z_{12} = \frac{h_{12}}{h_{22}}$$

$$Z_{21} = -\frac{h_{21}}{h_{22}} ; Z_{22} = \frac{1}{h_{22}}$$

Y-parameters in terms of other parameters

### 1. Y-parameters in terms of $\pi$ -parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

By cramer's rule,

$$I_1 = \frac{\begin{vmatrix} V_1 & Z_{12} \\ V_2 & Z_{22} \end{vmatrix}}{\begin{vmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix}} = \frac{Z_{22} V_1 - Z_{12} V_2}{Z_{11} Z_{22} - Z_{12} Z_{21}} = \frac{Z_{22}}{\Delta Z} V_1 - \frac{Z_{12}}{\Delta Z} V_2 \quad \text{--- ①}$$

Where  $\Delta Z = Z_{11} Z_{22} - Z_{12} Z_{21}$

$$I_2 = \frac{\begin{vmatrix} Z_{11} & V_1 \\ Z_{21} & V_2 \end{vmatrix}}{\Delta Z} = \frac{Z_{11} V_2 - Z_{21} V_1}{\Delta Z} = -\frac{Z_{21}}{\Delta Z} V_1 + \frac{Z_{11}}{\Delta Z} V_2 \quad \text{--- ②}$$

Comparing ① and ② with Y-parameter eqns.

$$Y_{11} = \frac{Z_{22}}{\Delta Z}, Y_{12} = -\frac{Z_{12}}{\Delta Z}$$

$$Y_{21} = -\frac{Z_{21}}{\Delta Z}, Y_{22} = \frac{Z_{11}}{\Delta Z}$$

2. Y-parameters in terms of ABCD parameters.

$$V_1 = AV_2 - BI_2 \quad \textcircled{1}$$

$$I_1 = CV_2 - DI_2 \quad \textcircled{2}$$

From ①,  $BI_2 = AV_2 - V_1$

$$I_2 = -\frac{1}{B}V_1 + \frac{A}{B}V_2 \quad \textcircled{3}$$

Substituting ③ in ②,

$$\begin{aligned} I_1 &= CV_2 - D\left[-\frac{1}{B}V_1 + \frac{A}{B}V_2\right] \\ &= \frac{D}{B}V_1 + \left[C - \frac{AD}{B}\right]V_2 = \frac{D}{B}V_1 + \frac{[BC - AD]}{B}V_2 \end{aligned} \quad \textcircled{4}$$

Comparing ④ and ③ with y-parameter eqns

$$Y_{11} = \frac{D}{B}, Y_{12} = \frac{BC - AD}{B}$$

$$Y_{21} = -\frac{1}{B}, Y_{22} = \frac{A}{B}$$

3. Y-parameters in terms of hybrid-parameters

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad \textcircled{1}$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \textcircled{2}$$

From ①,

$$h_{11}I_1 = V_1 - h_{12}V_2$$

$$I_1 = \frac{1}{h_{11}}V_1 - \frac{h_{12}}{h_{11}}V_2 \quad \textcircled{3}$$

Subst ③ in ②,

$$\begin{aligned} I_2 &= h_{21} \left[ \frac{1}{h_{11}} v_1 - \frac{h_{12}}{h_{11}} v_2 \right] + h_{22} v_2 \\ &= \frac{h_{21}}{h_{11}} v_1 + \left[ h_{22} - \frac{h_{12} h_{21}}{h_{11}} \right] v_2 \\ &= \frac{h_{21}}{h_{11}} v_1 + \left[ \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{11}} \right] v_2 \end{aligned} \quad \text{--- } ④$$

Comparing ③ and ④ with  $y$ -parameter eqns.

$$Y_{11} = \frac{1}{h_{11}}, \quad Y_{12} = -\frac{h_{12}}{h_{11}}$$

$$Y_{21} = \frac{h_{21}}{h_{11}}, \quad Y_{22} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{11}} = \frac{\Delta h}{h_{11}}$$

16/12/20 ABCD parameters in terms of other parameters

### 1. ABCD parameters in terms of $\pi$ -parameters

$$V_1 = \pi_{11} I_1 + \pi_{12} I_2 \quad \text{--- } ①$$

$$V_1 = A V_2 - B I_2$$

$$V_2 = \pi_{21} I_1 + \pi_{22} I_2 \quad \text{--- } ②$$

$$I_1 = C V_2 - D I_2$$

From ②,

$$\pi_{21} I_1 = V_2 - \pi_{22} I_2$$

$$I_1 = \frac{1}{\pi_{21}} V_2 - \frac{\pi_{22}}{\pi_{21}} I_2 \quad \text{--- } ③$$

Subs ③ in ①,

$$\begin{aligned} V_1 &= \pi_{11} \left[ \frac{1}{\pi_{21}} V_2 - \frac{\pi_{22}}{\pi_{21}} I_2 \right] + \pi_{12} I_2 \\ &= \frac{\pi_{11}}{\pi_{21}} V_2 - \frac{\pi_{11} \pi_{22}}{\pi_{21}} I_2 + \pi_{12} I_2 \\ &= \frac{\pi_{11}}{\pi_{21}} V_2 - \left[ \frac{\pi_{11} \pi_{22} - \pi_{12} \pi_{21}}{\pi_{21}} \right] I_2 \end{aligned} \quad \text{--- } ④$$

Comparing ④ and ③ with ABCD parameter eqns.

$$A = \frac{Z_{11}}{Z_{21}}, B = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}} = \frac{\Delta Z}{Z_{21}}$$

$$C = \frac{1}{Z_{21}}, D = \frac{Z_{22}}{Z_{21}}$$

## 2. ABCD parameters in terms of Y-parameters

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- } ①$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- } ②$$

From ②,  $V_1 = -Y_{22}V_2 + I_2$

$$V_1 = -\frac{Y_{22}}{Y_{21}}V_2 + \frac{1}{Y_{21}}I_2 \quad \text{--- } ③$$

Subs ③ in ①,

$$\begin{aligned} I_1 &= Y_{11} \left[ -\frac{Y_{22}}{Y_{21}}V_2 + \frac{1}{Y_{21}}I_2 \right] + Y_{12}V_2 \\ &= \left[ Y_{12} - \frac{Y_{11}Y_{22}}{Y_{21}} \right] V_2 + \frac{Y_{11}}{Y_{21}}I_2 \\ &= \left[ \frac{Y_{12}Y_{21} - Y_{11}Y_{22}}{Y_{21}} \right] V_2 + \frac{Y_{11}}{Y_{21}}I_2 \quad \text{--- } ④ \end{aligned}$$

Comparing ③ and ④ with ABCD parameter eqns.

$$A = -\frac{Y_{22}}{Y_{21}}, B = -\frac{1}{Y_{21}}$$

$$C = \frac{Y_{12}Y_{21} - Y_{11}Y_{22}}{Y_{21}} = -\frac{\Delta Y}{Y_{21}}$$

$$D = -\frac{Y_{11}}{Y_{21}}$$

### 3. ABCD parameters in terms of hybrid parameters

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \text{--- (2)}$$

From (2),

$$h_{21}I_1 = I_2 - h_{22}V_2$$

$$I_1 = -\frac{h_{22}}{h_{21}}V_2 + \frac{1}{h_{21}}I_2 \quad \text{--- (3)}$$

Subs. (3) in (1),

$$\begin{aligned} V_1 &= h_{11} \left[ -\frac{h_{22}}{h_{21}}V_2 + \frac{1}{h_{21}}I_2 \right] + h_{12}V_2 \\ &= \left[ h_{12} - \frac{h_{11}h_{22}}{h_{21}} \right] V_2 + \frac{h_{11}}{h_{21}}I_2 \\ &= \left[ \frac{h_{12}h_{21} - h_{11}h_{22}}{h_{21}} \right] V_2 + \frac{h_{11}}{h_{21}}I_2 \quad \text{--- (4)} \end{aligned}$$

Comparing (4) and (3) with ABCD parameter eqns.

$$A = \frac{h_{12}h_{21} - h_{11}h_{22}}{h_{21}} = -\frac{\Delta h}{h_{21}}, \quad B = -\frac{h_{11}}{h_{21}}$$

$$C = -\frac{h_{22}}{h_{21}}, \quad D = -\frac{1}{h_{21}}$$

### Hybrid parameters in terms of other parameters.

#### 1. Hybrid parameters in terms of Z-parameters.

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{--- (2)}$$

From (2),

$$Z_{22}I_2 = V_2 - Z_{21}I_1$$

$V_1 = h_{11}I_1 + h_{12}V_2$
$I_2 = h_{21}I_1 + h_{22}V_2$

$$I_2 = -\frac{Z_{21}}{Z_{22}} I_1 + \frac{1}{Z_{22}} V_2 \quad \text{--- (3)}$$

Subst. (3) in (1),

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} \left[ -\frac{Z_{21}}{Z_{22}} I_1 + \frac{1}{Z_{22}} V_2 \right] \\ &= \left[ Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22}} \right] I_1 + \frac{Z_{12}}{Z_{22}} V_2 \\ &= \left[ \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}} \right] I_1 + \frac{Z_{12}}{Z_{22}} V_2 \quad \text{--- (4)} \end{aligned}$$

Comparing (4) and (3) with h-parameter eqns.

$$h_{11} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}} = \frac{\Delta Z}{Z_{22}}$$

$$h_{12} = \frac{Z_{12}}{Z_{22}}$$

$$h_{21} = -\frac{Z_{21}}{Z_{22}}$$

$$h_{22} = \frac{1}{Z_{22}}$$

## 2. Hybrid parameters in terms of Y-parameters

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$

From (1),

$$Y_{11} V_1 = I_1 - Y_{12} V_2$$

$$V_1 = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \quad \text{--- (3)}$$

Subs (3) in (2),

$$I_2 = Y_{21} \left[ \frac{I_1}{Y_{11}} - \frac{Y_{12}}{Y_{11}} V_2 \right] + Y_{22} V_2$$

$$\begin{aligned}
 &= \left[ Y_{22} - \frac{Y_{12}Y_{21}}{Y_{11}} \right] V_2 + \frac{Y_{21}}{Y_{11}} I_1 \\
 &= \left[ \frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{11}} \right] V_2 + \frac{Y_{21}}{Y_{11}} I_1 \quad \text{--- (4)}
 \end{aligned}$$

Comparing (3) and (4) with h-parameter equations.

$$h_{11} = \frac{1}{Y_{11}}, \quad h_{12} = -\frac{Y_{12}}{Y_{11}}$$

$$h_{21} = \frac{Y_{21}}{Y_{11}}, \quad h_{22} = \frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{11}} = \frac{\Delta Y}{Y_{11}}$$

3. Hybrid parameters in terms of ABCD parameters.

$$V_1 = AV_2 - BI_2 \quad \text{--- (1)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (2)}$$

From (2),

$$DI_2 = -I_1 + CV_2$$

$$I_2 = -\frac{1}{D}I_1 + \frac{C}{D}V_2 \quad \text{--- (3)}$$

Substituting in (1),

$$\begin{aligned}
 V_1 &= AV_2 - B \left[ -\frac{1}{D}I_1 + \frac{C}{D}V_2 \right] \\
 &= \frac{B}{D}I_1 + \left[ A - \frac{BC}{D} \right] V_2 \\
 &= \frac{B}{D}I_1 + \left[ \frac{AD - BC}{D} \right] V_2 \quad \text{--- (4)}
 \end{aligned}$$


Comparing (4) and (3) with h-parameter eqns.

$$h_{11} = \frac{B}{D}, \quad h_{12} = \frac{AD - BC}{D} = \frac{\Delta T}{D}$$

$$h_{21} = \frac{-1}{D}, \quad h_{22} = \frac{C}{D}$$

17/12/20 INTERCONNECTION OF TWO-PORT nLNs

1. Cascade connection

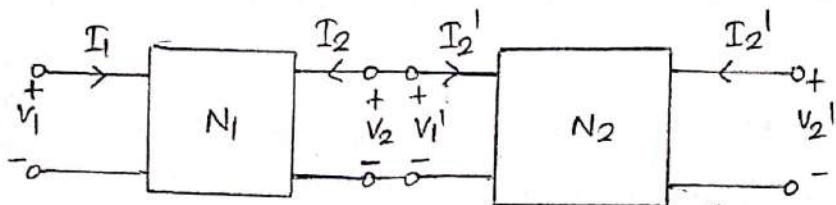

In the cascade connection, the o/p port of the first nLNs becomes the input port of 2nd nLNs.

Let  $A_1, B_1, C_1, D_1$  be the transmission parameters of nLNs  $N_1$  and  $A_2, B_2, C_2, D_2$  that of nLNs  $N_2$ .

For  $N_1$ ,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \quad \text{--- (1)}$$

For  $N_2$ ,

$$\begin{bmatrix} V_1' \\ I_1' \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ I_2' \end{bmatrix} \quad \text{--- (2)}$$

$$V_2 = V_1' \text{ and } -I_2 = I_1'$$

$$\begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} \quad \text{--- (3)}$$


From (1) and (3),

$$\begin{aligned} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} &= \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} \\ &= \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} \end{aligned}$$


$$\therefore \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

The resultant ABCD matrix of the cascaded connection is the product of individual ABCD matrices.

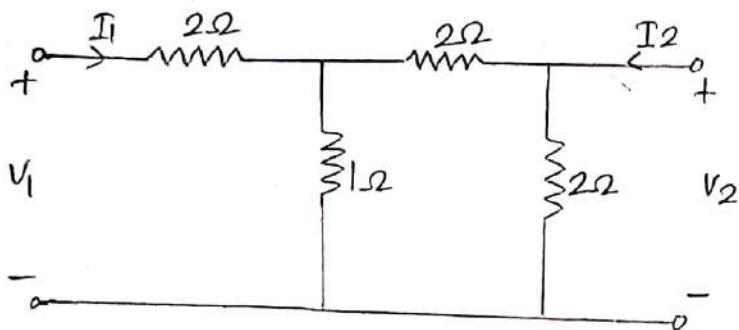- 1) Two identical sections of n/w shown below are connected in cascade. Obtain the transmission parameters of the overall n/w.



Redrawing the n/w

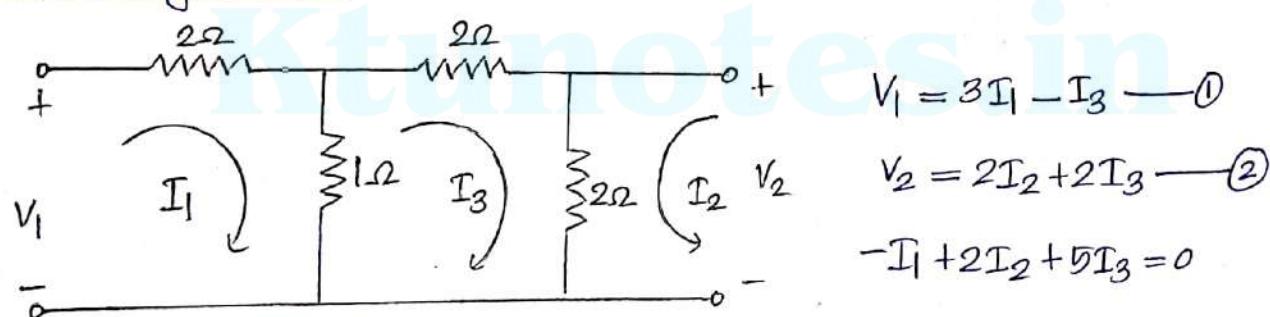

$$5I_3 = I_1 - 2I_2$$

$$I_3 = \frac{1}{5}I_1 - \frac{2}{5}I_2 \quad \text{--- (3)}$$

Subst. (3) in (1),

$$\begin{aligned}
 V_1 &= 3I_1 - I_3 \\
 &= 3I_1 - \left( \frac{1}{5}I_1 - \frac{2}{5}I_2 \right) \\
 &= \frac{14}{5}I_1 + \frac{2}{5}I_2 \quad \text{--- (4)}
 \end{aligned}$$

Subst. (3) in (2),

$$V_2 = 2I_2 + 2\left(\frac{1}{5}I_1 - \frac{2}{5}I_2\right)$$

$$= \frac{2}{5} I_1 + \frac{6}{5} I_2$$

$$\frac{2}{5} I_1 = V_2 - \frac{6}{5} I_2$$

$$I_1 = \frac{5}{2} V_2 - 3I_2 \quad \text{--- (5)}$$

Subst. (5) in (4),

$$V_1 = \frac{14}{5} \left( \frac{5}{2} V_2 - 3I_2 \right) + \frac{2}{5} I_2 = 7V_2 - 8I_2 \quad \text{--- (6)}$$


Comparing (6) and (5) with ABCD parameter eqns.

$$\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} = \begin{bmatrix} 7 & 8 \\ 2.5 & 3 \end{bmatrix}$$

Hence, transmission parameters of the overall cascaded n/w are,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 7 & 8 \\ 2.5 & 3 \end{bmatrix} \begin{bmatrix} 7 & 8 \\ 2.5 & 3 \end{bmatrix} = \begin{bmatrix} 69 & 80 \\ 25 & 29 \end{bmatrix}$$

### Parallel connection

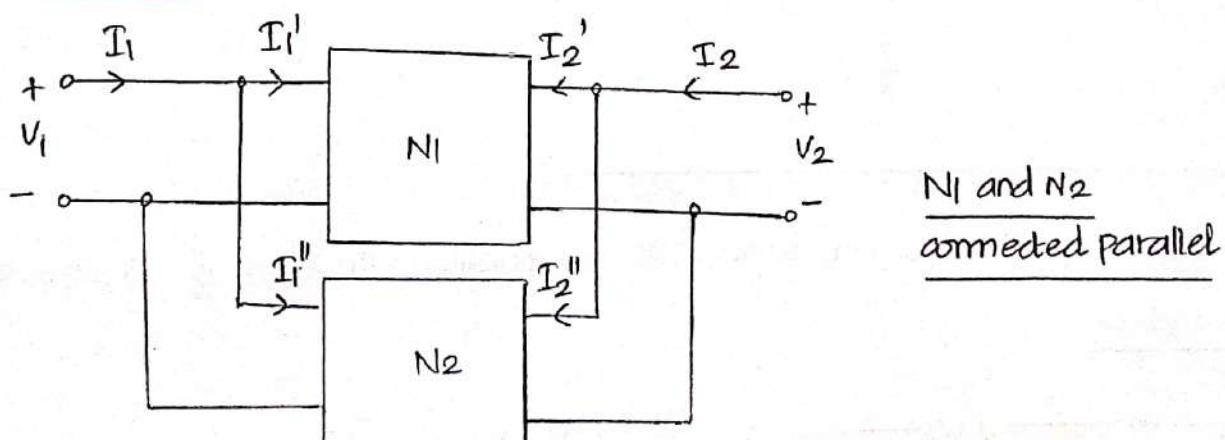

In parallel connection the two n/w's have the same input and output voltages.

Let  $Y_{11}', Y_{12}', Y_{21}', Y_{22}'$  be the Y-parameters of  $N_1$  and  $Y_{11}'', Y_{12}'', Y_{21}'', Y_{22}''$  be the Y-parameters of  $N_2$ .

For  $N_1$ ,

$$\begin{bmatrix} I_1' \\ I_2' \end{bmatrix} = \begin{bmatrix} Y_{11}' & Y_{12}' \\ Y_{21}' & Y_{22}' \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

For nlu N<sub>1</sub>,

$$\begin{bmatrix} I_1'' \\ I_2'' \end{bmatrix} = \begin{bmatrix} Y_{11}'' & Y_{12}'' \\ Y_{21}'' & Y_{22}'' \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

For the combined nlu,


$$I_1 = I_1' + I_1'' \text{ and } I_2 = I_2' + I_2''$$

$$\therefore \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_1' + I_1'' \\ I_2' + I_2'' \end{bmatrix} = \begin{bmatrix} Y_{11}' + Y_{11}'' & Y_{12}' + Y_{12}'' \\ Y_{21}' + Y_{21}'' & Y_{22}' + Y_{22}'' \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Thus the resultant Y-parameter matrix for parallel connected nlus is the sum of Y-matrices of each individual two port nlus.


### PROBLEMS

1. Determine Y-parameters of the nlu.

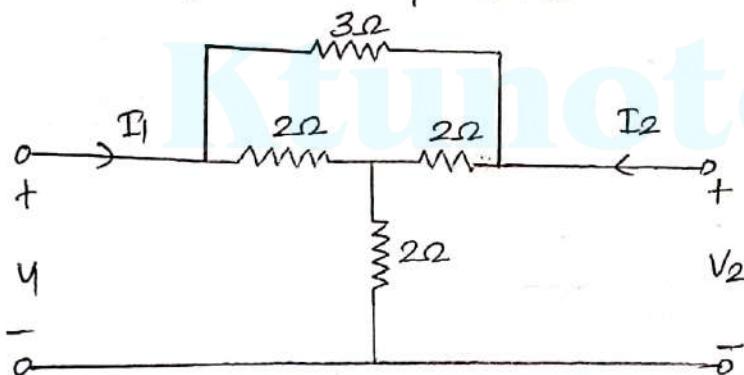

The above nlu can be considered as the parallel connection of two nlus N<sub>1</sub> and N<sub>2</sub>.

Network N<sub>1</sub>

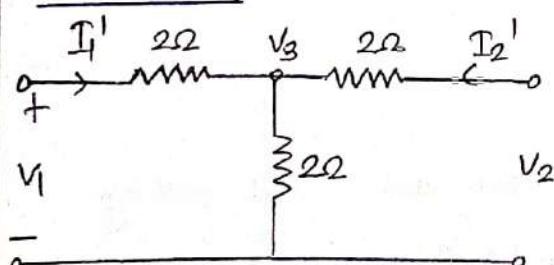

$$I_1' = \frac{V_1 - V_3}{2} \quad \text{--- (1)}$$

$$I_2' = \frac{V_2 - V_3}{2} \quad \text{--- (2)}$$

$$I_1' + I_2' = \frac{V_3}{2} \quad \text{--- (3)}$$

Subst. (1) and (2) in (3),

$$\frac{V_1 - V_3}{2} + \frac{V_2 - V_3}{2} = \frac{V_3}{2}$$

$$\frac{V_1 + V_2 - 2V_3}{2} = \frac{V_3}{2}$$

$$3V_3 = V_1 + V_2$$

$$V_3 = \frac{V_1}{3} + \frac{V_2}{3} \quad \text{--- (4)}$$

$$\textcircled{4} \text{ in } \textcircled{1}, I_1' = \frac{V_1}{2} - \frac{V_3}{2} = \frac{V_1}{2} - \frac{1}{2} \left( \frac{V_1}{3} + \frac{V_2}{3} \right).$$

$$= \frac{1}{3}V_1 - \frac{1}{6}V_2 \quad \text{--- (5)}$$

Subst (4) in (2),

$$\begin{aligned} I_2' &= \frac{V_2}{2} - \frac{1}{2} \left[ \frac{V_1}{3} + \frac{V_2}{3} \right] \\ &= -\frac{1}{6}V_1 + \frac{1}{3}V_2 \quad \text{--- (6)} \end{aligned}$$


Comparing (5) and (6) with y-parameter eqns

$$\begin{bmatrix} Y_{11}' & Y_{12}' \\ Y_{21}' & Y_{22}' \end{bmatrix} = \begin{bmatrix} \frac{1}{3} & -\frac{1}{6} \\ -\frac{1}{6} & \frac{1}{3} \end{bmatrix}$$

Network N2 is shown below

$$I_1'' = -I_2'' = \frac{V_1 - V_2}{3} = \frac{1}{3}V_1 - \frac{1}{3}V_2$$
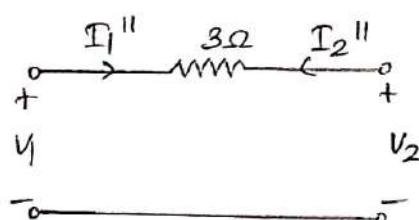
$$I_2'' = -\frac{1}{3}V_1 + \frac{1}{3}V_2$$




$$\begin{bmatrix} Y_{11}'' & Y_{12}'' \\ Y_{21}'' & Y_{22}'' \end{bmatrix} = \begin{bmatrix} \frac{1}{3} & -\frac{1}{3} \\ -\frac{1}{3} & \frac{1}{3} \end{bmatrix}$$

The overall Y-parameters of the nlu are,

$$\begin{aligned} \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} &= \begin{bmatrix} Y_{11}' + Y_{11}'' & Y_{12}' + Y_{12}'' \\ Y_{21}' + Y_{21}'' & Y_{22}' + Y_{22}'' \end{bmatrix} \\ &= \begin{bmatrix} \frac{1}{3} + \frac{1}{3} & -\frac{1}{6} - \frac{1}{3} \\ -\frac{1}{6} - \frac{1}{3} & \frac{1}{3} + \frac{1}{3} \end{bmatrix} = \begin{bmatrix} \frac{2}{3} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{2}{3} \end{bmatrix} \end{aligned}$$

28/12/2020

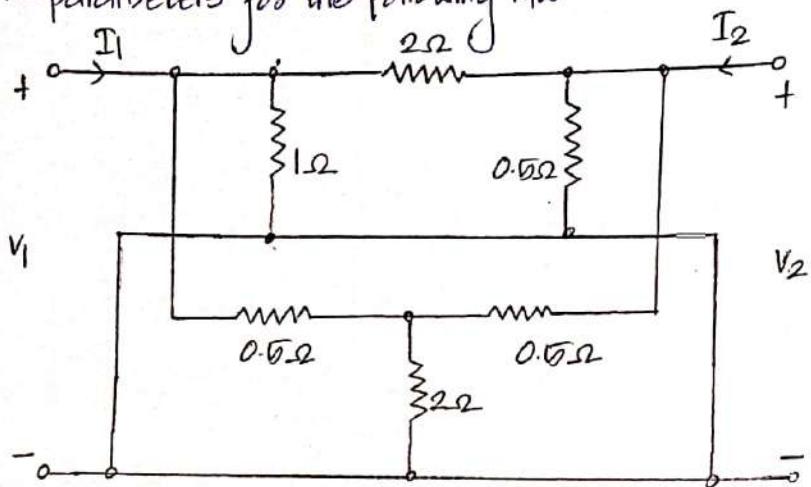
2. Find Y-parameters for the following n/w.



The above n/w can be considered as a parallel combination of two n/w's N<sub>1</sub> and N<sub>2</sub>.

Node -1
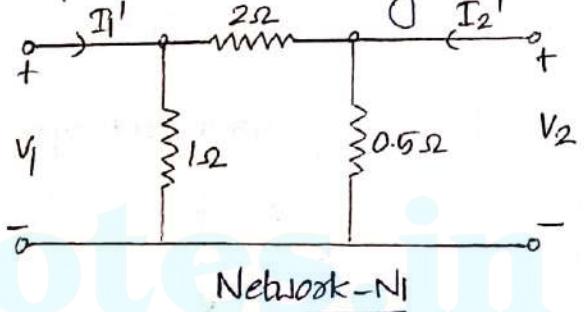
$$\begin{aligned} I_1' &= \frac{V_1}{1} + \frac{V_1 - V_2}{2} \\ &= \frac{3}{2}V_1 - \frac{1}{2}V_2 \quad \text{--- } ① \end{aligned}$$



Node -2


$$\begin{aligned} I_2' &= \frac{V_2}{0.5} + \frac{V_2 - V_1}{2} \\ &= -\frac{1}{2}V_1 + \frac{5}{2}V_2 \quad \text{--- } ② \end{aligned}$$

Comparing ① and ② with y-parameter eqns.

$$\begin{bmatrix} Y_{11}' & Y_{12}' \\ Y_{21}' & Y_{22}' \end{bmatrix} = \begin{bmatrix} 3/2 & -1/2 \\ -1/2 & 5/2 \end{bmatrix}$$

Network - N2
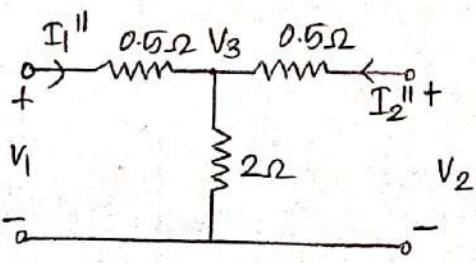
$$I_1'' = \frac{V_1 - V_3}{0.5} = 2V_1 - 2V_3 \quad \text{--- } ①$$



$$I_2'' = \frac{V_2 - V_3}{0.5} = 2V_2 - 2V_3 \quad \text{--- } ②$$

$$I_1'' + I_2'' = \frac{V_3}{2} \quad \text{--- (3)}$$

Subst (1) and (2) in (3),

$$2V_1 - 2V_3 + 2V_2 - 2V_3 = \frac{V_3}{2}$$

$$\frac{9}{2}V_3 = 2V_1 + 2V_2$$

$$V_3 = \frac{4}{9}V_1 + \frac{4}{9}V_2 \quad \text{--- (4)}$$

Subst. in (1),

$$I_1''' = 2V_1 - 2\left[\frac{4}{9}V_1 + \frac{4}{9}V_2\right]$$

$$= \frac{10}{9}V_1 - \frac{8}{9}V_2 \quad \text{--- (5)}$$

Substituting  $V_3$  in (2),

$$I_2' = 2V_2 - 2V_3$$

$$= 2V_2 - 2\left(\frac{4}{9}V_1 + \frac{4}{9}V_2\right) = -\frac{8}{9}V_1 + \frac{10}{9}V_2 \quad \text{--- (6)}$$

Comparing (5) and (6) with parameter eqns.

$$\begin{bmatrix} Y_{11}'' & Y_{12}'' \\ Y_{21}'' & Y_{22}'' \end{bmatrix} = \begin{bmatrix} \frac{10}{9} & -\frac{8}{9} \\ -\frac{8}{9} & \frac{10}{9} \end{bmatrix}$$


Hence the overall Y-parameters of the n/w are,

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Y_{11}' + Y_{11}'' & Y_{12}' + Y_{12}'' \\ Y_{21}' + Y_{21}'' & Y_{22}' + Y_{22}'' \end{bmatrix}$$

$$= \begin{bmatrix} \frac{3}{2} + \frac{10}{9} & \frac{-1}{2} - \frac{8}{9} \\ \frac{-1}{2} - \frac{8}{9} & \frac{5}{2} + \frac{10}{9} \end{bmatrix} = \begin{bmatrix} \frac{47}{18} & -\frac{25}{18} \\ -\frac{25}{18} & \frac{65}{18} \end{bmatrix}$$
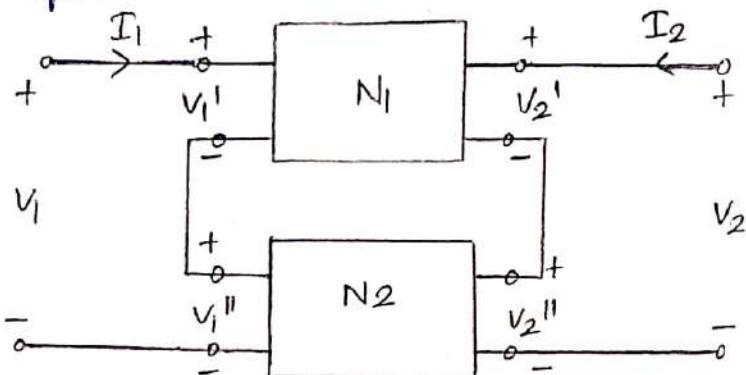
## SERIES CONNECTION OF NWS

In series connection, both nws carry the same input current. Their o/p currents are also equal.



Let  $\pi_{11}', \pi_{12}', \pi_{21}', \pi_{22}'$  be the  $\pi$ -parameters of  $N_1$  and  $\pi_{11}'', \pi_{12}'', \pi_{21}'', \pi_{22}''$  be that of  $N_2$ .

$$\text{For } N_1, \begin{bmatrix} V_1' \\ V_2' \end{bmatrix} = \begin{bmatrix} \pi_{11}' & \pi_{12}' \\ \pi_{21}' & \pi_{22}' \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

For  $N_2$ ,

$$\begin{bmatrix} V_1'' \\ V_2'' \end{bmatrix} = \begin{bmatrix} \pi_{11}'' & \pi_{12}'' \\ \pi_{21}'' & \pi_{22}'' \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

For the combined n/w,


$$V_1 = V_1' + V_1'' \text{ and } V_2 = V_2' + V_2''$$

$$\begin{aligned} \text{Hence, } \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} &= \begin{bmatrix} V_1' + V_1'' \\ V_2' + V_2'' \end{bmatrix} = \begin{bmatrix} \pi_{11}' + \pi_{11}'' & \pi_{12}' + \pi_{12}'' \\ \pi_{21}' + \pi_{21}'' & \pi_{22}' + \pi_{22}'' \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \\ &= \begin{bmatrix} \pi_{11} & \pi_{12} \\ \pi_{21} & \pi_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \end{aligned}$$

where the resultant  $\pi$ -parameter matrix for the series-connected nws is the sum of  $\pi$ -matrices of each individual two-port nws.

## PROBLEMS

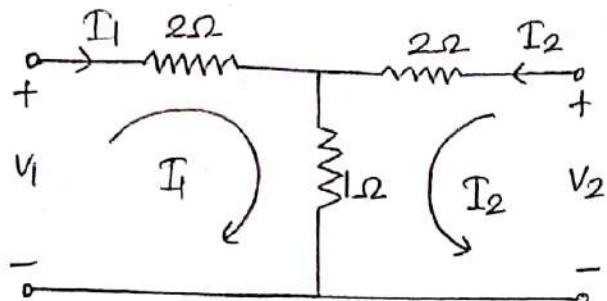1. Two identical sections of the n/w shown below are connected in series. Obtain z-parameters of the overall n/w.



Applying KVL,

$$V_1 = 3I_1 + I_2 \quad \text{--- (1)}$$

$$V_2 = 3I_2 + I_1$$

$$= I_1 + 3I_2 \quad \text{--- (2)}$$


Comparing (1) and (2) with z-parameter eqns.

$$\begin{bmatrix} Z_{11}' & Z_{12}' \\ Z_{21}' & Z_{22}' \end{bmatrix} = \begin{bmatrix} 3 & 1 \\ 1 & 3 \end{bmatrix}$$

z-parameters of the overall n/w are:

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 3 & 1 \\ 1 & 3 \end{bmatrix} + \begin{bmatrix} 3 & 1 \\ 1 & 3 \end{bmatrix} = \begin{bmatrix} 6 & 2 \\ 2 & 6 \end{bmatrix}$$

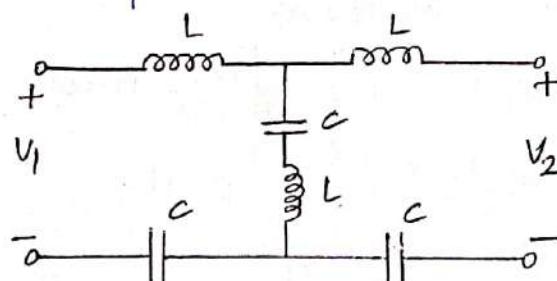2. Determine z-parameters for the n/w shown below.




The n/w can be considered as the series connection of two n/w's N<sub>1</sub> and N<sub>2</sub>.

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Network - N<sub>1</sub> (transformed)

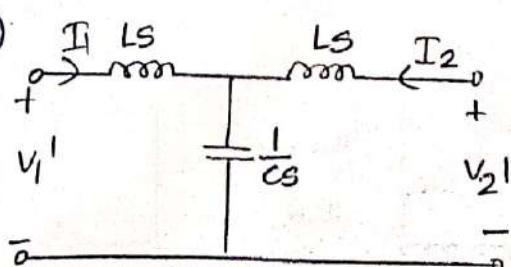


$$V_1' = \left( LS + \frac{1}{CS} \right) I_1 + \left( \frac{1}{CS} \right) I_2 \quad \text{--- (1)}$$

$$V_2' = \left( \frac{1}{CS} \right) I_1 + \left( LS + \frac{1}{CS} \right) I_2 \quad \text{--- (2)}$$

Comparing (1) and (2) with  $\pi$ -parameter eqns,

$$\begin{bmatrix} Z_{11}' & Z_{12}' \\ Z_{21}' & Z_{22}' \end{bmatrix} = \begin{bmatrix} LS + \frac{1}{CS} & \frac{1}{CS} \\ \frac{1}{CS} & LS + \frac{1}{CS} \end{bmatrix}$$

Network-N2 (transformed)

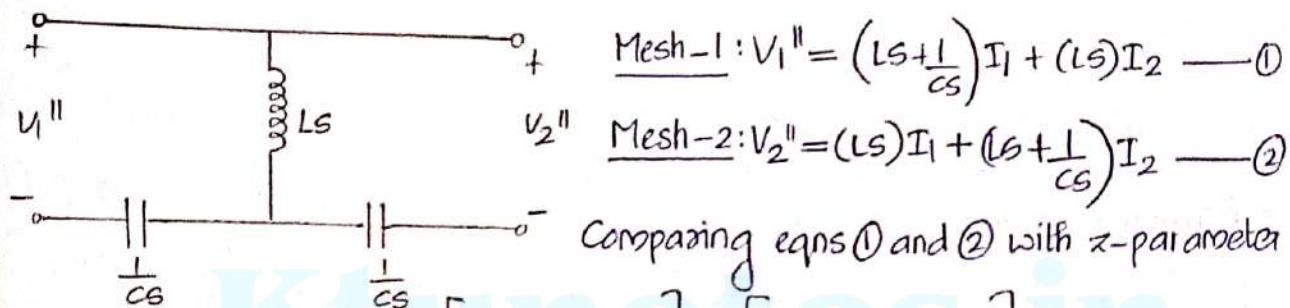

Comparing eqns (1) and (2) with  $\pi$ -parameter eqns.


$$\begin{bmatrix} Z_{11}'' & Z_{12}'' \\ Z_{21}'' & Z_{22}'' \end{bmatrix} = \begin{bmatrix} LS + \frac{1}{CS} & LS \\ LS & LS + \frac{1}{CS} \end{bmatrix}$$

The overall  $\pi$ -parameters of the n/w are,

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{11}' + Z_{11}'' & Z_{12}' + Z_{12}'' \\ Z_{21}' + Z_{21}'' & Z_{22}' + Z_{22}'' \end{bmatrix} = \begin{bmatrix} LS + \frac{1}{CS} + LS + \frac{1}{CS} & \frac{1}{CS} + LS \\ \frac{1}{CS} + LS & LS + \frac{1}{CS} + LS + \frac{1}{CS} \end{bmatrix}$$

$$= \begin{bmatrix} 2LS + \frac{2}{CS} & LS + \frac{1}{CS} \\ LS + \frac{1}{CS} & 2LS + \frac{2}{CS} \end{bmatrix} = \left( LS + \frac{1}{CS} \right) \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}$$

29/12/20 TERMINATED TWO PORT n/w

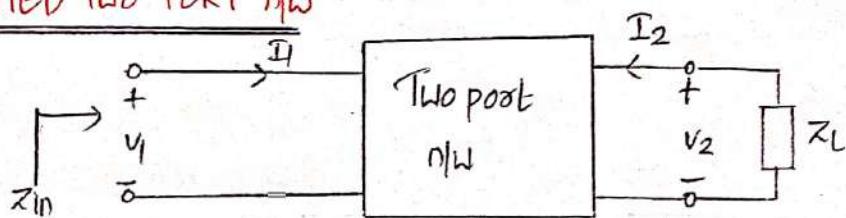


$$V_2 = -Z_L I_2$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{Z_{11}Z_{22} + Z_{11}Z_L - Z_{12}Z_{21}}{Z_{22} + Z_L}$$

With op post open circuited,  $Z_L = \infty$ .  $Z_{in} = Z_{11}$
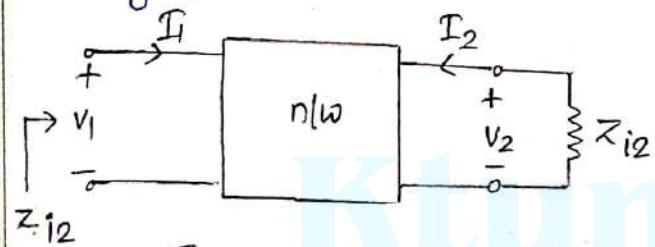
### Image impedances

If the driving point impedance at port 1, with impedance  $Z_{i2}$  connected across port 2 is  $Z_{ii}$  and driving point impedance at port 2, with impedance  $Z_{ii}$  connected across port 1 is  $Z_{i2}$ , then  $Z_{ii}$  and  $Z_{i2}$  are known as image impedances of the n/w or image parameters.




$$Z_{ii} = \frac{AZ_{i2} + B}{CZ_{i2} + D} \quad \text{--- (1)}$$

Two port n/w terminated

at port -2
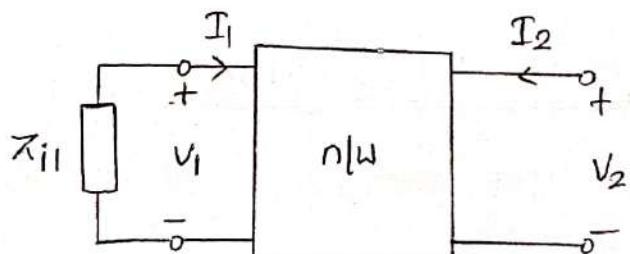
$$Z_{i2} = \frac{DZ_{ii} + B}{CZ_{ii} + A} \quad \text{--- (2)}$$




Two port n/w terminated at port -1

Solving (1) and (2),

$$Z_{ii} = \sqrt{\frac{AB}{CD}}, Z_{i2} = \sqrt{\frac{BD}{AC}}$$

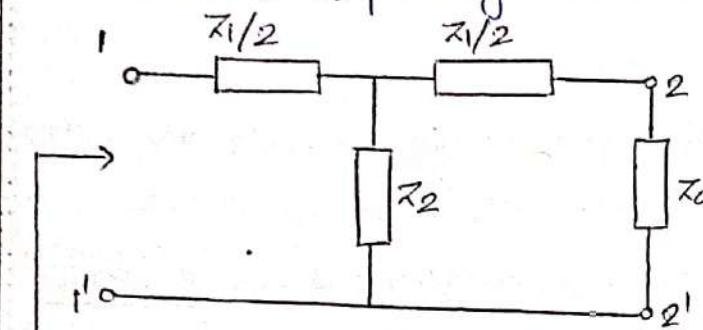
## CHARACTERISTIC IMPEDANCE

For a symmetrical N/W, the image impedances  $Z_{11}$  and  $Z_{12}$  are equal and the image impedance is then called the characteristic or the iterative impedance  $Z_0$ . Thus, if a symmetrical T-N/W is terminated in  $Z_0$ , its input impedance will also be  $Z_0$ .  $Z_0$  for a symmetrical N/W can be found as follows.



$Z_{11}$

T-N/W

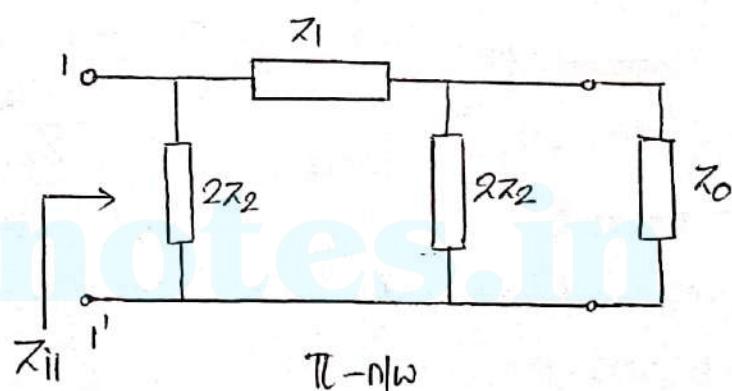


$Z_{11}$

Pi-N/W
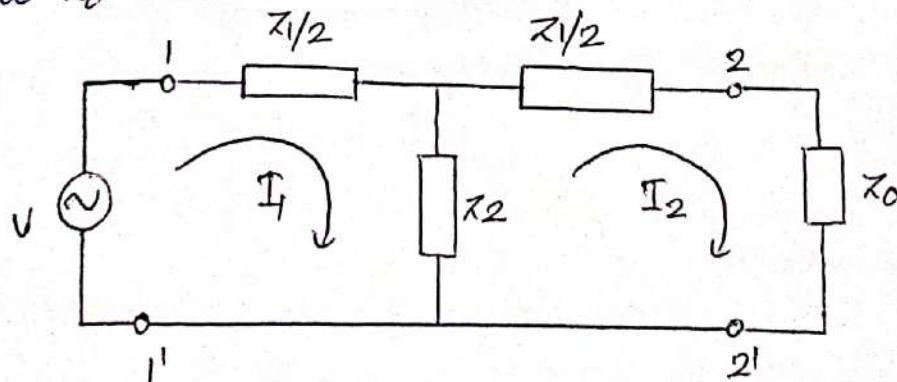
## ATTENUATION AND PHASE CONSTANTS

Consider the T-N/W terminated with a load equal to its characteristic impedance  $Z_0$ .



$\frac{I_1}{I_2} = e^{\sigma}$  where  $\sigma$  is called propagation constant and is a complex number.

$$\gamma = \alpha + j\beta$$

$\alpha$  is known as the attenuation constant, since it determines the magnitude ratio between input and output quantities or the attenuation produced in passing through this n/w. Unit is nepers.

The parameter  $\beta$  is known as the phase constant, since it determines the phase angle between input and output quantities or the shift in phase introduced by the n/w. Its unit is radians.

Ktunotes.in