




KTU **NOTES**


The learning companion.

**KTU STUDY MATERIALS | SYLLABUS | LIVE
NOTIFICATIONS | SOLVED QUESTION PAPERS**

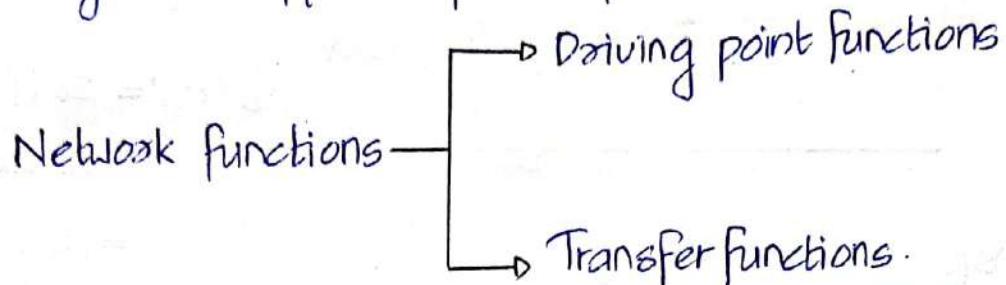A network function gives the relation between currents or voltages at different parts of the network.



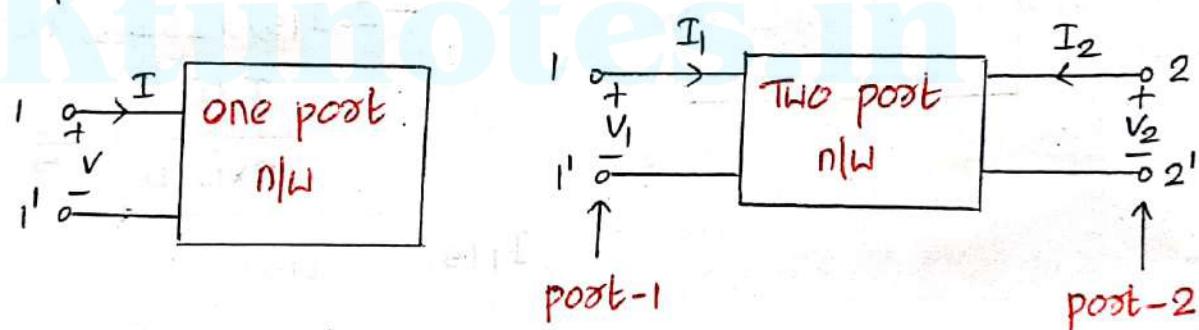- A network may be schematically represented by a rectangular box. Terminals are used to connect any n/w to any other n/w or for taking measurements. Two such terminals are called a post. Network with one pair of terminals or single post is called a one-port n/w. If there are two posts, it is called a two-port n/w.



- The port to which energy source (i/p) is connected is called input port and the port to which load is connected is called the o/p port.
- V_1 and I_1 are the voltage and current assigned to input port and V_2 and I_2 assigned to o/p port. I_1 and I_2 are entering into the n/w at upper terminals 1 and 2 respectively.

DRIVING POINT FUNCTIONS

If excitation and response are measured at the same port, the n/w function is known as the driving point function.

→ Since for a one port n/w, only a single voltage and current are specified, only one n/w function (and its reciprocal) can be defined.

1. Driving-point impedance function ($Z(s)$)

It is the ratio of voltage transform at one port to the current transform at the same port.

$$Z(s) = \frac{V(s)}{I(s)}$$

2. Driving point admittance function - $Y(s)$

Ratio of $I(s)$ to $V(s)$ at the same port.

$$Y(s) = \frac{I(s)}{V(s)}$$

For a two port n/w, the driving point impedance function and driving point admittance function at port-1 are

$$Z_{11}(s) = \frac{V_1(s)}{I_1(s)}, \quad Y_{11}(s) = \frac{I_1(s)}{V_1(s)}$$

Similarly, at port 2

$$Z_{22}(s) = \frac{V_2(s)}{I_2(s)}, \quad Y_{22}(s) = \frac{I_2(s)}{V_2(s)}$$

TRANSFER FUNCTIONS

The transfer function is used to describe networks which have atleast two ports. It relates a voltage or current at one port to the voltage or current at another port. These functions are also defined as the ratio of response transforms to an excitation transforms. Thus, there are four possible forms of transfer functions.

1. Voltage transfer function

It is the ratio of voltage transform at one port to the voltage transform at another port. Denoted by $G(s)$.

$$G_{12}(s) = \frac{V_1(s)}{V_2(s)} ; G_{21}(s) = \frac{V_2(s)}{V_1(s)}$$

2. Current transfer function - $\alpha(s)$

Ratio of current transform at one port to the current transform at another port.

$$\alpha_{12}(s) = \frac{I_1(s)}{I_2(s)} ; \alpha_{21}(s) = \frac{I_2(s)}{I_1(s)}$$

3. Transfer Impedance function - $Z(s)$

Ratio of voltage transform at one port to the current transform at another port.

$$Z_{12}(s) = \frac{V_1(s)}{I_2(s)} ; Z_{21}(s) = \frac{V_2(s)}{I_1(s)}$$


4. Transfer admittance function - $Y(s)$

Ratio of the current transform at one port to the voltage transform at another port.

$$Y_{12}(s) = \frac{I_1(s)}{V_2(s)} ; Y_{21}(s) = \frac{I_2(s)}{V_1(s)}$$


PROBLEMS

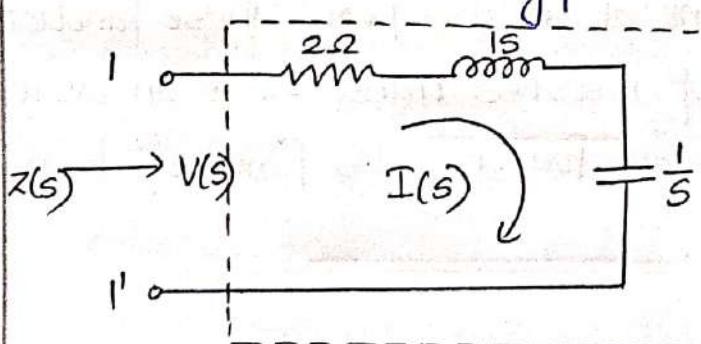1. For the n/w, obtain driving point impedance.



$$Z(s) = \frac{V(s)}{I(s)} = 2 + s + \frac{1}{s} = \frac{2s + s^2 + 1}{s} = \underline{\underline{\frac{(s+1)^2}{s}}}$$

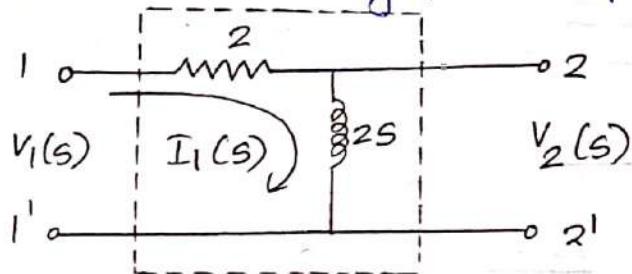2. For the n/w shown below obtain the transfer functions $G_{21}(s)$, $Z_{21}(s)$ and the driving point impedance $Z_{11}(s)$.




$$G_{21}(s) = \frac{V_2(s)}{V_1(s)} = \frac{2s}{2+2s} = \underline{\underline{\frac{s}{s+1}}}$$

$$Z_{21}(s) = \frac{V_2(s)}{I_1(s)} = \underline{\underline{2s}}$$

$$Z_{11}(s) = \frac{V_1(s)}{I_1(s)} = 2+2s = \underline{\underline{2(s+1)}}$$

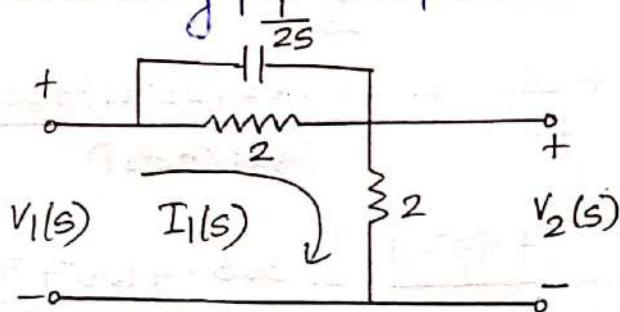3. For the n/w shown below , obtain the transfer functions $G_{21}(s)$, $Z_{21}(s)$ and driving point impedance $Z_{11}(s)$.



Parallel combination of $\frac{1}{2s}$ and 2 , $\frac{2 \times \frac{1}{2s}}{2 + \frac{1}{2s}} = \underline{\underline{\frac{2}{4s+1}}}$

$$V_1(s) = I_1(s) \left[\frac{2}{4s+1} + 2 \right] = I_1(s) \left[\frac{2+8s+2}{4s+1} \right] = I_1(s) \left[\frac{8s+4}{4s+1} \right]$$

$$V_2(s) = 2I_1(s)$$

Transfer functions


$$G_{21}(s) = \frac{V_2(s)}{V_1(s)} = \frac{2I_1(s)}{I_1(s) \left[\frac{8s+4}{4s+1} \right]} = \frac{4s+1}{4s+2}$$

$$Z_{21}(s) = \frac{V_2(s)}{I_1(s)} = 2$$

Driving point functions

$$Z_{11}(s) = \frac{V_1(s)}{I_1(s)} = \frac{8s+4}{4s+1}$$

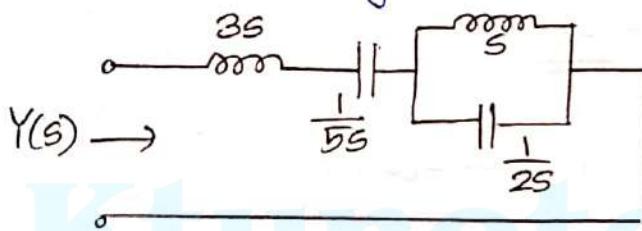4. ReFind the driving point admittance of the following n/w.



$$\begin{aligned} Z(s) &= 3s + \frac{1}{5s} + \frac{s \times \frac{1}{2s}}{s + \frac{1}{2s}} \\ &= 3s + \frac{1}{5s} + \frac{s}{2s^2 + 1} = \frac{3s + 5s(2s^2 + 1) + 2s^2 + 1 + 5s^2}{5s(2s^2 + 1)} \end{aligned}$$






$$= \frac{10s^2(2s^2 + 1) + 7s^2 + 1}{5s(2s^2 + 1)} = \frac{30s^4 + 10s^2 + 7s^2 + 1}{5s(2s^2 + 1)}$$

$$= \frac{30s^4 + 22s^2 + 1}{5s(2s^2 + 1)}$$

$$Y(s) = \frac{1}{Z(s)} = \frac{5s(2s^2 + 1)}{30s^4 + 22s^2 + 1}$$

11/11/2020

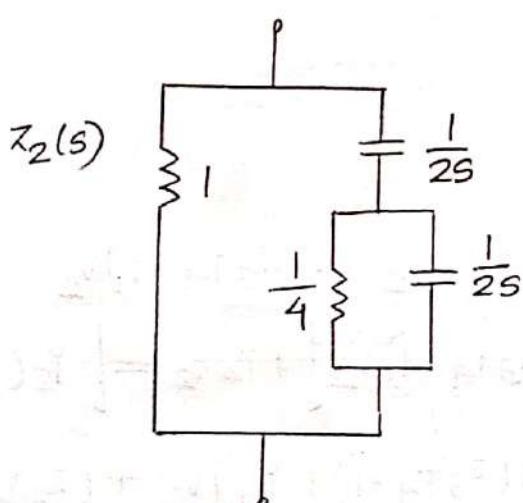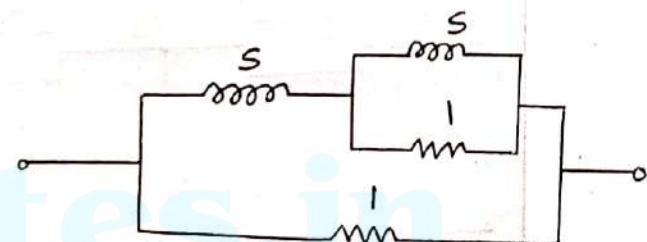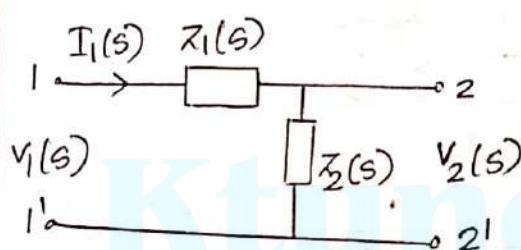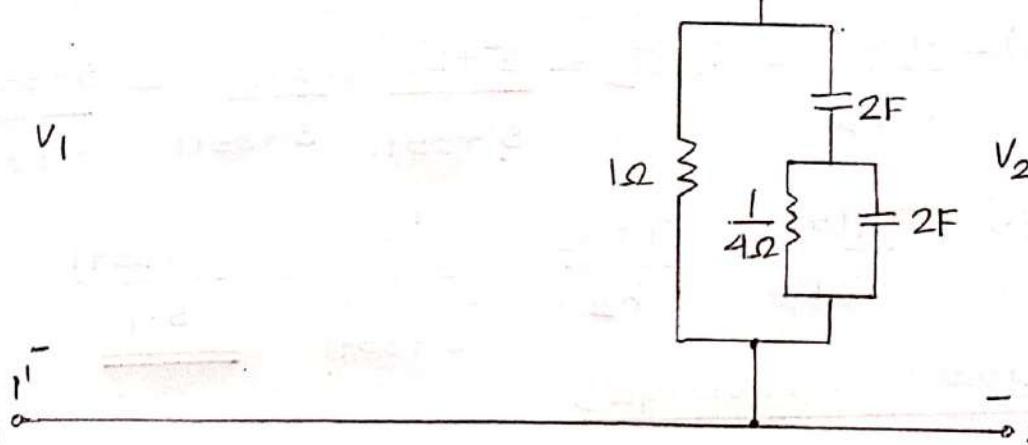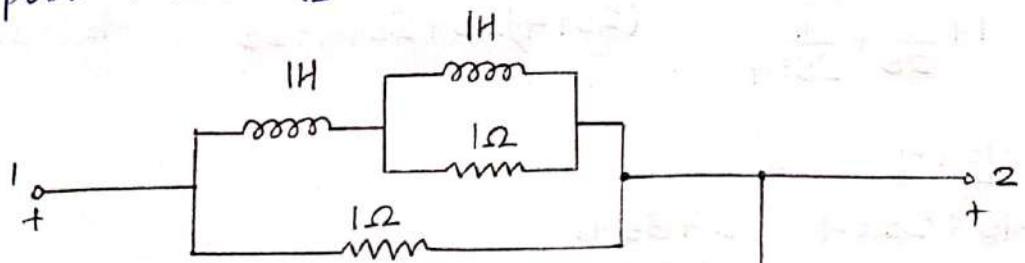1. For the following nw find the driving point impedance at port-1 and Z_{12} .



$$\begin{aligned}
 Z_1(s) &= \frac{I_1(s) \left(s + \frac{s}{s+1} \right)}{1+s + \frac{s}{s+1}} \\
 &= \frac{s^2 + s + s}{(s+1)^2 + s} - \frac{s^2 + 2s}{s^2 + 2s + 1 + s} \\
 &= \frac{s^2 + 2s}{s^2 + 3s + 1}
 \end{aligned}$$

$$\begin{aligned}
 Z_2(s) &= \frac{1 \times \left(\frac{1}{2s} + \frac{1}{4} \times \frac{1}{2s} \right)}{\frac{1}{4} + \frac{1}{2s}} = \frac{\frac{1}{2s} + \frac{1}{8s}}{\frac{1}{4} + \frac{1}{2s}} \\
 &= \frac{1}{2s} + \frac{\frac{1}{8s}}{\frac{2s+4}{8s}}
 \end{aligned}$$


$$= \frac{\frac{1}{2s} + \frac{1}{2s+4}}{1 + \frac{1}{2s} + \frac{1}{2s+4}} = \frac{2s+4+2s}{(2s+4)2s+2s+4+2s} = \frac{4s+4}{4s^2+8s+4s+4}$$

$$= \frac{4s+4}{4s^2+12s+4} = \frac{s+1}{\underline{s^2+3s+1}}$$

$$Z_{11}(s) = \frac{V_1(s)}{I_1(s)} = Z_1 + Z_2 = \frac{s^2+2s}{s^2+3s+1} + \frac{s+1}{s^2+3s+1} = \frac{s^2+3s+1}{s^2+3s+1} = \underline{\underline{1}}$$

$$G_{12}(s) = \frac{V_1(s)}{V_2(s)} = \frac{Z_1 + Z_2}{Z_2} = \frac{1}{\frac{s+1}{s^2+3s+1}} = \frac{s^2+3s+1}{s+1} = \underline{\underline{1}}$$

ANALYSIS OF LADDER NETWORKS

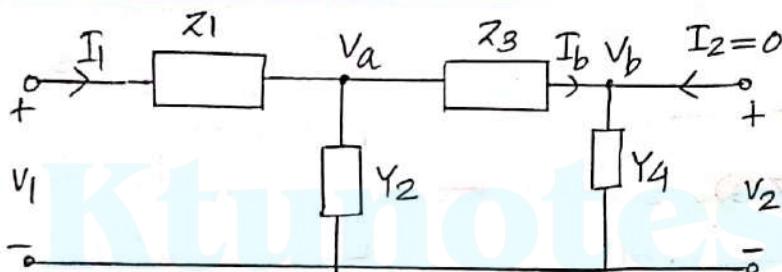

Ladder n/w

$$V_b = V_2$$


$$I_b = Y_4 V_2$$

$$V_a = Z_3 I_b + V_2 = Z_3 Y_4 V_2 + V_2 = (Z_3 Y_4 + 1)V_2$$


$$I_1 = Y_2 V_a + I_b = [Y_2 (Z_3 Y_4 + 1)V_2] + Y_4 V_2 = [Y_2 (Z_3 Y_4 + 1) + Y_4]V_2$$

$$\begin{aligned} V_1 &= Z_1 I_1 + V_a = Z_1 \{Y_2 (Z_3 Y_4 + 1) + Y_4\} V_2 + (Z_3 Y_4 + 1)V_2 \\ &= [Z_1 \{Y_2 (Z_3 Y_4 + 1) + Y_4\} + (Z_3 Y_4 + 1)] V_2 \end{aligned}$$

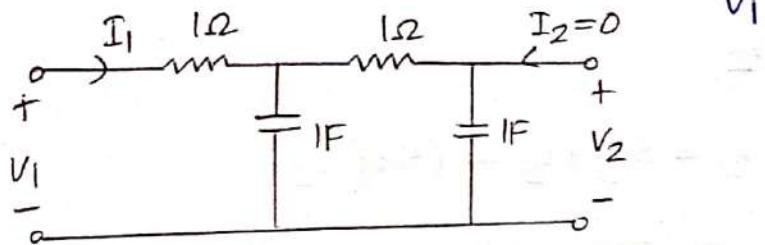1. For the n/w determine transfer function $\frac{V_2}{V_1}$



Transformed n/w

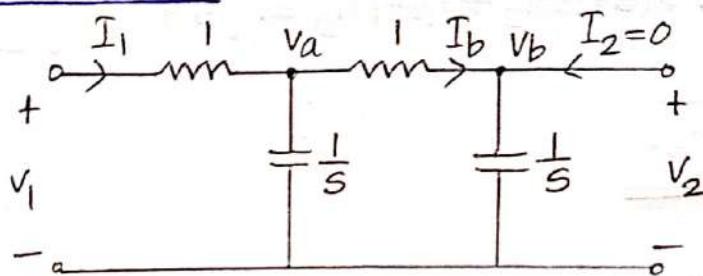

$$V_b = V_2$$

$$I_b = \frac{V_2}{\frac{1}{s}} = sV_2$$


$$V_a = I_b + V_2 = sV_2 + V_2 = (s+1)V_2$$

$$\begin{aligned} I_1 &= \frac{V_a}{\frac{1}{s}} + I_b = sV_a + I_b = s(s+1)V_2 + sV_2 \\ &= [s^2 + s + 1]V_2 = [s^2 + 2s]V_2 \end{aligned}$$

$$V_1 = I_1 + V_a = [s^2 + 2s]V_2 + (s+1)V_2 = (s^2 + 3s + 1)V_2$$

$$\underline{\underline{\frac{V_2}{V_1} = \frac{1}{s^2 + 3s + 1}}}$$

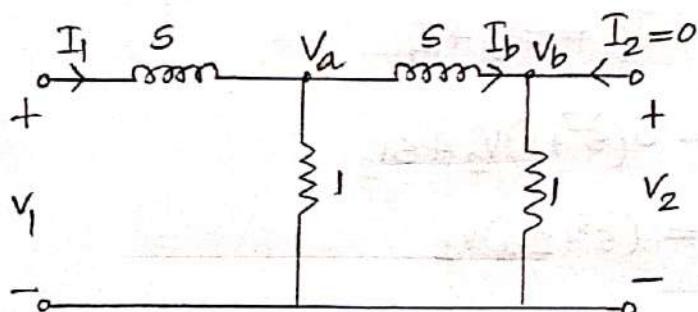2. For the n/w shown below determine the transfer function $\frac{V_2}{V_1}$



$$V_b = V_2$$

$$I_b = \frac{V_2}{1} = V_2$$


$$V_a = 6I_b + V_2 = 6V_2 + V_2 = (s+1)V_2$$

$$I_1 = \frac{V_a}{1} + I_b = (s+1)V_2 + V_2 = (s+2)V_2$$


$$V_1 = sI_1 + V_a = s(s+2)V_2 + (s+1)V_2 = [s^2 + 3s + 1]V_2$$

$$\underline{\underline{\frac{V_2}{V_1} = \frac{1}{s^2 + 3s + 1}}}$$

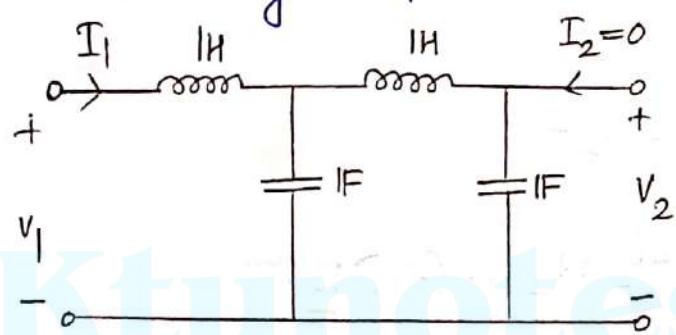3. For the following n/w find the network functions $\frac{V_1}{I_1}$, $\frac{V_2}{V_1}$ and $\frac{V_2}{I_1}$



Transformed n/w

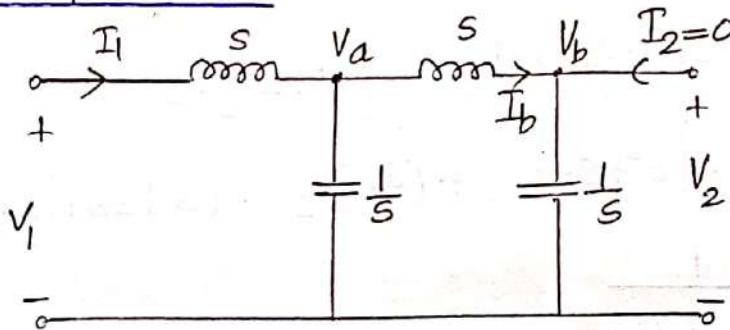

$$V_b = V_2$$

$$I_b = \frac{V_2}{s} = sV_2$$

$$V_a = sI_b + V_2$$

$$= s(sV_2) + V_2 \\ = (s^2 + 1)V_2$$

$$I_1 = \frac{V_a}{s} + I_b = sV_a + I_b$$

$$= s(s^2 + 1)V_2 + sV_2$$

$$= (s^3 + 2s)V_2$$

$$V_1 = sI_1 + V_a = s(s^3 + 2s)V_2 + (s^2 + 1)V_2$$

$$= (s^4 + 2s^2 + s^2 + 1) V_2$$


$$= (s^4 + 3s^2 + 1) V_2$$

$$\frac{V_1}{I_1} = \frac{s^4 + 3s^2 + 1}{s^3 + 2s}$$


$$\frac{V_2}{V_1} = \frac{1}{s^4 + 3s^2 + 1}$$

$$\frac{V_2}{I_1} = \frac{1}{s^3 + 2s}$$

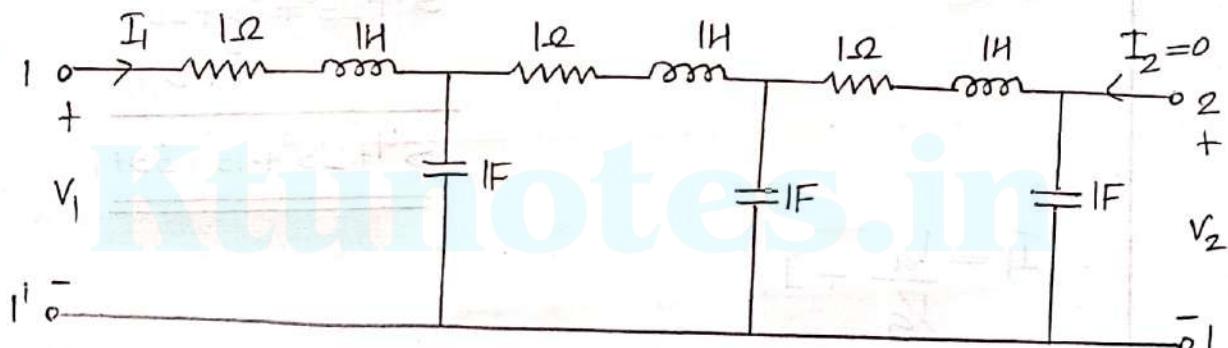4. For the following ladder n/w find the driving point impedance at the 1-1' terminal with 2-2' open.



Transformed n/w

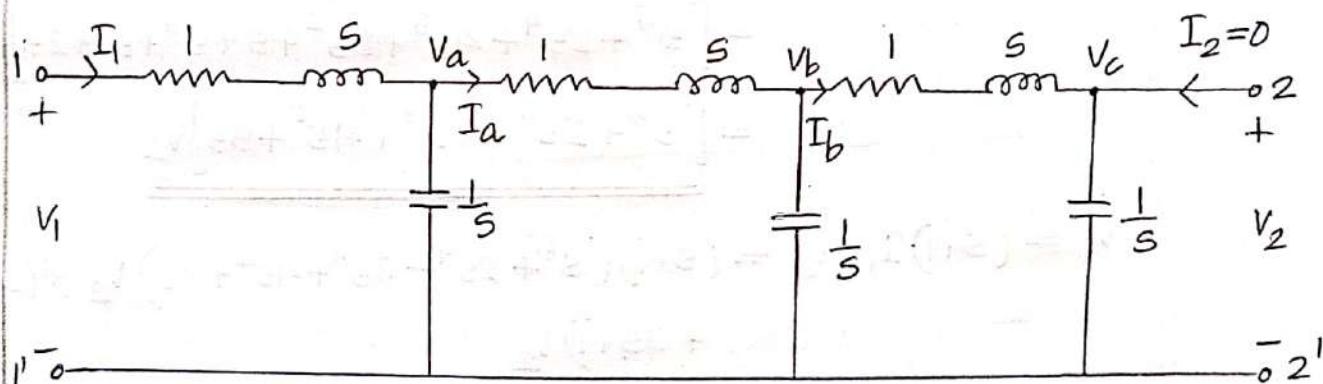

$$V_C = V_2$$

$$I_b = \frac{V_2}{\frac{1}{s}} = sV_2$$

$$V_b = (s+1)I_b + V_2 = (s+1)sV_2 + V_2 = (s^2 + s + 1)V_2$$

$$\begin{aligned}
 I_a &= \frac{V_b}{Y_s} + I_b = sV_b + I_b = s(s^2 + s + 1)V_2 + sV_2 \\
 &= [s^3 + s^2 + s + s]V_2 \\
 &= (s^3 + s^2 + 2s)V_2
 \end{aligned}$$

$$\begin{aligned}
 V_a &= (s+1)I_a + V_b \\
 &= (s+1)(s^3 + s^2 + 2s)V_2 + (s^2 + s + 1)V_2 \\
 &= (s^4 + 2s^3 + 4s^2 + 3s + 1)V_2
 \end{aligned}$$

$$\begin{array}{r}
 s^3 + s^2 + 2s \\
 \hline
 s+1 \\
 \hline
 s^3 + s^2 + 2s \\
 \hline
 s^4 + s^3 + 2s^2 \\
 \hline
 s^4 + 2s^3 + 3s^2 + 2s + \\
 \hline
 s^2 + s + 1 \\
 \hline
 s^4 + 2s^3 + 4s^2 + 3s + 1
 \end{array}$$


$$\begin{aligned}
 I_1 &= \frac{V_a}{Y_s} + I_a \\
 &= sV_a + I_a = s(s^4 + 2s^3 + 4s^2 + 3s + 1)V_2 + (s^3 + s^2 + 2s)V_2 \\
 &= [s^5 + 2s^4 + 4s^3 + 3s^2 + s + s^3 + s^2 + 2s]V_2 \\
 &= [s^5 + 2s^4 + 5s^3 + 4s^2 + 3s]V_2
 \end{aligned}$$

$$\begin{aligned}
 V_1 &= (s+1)I_1 + V_a = (s+1)(s^5 + 2s^4 + 5s^3 + 4s^2 + 3s)V_2 + (s^4 + 2s^3 + 4s^2 + \\
 &\quad + 3s + 1)V_2 \\
 &= (s^6 + 3s^5 + 8s^4 + 11s^3 + 6s^2 + 7s + 1)V_2
 \end{aligned}$$


$$\begin{array}{r}
 s^5 + 2s^4 + 5s^3 + 4s^2 + 3s \times \\
 \hline
 s+1 \\
 \hline
 s^5 + 2s^4 + 5s^3 + 4s^2 + 3s \\
 \hline
 s^6 + 2s^5 + 5s^4 + 4s^3 + 3s^2 \\
 \hline
 s^6 + 3s^5 + 7s^4 + 9s^3 + 7s^2 + 3s + \\
 \hline
 s^4 + 2s^3 + 4s^2 + 3s + 1 \\
 \hline
 s^6 + 3s^5 + 8s^4 + 11s^3 + 11s^2 + 6s + 1 \\
 \hline
 \end{array}$$

$$Z_{II} = \frac{V_1}{I_1} = \frac{s^6 + 3s^5 + 8s^4 + 11s^3 + 11s^2 + 6s + 1}{s^5 + 2s^4 + 5s^3 + 4s^2 + 3s}$$

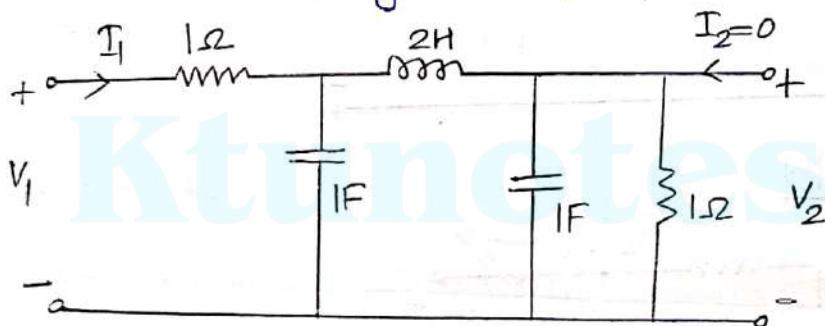5. Determine the voltage transfer function $\frac{V_2}{V_1}$ for the NW shown below.



Transformed NW

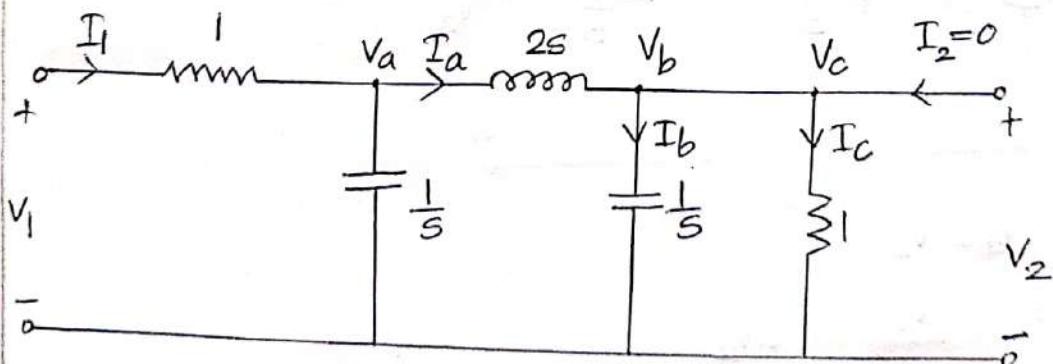

$$V_c = V_b = V_2$$

$$I_a = I_b + I_c = \frac{V_2}{\frac{1}{s}} + \frac{V_2}{1} = sV_2 + V_2 = (s+1)V_2$$


$$V_a = 2sI_a + V_2 = 2s(s+1)V_2 + V_2 = (2s^2 + 2s + 1)V_2$$

$$I_1 = \frac{V_a}{\gamma s} + I_a = sV_a + I_a = s(2s^2 + 2s + 1)V_2 + (s+1)V_2 \\ = (2s^3 + 2s^2 + s + s + 1) = (2s^3 + 2s^2 + 2s + 1)V_2$$


$$V_1 = I_1 \cdot I_1 + V_a = (2s^3 + 2s^2 + 2s + 1)V_2 + (2s^2 + 2s + 1)V_2 \\ = (2s^3 + 4s^2 + 4s + 2)V_2$$

Hence $\frac{V_2}{V_1} = \frac{1}{2s^3 + 4s^2 + 4s + 2}$

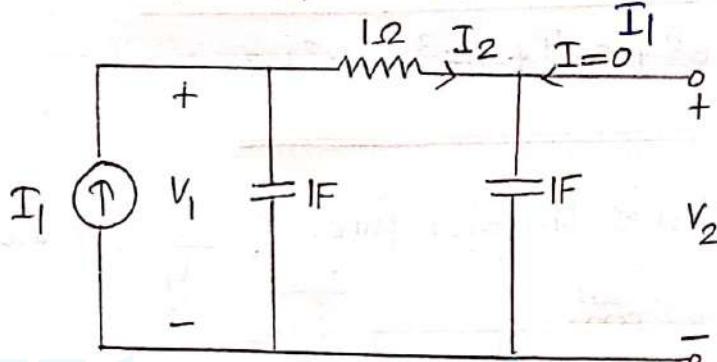6. For the n/w, compute $\alpha_{21}(s) = \frac{I_2}{I_1}$ and $\chi_{21}(s) = \frac{V_2}{I_1}$



Transformed n/w

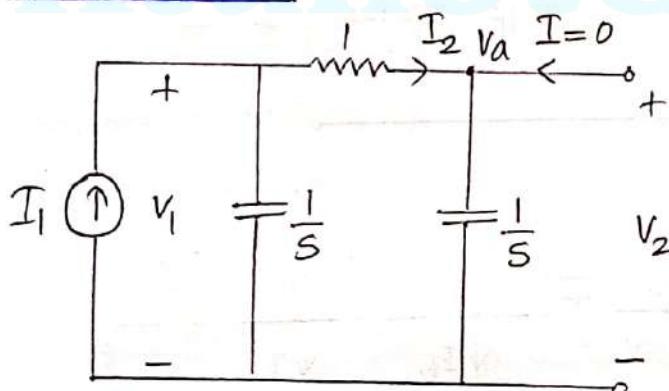

$$V_a = V_2$$

$$I_2 = \frac{V_2}{\gamma s} = sV_2$$



$$V_1 = I_1 \cdot I_2 + V_a = sV_2 + V_2 = (s+1)V_2$$

$$I_1 = \frac{V_1}{\gamma s} + I_2 = sV_1 + I_2 = s(s+1)V_2 + sV_2 = (s^2 + 2s)V_2$$

$$\alpha_{21}(s) = \frac{I_2}{I_1} = \frac{sV_2}{(s^2 + 2s)V_2} = \frac{1}{s+2}$$

$$Z_{21}(s) = \frac{V_2}{I_1} = \frac{1}{s^2 + 2s}$$

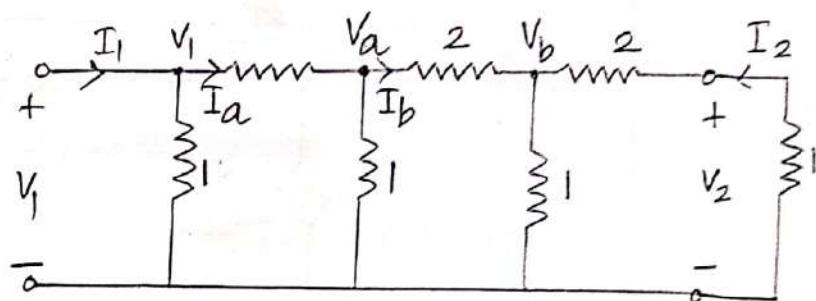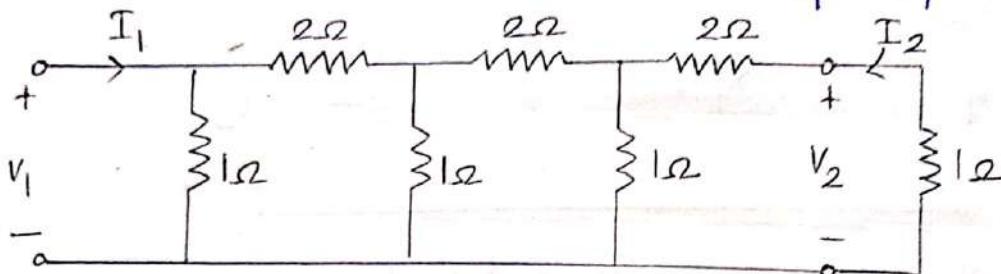12/11/2020 7. For the resistive two port network, find $\frac{V_2}{V_1}$, $\frac{V_2}{I_1}$, $\frac{I_2}{V_1}$ and $\frac{I_2}{I_1}$.



$$I_2 = -\frac{V_2}{1} = -V_2$$

$$V_b = -3I_2 = 3V_2$$

$$I_b = \frac{V_b}{1} + \frac{V_b}{3} = \frac{4V_b}{3} = 4V_2$$

$$V_a = 2I_b + V_b = 8V_2 + 3V_2 = 11V_2$$

$$I_a = \frac{V_a}{1} + I_b = 11V_2 + 4V_2 = 15V_2$$

$$V_1 = 2I_a + V_a = 2 \times 15V_2 + 11V_2 = 41V_2$$

$$I_1 = \frac{V_1}{1} + I_a = 41V_2 + 15V_2 = 56V_2$$


$$\frac{V_2}{V_1} = \frac{1}{41}$$

$$\frac{V_2}{I_1} = \frac{1}{56} \Omega$$


$$\frac{I_2}{V_1} = -\frac{1}{41} s$$

$$\frac{I_2}{I_1} = -\frac{1}{56}$$

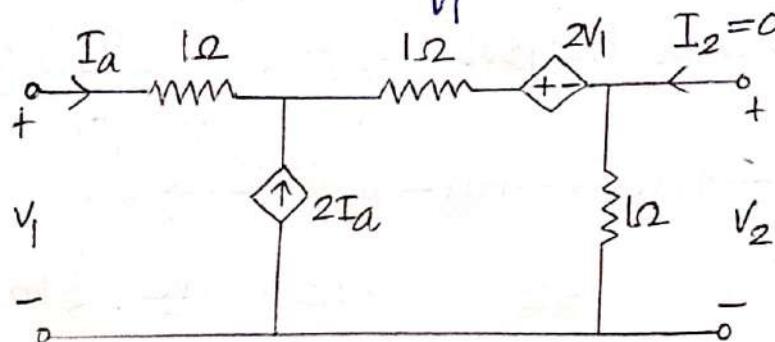8. Find the n/w function $\frac{V_2}{V_1}$ for the n/w.



The n/w can be redrawn as below:

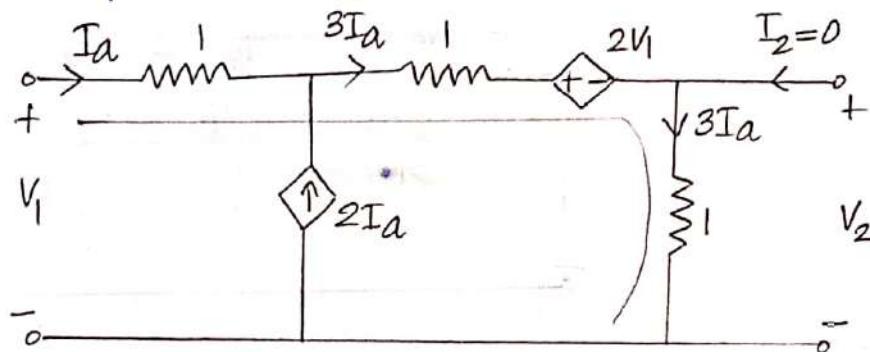

$$V_2 = 1 \cdot 3I_a = 3I_a$$

Applying KVL in the outermost loop,


$$-V_1 + 1(I_a) + 1(3I_a) + 2V_1 + 1(3I_a) = 0$$


$$V_1 + 7I_a = 0$$

$$V_1 = -7I_a$$

$$\frac{V_2}{V_1} = \frac{3I_a}{-7I_a} = -\frac{3}{7}$$

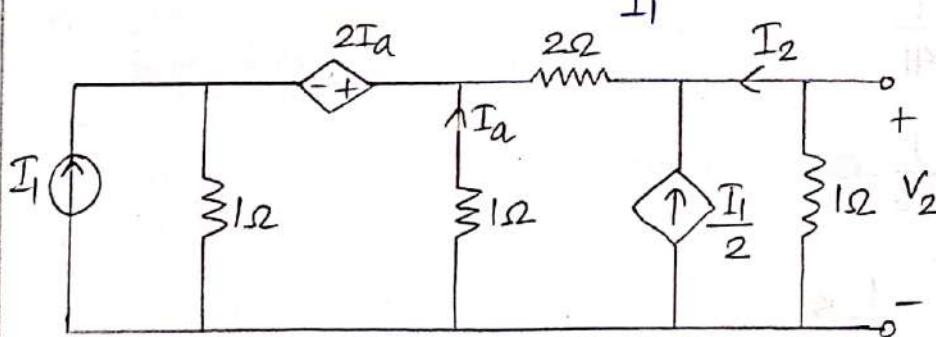9. Find the network function $\frac{I_2}{I_1}$ for the n/w.



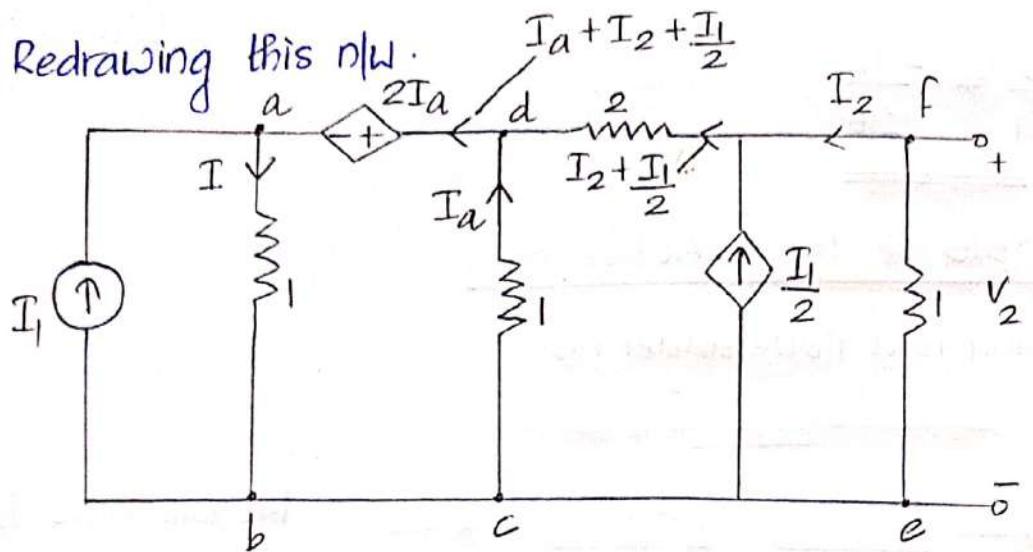

$$I = I_1 + I_a + I_2 + \frac{I_1}{2}$$

$$= \frac{3}{2}I_1 + I_a + I_2 \quad \text{--- (1)}$$

Applying KVL to loop abcda,

$$-I - 2I_a - I_a = 0$$

$$I + 3I_a = 0 \quad \text{--- (2)}$$

Substituting for (2) from (1),

$$\frac{3}{2}I_1 + I_a + I_2 + 3I_a = 0$$

$$\frac{3}{2}I_1 + I_2 + 4I_a = 0 \quad \text{--- (3)}$$

Applying KVL to the loop dcefd,

$$I_a - 2\left(I_2 + \frac{I_1}{2}\right) - I_2 = 0$$

$$I_a - 3I_2 - I_1 = 0$$

$$I_a = I_1 + 3I_2 \quad \text{--- (4)}$$

Substituting (4) in (3),

$$\frac{3}{2}I_1 + I_2 + 4(I_1 + 3I_2) = 0$$

$$\frac{3}{2}I_1 + I_2 + 4I_1 + 12I_2 = 0$$


$$\frac{11I_1}{2} + 13I_2 = 0$$

$$13I_2 = -\frac{11I_1}{2}$$

$$\therefore \frac{I_2}{I_1} = \frac{-11}{26}$$


ANALYSIS OF NON-LADDER N/LW

Following is a non-ladder n/lw.

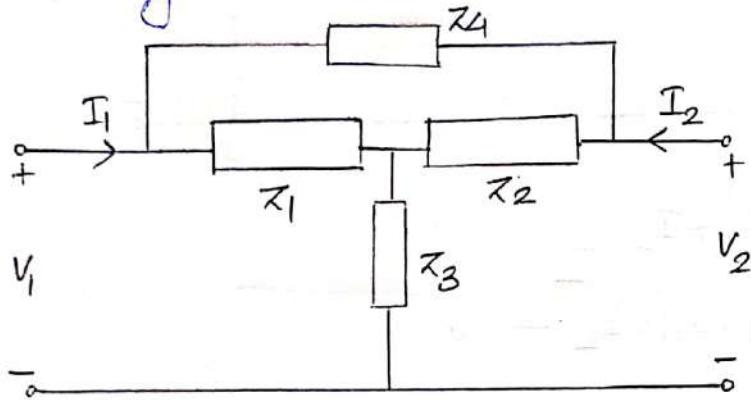

We will have to apply KVL or KCL. Then n/lw functions are to be represented as a quotient of determinants.

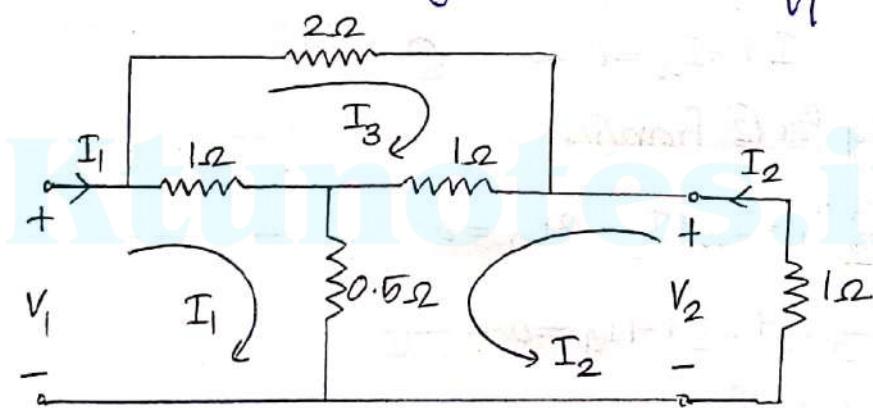1. For the resistive bridged T-nlw. find $\frac{V_2}{V_1}$, $\frac{V_2}{I_1}$, $\frac{I_2}{V_1}$ and $\frac{I_2}{I_1}$.



$$\text{Mesh-1 : } V_1 = 1.5I_1 + 0.5I_2 - I_3 \quad \textcircled{1} \quad 1.5I_1 + 0.5I_2 - I_3 = V_1$$

$$\text{Mesh-2 : } 0.5I_1 + 2.5I_2 + I_3 = 0 \quad \textcircled{2}$$

$$\text{Mesh-3 : } -I_1 + I_2 + 4I_3 = 0 \quad \textcircled{3}$$

$$I_1 = \frac{\begin{vmatrix} V_1 & 0.5 & -1 \\ 0 & 2.5 & 1 \\ 0 & 1 & 4 \end{vmatrix}}{\begin{vmatrix} 1.5 & 0.5 & -1 \\ 0.5 & 2.5 & 1 \\ -1 & 1 & 4 \end{vmatrix}} = \frac{10V_1 - V_1}{15 - 0.5 - 0.5 - 2.5 - 1.5 - 1} = \frac{9V_1}{9} = V_1 \quad \textcircled{4}$$

$$I_2 = \frac{1.5 \quad V_1 \quad -1}{0.5 \quad 0 \quad 1} = -\frac{V_1 + 2V_1}{9} = -\frac{V_1}{3} \quad \text{--- (5)}$$

$$V_2 = 1(-I_2) = -I_2$$

$$\text{From (5), } V_1 = -3I_2$$

$$\text{From (4), } I_1 = V_1 = -3I_2$$



$$\frac{I_2}{V_1} = -\frac{1}{3}$$

$$\frac{I_2}{I_1} = -\frac{1}{3}$$

$$\frac{V_2}{V_1} = \frac{-I_2}{-3I_2} = \frac{1}{3}$$

$$\frac{V_2}{I_1} = \frac{-I_2}{-3I_2} = \underline{\underline{\frac{1}{3}}}$$

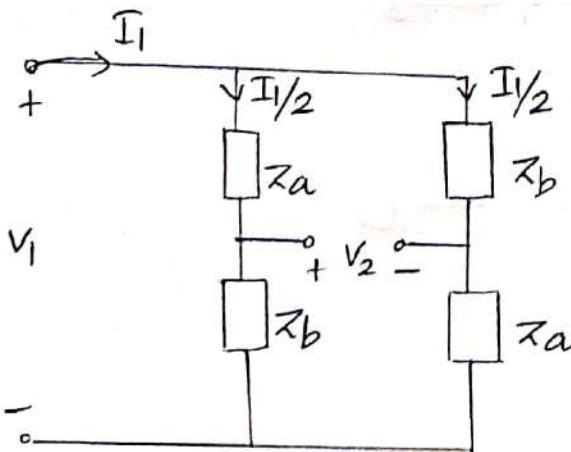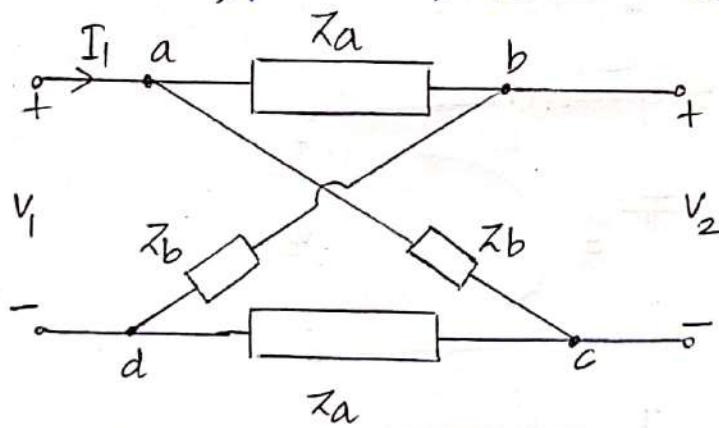2. For the network, find Z_{11} , Z_{21} and G_{21} .



Redrawing,

$$V_1 = (Z_a + Z_b) \frac{I_1}{2}$$


$$Z_{11} = \frac{V_1}{I_1} = \underline{\underline{\frac{Z_a + Z_b}{2}}}$$

$$V_2 = -Z_a \frac{I_1}{2} + Z_b \frac{I_1}{2} = \frac{(Z_b - Z_a)}{2} I_1$$


$$Z_{21} = \frac{V_2}{I_1} = \underline{\underline{\frac{Z_b - Z_a}{2}}}$$

$$G_{21} = \frac{V_2}{V_1} = \frac{\frac{(Z_b - Z_a)}{2} I_1}{\frac{(Z_a + Z_b) I_1}{2}} = \underline{\underline{\frac{Z_b - Z_a}{Z_a + Z_b}}}$$

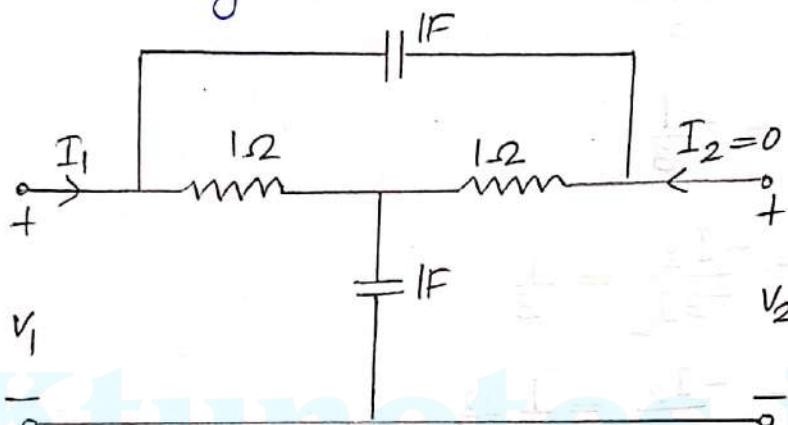3. For the following n/w, determine $Z_{11}(s)$, $G_{21}(s)$ and $Z_{21}(s)$.



Transformed n/w

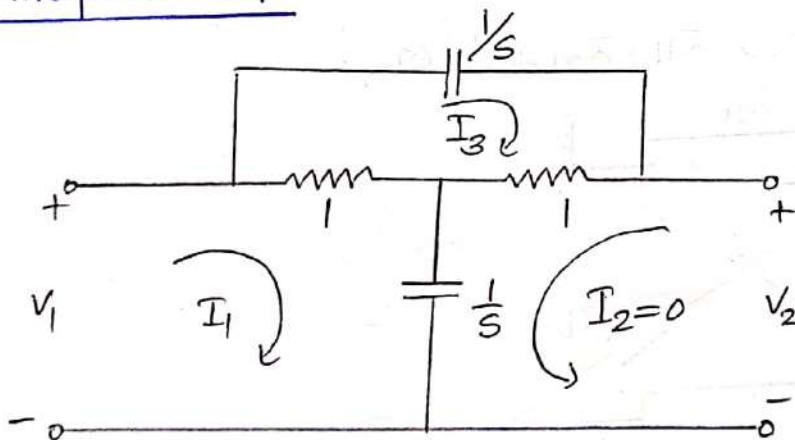

$$\text{Mesh-1 : } (1 + \frac{1}{s}) I_1 - I_3 = V_1 \quad \text{--- (1)}$$

$$\text{Mesh-2 : } \frac{1}{s} I_1 + I_3 = V_2 \quad \text{--- (2)}$$

$$\text{Mesh-3 : } -I_1 + (2 + \frac{1}{s}) I_3 = 0 \quad \text{--- (3)}$$

$$I_3 = \left(\frac{s}{2s+1} \right) I_1$$

Substituting I_3 in ① and ②,

$$\begin{aligned}V_1 &= \left(1 + \frac{1}{s}\right) I_1 - \frac{s}{2s+1} I_1 = I_1 \left[\frac{s+1}{s} - \frac{s}{2s+1} \right] \\&= I_1 \left[\frac{(s+1)(2s+1) - s^2}{s(2s+1)} \right] = I_1 \left[\frac{2s^2 + 3s + 1 - s^2}{s(2s+1)} \right] \\&= \frac{s^2 + 3s + 1}{s(2s+1)} \cdot I_1\end{aligned}$$

$$\begin{aligned}V_2 &= \frac{1}{s} I_1 + \frac{s}{2s+1} I_1 = I_1 \left[\frac{1}{s} + \frac{s}{2s+1} \right] \\&= I_1 \left[\frac{2s+1+s^2}{s(2s+1)} \right] = I_1 \frac{(s+1)^2}{s(2s+1)}\end{aligned}$$

$$Z_{11}(s) = \frac{V_1}{I_1} = \frac{\underline{s^2 + 3s + 1}}{\underline{s(2s+1)}}$$

$$\begin{aligned}G_{21}(s) &= \frac{V_2}{V_1} = \frac{(s+1)^2}{s(2s+1)} I_1 \times \frac{s(2s+1)}{(s^2 + 3s + 1) I_1} \\&= \frac{\underline{(s+1)^2}}{\underline{(s^2 + 3s + 1)}}\end{aligned}$$

$$Z_{21}(s) = \frac{V_2}{I_1} = \frac{(s+1)^2}{s(2s+1)}$$

POLES AND ZEROS OF NETWORK FUNCTIONS

The n/w function $N(s)$ can be written as ratio of two polynomials.

$$N(s) = \frac{P(s)}{Q(s)} = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}$$

where a_0, a_1, \dots, a_n and b_0, b_1, \dots, b_m

b_m are the coefficients of polynomials $P(s)$ and $Q(s)$.

These are real and positive for n/w with positive elements.

Let $P(s)=0$ have n -roots as $\tau_1, \tau_2, \dots, \tau_n$ and $Q(s)=0$ have m -roots as P_1, P_2, \dots, P_m .

$$\begin{aligned} \text{Then } N(s) &= \frac{a_n \left[s^n + \frac{a_{n-1}}{a_n} s^{n-1} + \dots + \frac{a_1}{a_n} s + \frac{a_0}{a_n} \right]}{b_m \left[s^m + \frac{b_{m-1}}{b_m} s^{m-1} + \dots + \frac{b_1}{b_m} s + \frac{b_0}{b_m} \right]} \\ &= H \cdot \frac{(s-\tau_1)(s-\tau_2) \dots (s-\tau_n)}{(s-P_1)(s-P_2) \dots (s-P_m)} \end{aligned}$$

Where $H = \frac{a_n}{b_m}$ is a constant called scale factor. At τ_1 to τ_n ,

the n/w function becomes zero and are known as zeros of network function. At P_1 to P_m the n/w function becomes infinite and are known as poles.


A network function is completely specified by its poles, zeros and scale factor. If the poles or zeros are not repeated, then the function is said to be having simple poles or simple zeros. If the poles or zeros are repeated, then the function is said to be having multiple poles and multiple zeros.

When $n > m$, then $n - m$ poles are at $s = \infty$ and for $m > n$, $(m - n)$ zeros are at $s = \infty$. Zeros are denoted by 0 and poles are denoted by ∞ .

Consider a network function,

$$N(s) = \frac{(s+1)^2(s+5)}{(s+2)(s+3+j2)(s+3-j2)}$$

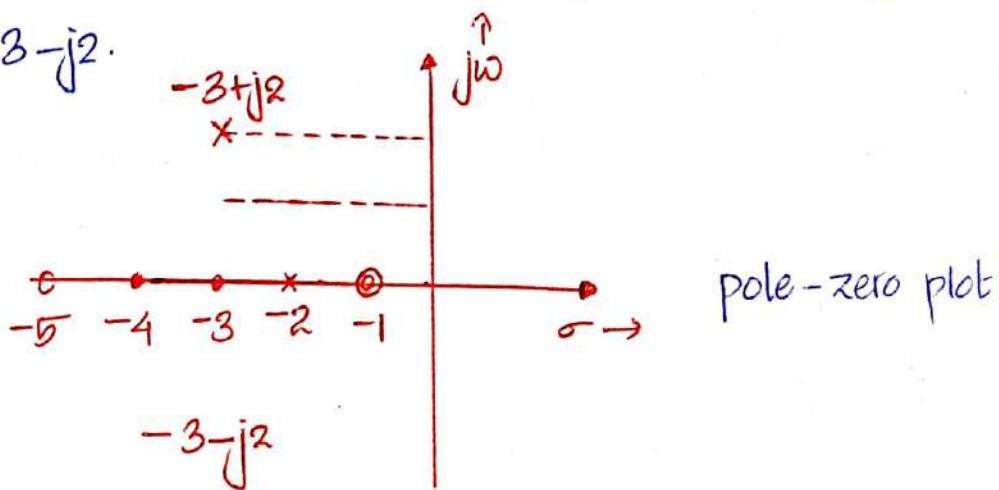It has two zeros at $s = -1$, one zero at $s = -5$. Three poles at $s = -2$, $s = -3+j2$ and $s = -3-j2$.



The network function is said to be stable when the real parts of the poles and zeros are negative. Otherwise, the poles and zeros must be within the left half of the s -plane.

Significance of poles and zeros

Poles and zeros are critical frequencies. The nw function becomes infinite at poles and zero at zeros. It has a finite non-zero value at other frequencies.

a. Driving point impedance

$$Z(s) = \frac{V(s)}{I(s)}$$

A poles of $Z(s)$ means zero current for a finite voltage which means an open circuit. A zero of $Z(s)$ implies no voltage for a finite current or a short circuit.

$$\text{Consider } z(s) = \frac{1}{cs}.$$

The above function has a pole at $s=0$ and zero at $s=\infty$.

∴ The function which represents a capacitor, acts as open circuit at pole frequency and acts as short circuit at zero frequency.

b. Driving point Admittance

$$Y(s) = \frac{I(s)}{V(s)}$$

A pole of $Y(s)$ implies zero voltage for a finite value of current which gives a short circuit. A zero of $Y(s)$ implies zero current for a finite value of voltage which gives an open circuit.

c. Voltage Transfer Ratio

$$G_{21}(s) = \frac{V_2(s)}{V_1(s)}$$

$$V_2(s) = G_{21}(s)V_1(s)$$

To obtain the o/p voltage, we require the product of input and transfer function. $G_{21}(s) \cdot V_1(s)$ is obtained in the form of a ratio of polynomials in s .

By partial fractions,

$$G_{21}(s) \cdot V_1(s) = \sum_{i=1}^n \frac{A}{s-a_i} + \sum_{j=1}^m \frac{A}{s-q_j} \quad \text{where } n \text{ and } m$$



are number of poles of $G_{21}(s)$ and $V_1(s)$ respectively.

The frequencies a_i (poles of $G_{21}(s)$) form the natural complex frequencies corresponding to free oscillations and depend on the network function $G_{21}(s)$. While frequencies q_j constitute the complex frequencies corresponding to the forced oscillations and depend on the driving force $V_1(s)$. From the above discussion, we can say that the poles determine the time variation of the response whereas the zeros determine the magnitude response.

d. Other Network Functions

Significance of poles and zeros in other transfer functions is the same as discussed above. In each of the cases, poles determine the time domain behaviour and zeros determine the magnitude of each of the terms of the response.




Examples:

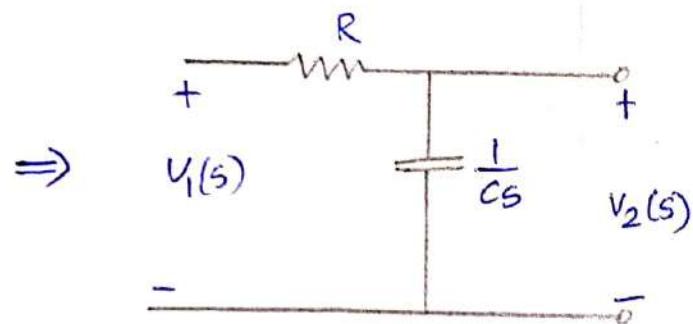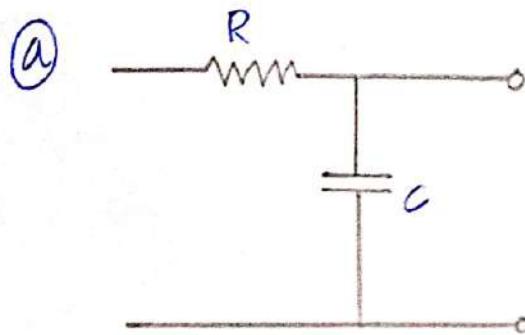

$$G_{21}(s) = \frac{V_2(s)}{V_1(s)} = \frac{\frac{1}{CS}}{R + \frac{1}{CS}} = \frac{1}{1 + s \cdot R \cdot C}$$

When $s=0$, $G_{21}(s)=1$,


$s=\infty$, $G_{21}(s)=0$

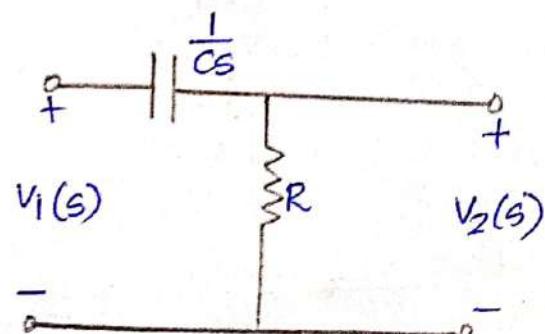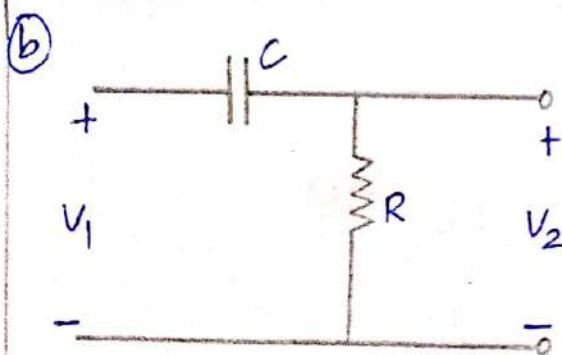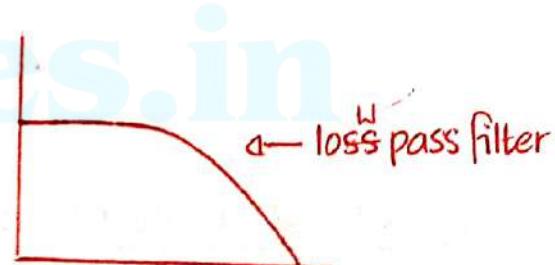

$$G_{21}(s) = \frac{R}{R + \frac{1}{CS}} = \frac{s \cdot R \cdot C}{s \cdot R \cdot C + 1} = \frac{s}{(s + \frac{1}{RC})}$$

$s=0 \Rightarrow G_{21}(s)=0$

$s=\infty \Rightarrow G_{21}(s)=1$

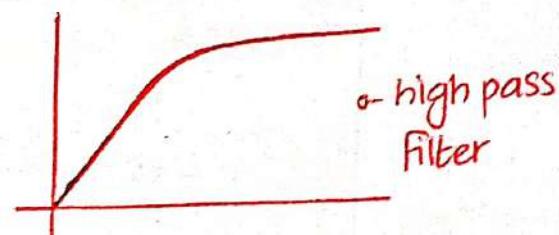

17/11/2020

TIME DOMAIN RESPONSE FROM THE POLE-ZERO PLOT


The time domain behaviour of a system can be determined from the pole-zero plot. Consider a nlw function.

$$F(s) = H \cdot \frac{(s-z_1)(s-z_2)(s-z_3) \dots (s-z_n)}{(s-p_1)(s-p_2) \dots (s-p_m)}$$

The poles of this function determine the time domain behaviour of $f(t)$. The function $f(t)$ can be determined from the knowledge of the poles, zeros and the scale factor H .


(1) When pole is at origin (at $s=0$)

$$F(s) = \frac{K}{s}, f(t) = Ku(t)$$

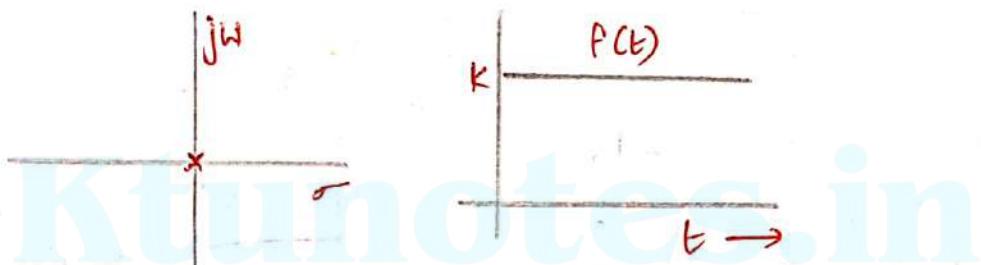


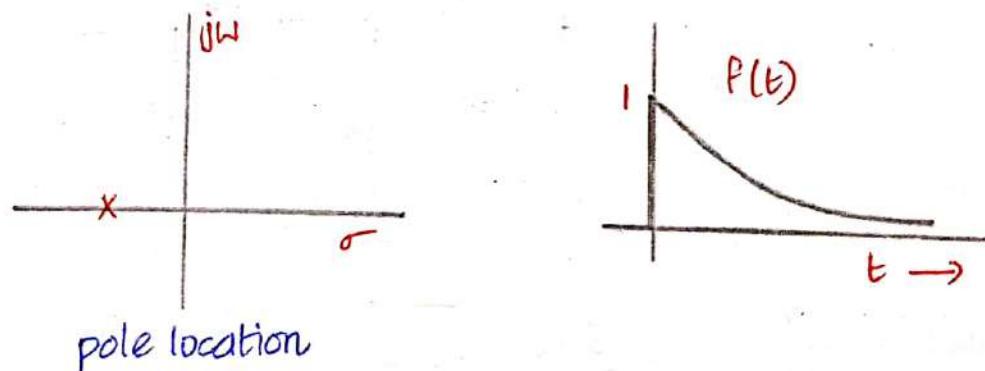
(2) Real and negative pole

$$F(s) = \frac{1}{s+a}, f(t) = e^{-at} u(t)$$



Real negative pole produces an exponentially decaying time response.

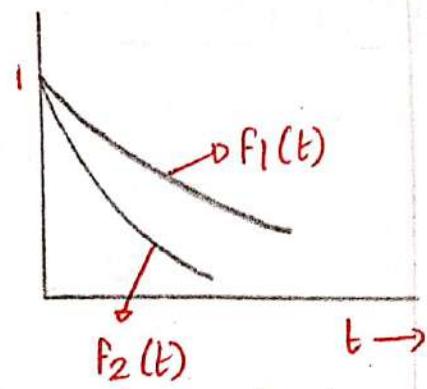
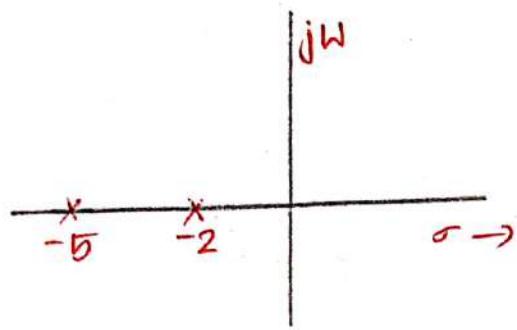
$$F_1(s) = \frac{1}{s+2}, F_2(s) = \frac{1}{s+5}; f_1(t) = e^{-2t} u(t) \text{ and } f_2(t) = e^{-5t} u(t)$$





As the pole moves away from origin, or the real axis, in the left half of the s-plane, the corresponding time response decays at a faster rate.

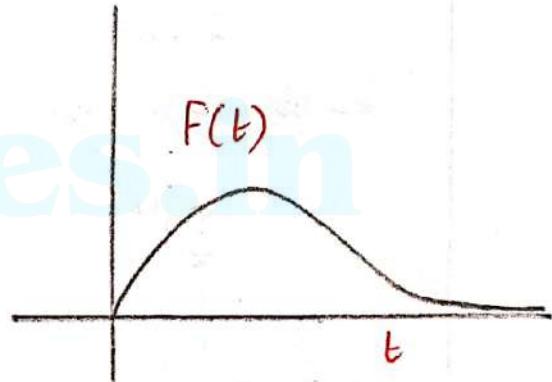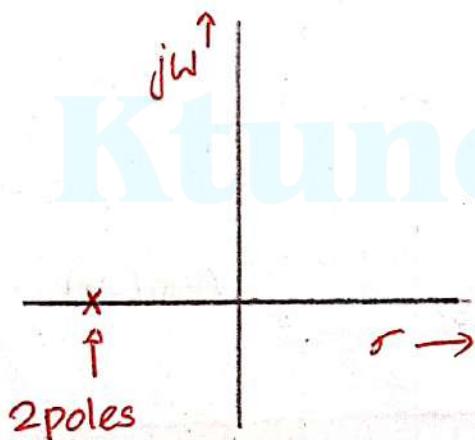(3) Real, negative repetitive pole

$$F(s) = \frac{1}{(s+a)^2}, \quad f(t) = t e^{-at} u(t)$$



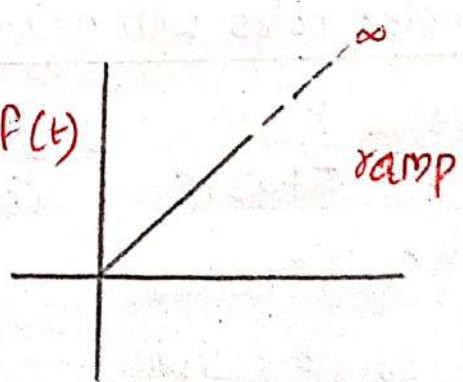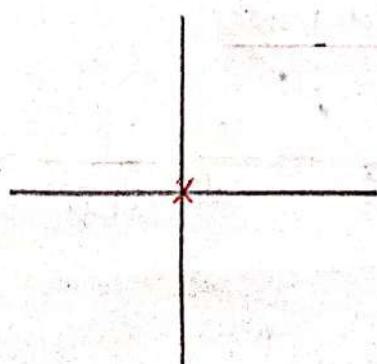
$$\text{If } a=0, \quad F(s) = \frac{1}{s^2}, \quad f(t) = t u(t) = \sigma(t)$$



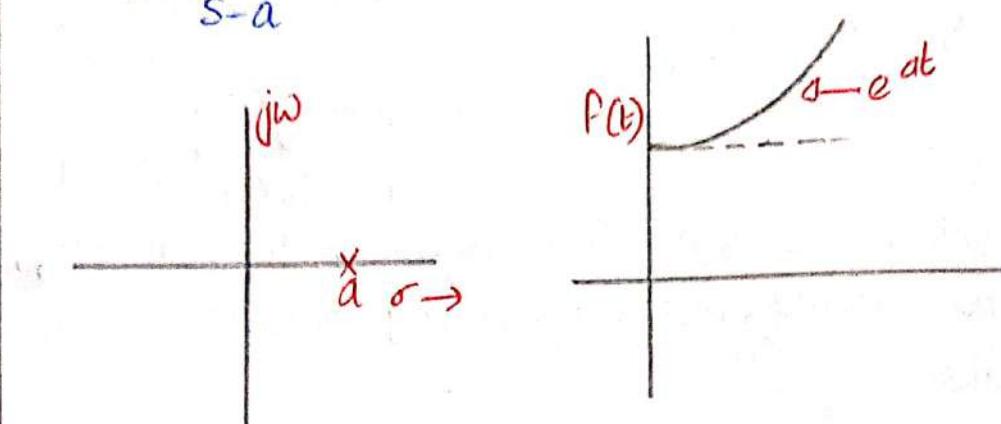(4) Real +ve pole


$$F(s) = \frac{1}{s-a}, F(t) = e^{at} u(t)$$



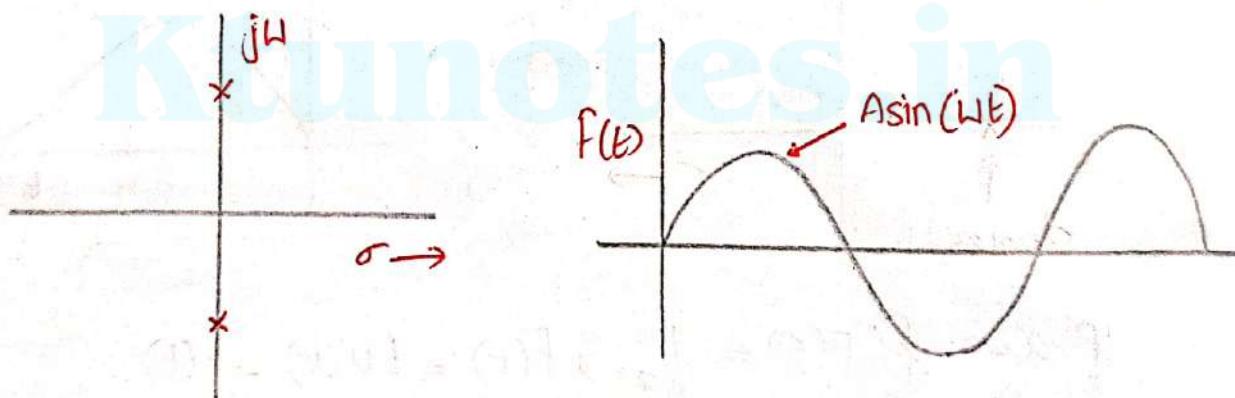(5) Complex poles on imaginary axis

$$F(s) = \frac{Aw}{s^2 + w^2}, F(t) = A \sin(wt) \cdot u(t)$$

Poles at $s = \pm jw \quad \because s^2 + w^2 = 0$



(6) Complex poles with negative real part



$$F(s) = \frac{k}{s^2 + \alpha s + \beta} = \frac{k}{(s+a)^2 + w^2} = \frac{k}{w} \cdot \frac{w}{(s+a)^2 + w^2}$$

$$(s+a)^2 + w^2 = 0$$

$$(s+a)^2 = -w^2$$

$$(s+a) = \pm jw \quad \text{or} \quad s = -a \pm jw$$
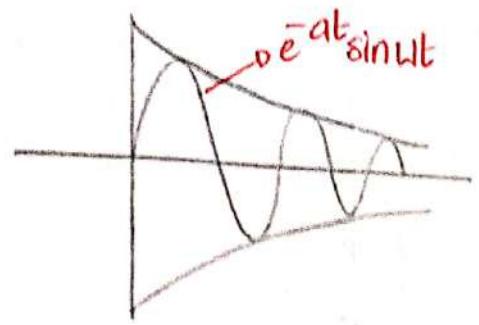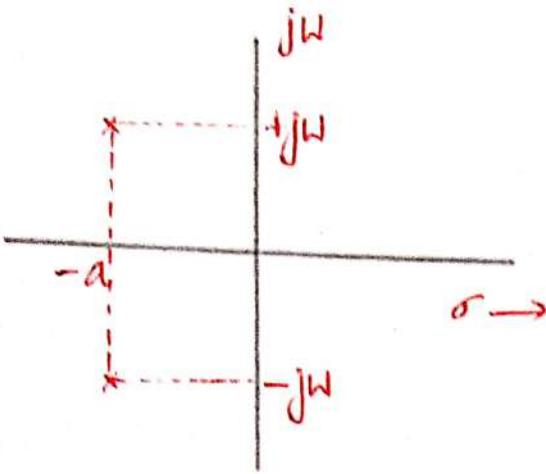
$$F(t) = \frac{k}{w} e^{-at} \sin wt \cdot u(t)$$





Damped oscillation or oscillations with decreasing amplitude.

(7) Complex poles with positive real part

$$F(s) = \frac{k}{(s-a)^2 + \omega^2} = \frac{k}{\omega} \cdot \frac{\omega}{(s-a)^2 + \omega^2}$$


$$F(t) = \frac{k}{\omega} e^{at} \sin \omega t \cdot u(t)$$

Poles at: $s = a \pm j\omega$

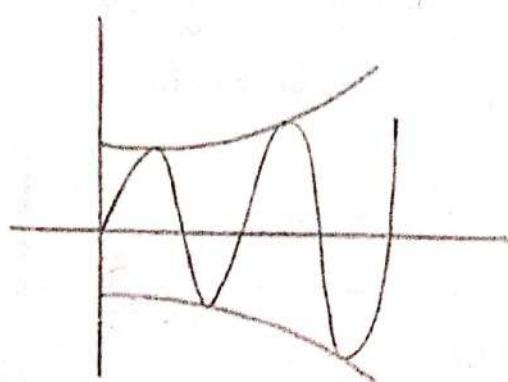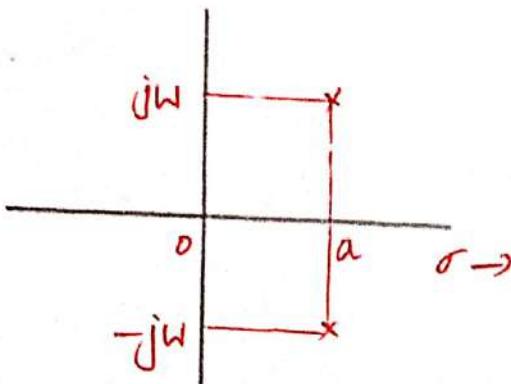

Growing oscillations.

IMPULSE RESPONSE

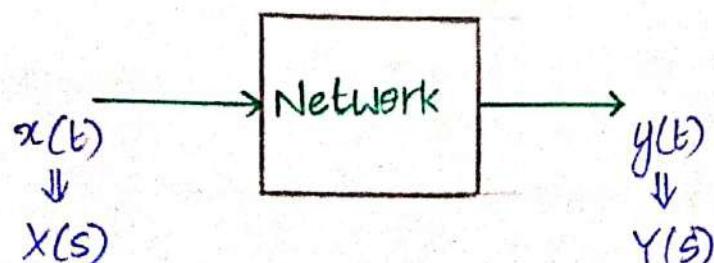

$$\text{Transfer fn, } H(s) = \frac{Y(s)}{X(s)}$$

$$\text{If } x(t) = \delta(t), x(s) = 1$$

$$\text{Then } H(s) = Y(s)$$


$$\text{Hence } h(t) = y(t)$$

Impulse response of a system is the response or output of the system, when the input is a unit impulse.

COMPLEX FREQUENCY PLANE

Circuit response as a function of s .

Consider

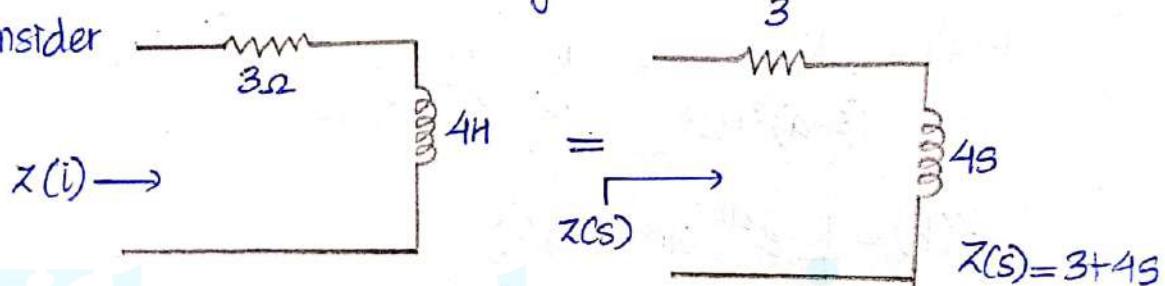


$$s = \sigma + j\omega$$

Z variation with σ

$$\text{Let } s = \sigma + j\cdot 0 = \sigma$$

$$Z(\sigma) = 3 + 4\sigma$$


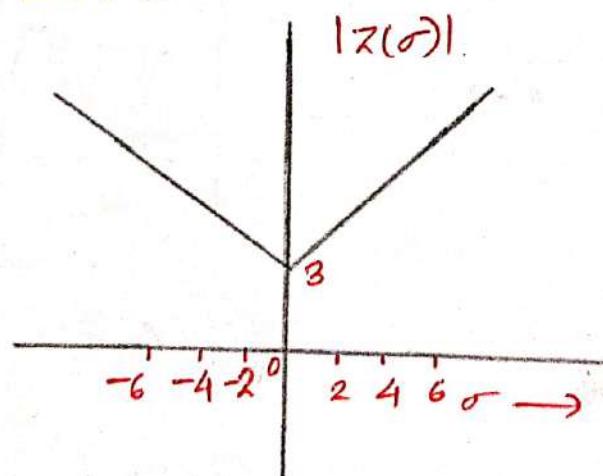


$\chi(j\omega)$ with ω

Let $s = \sigma + j\omega$


$$\chi(j\omega) = 3 + j4\omega$$

$$|\chi(j\omega)| = \sqrt{9 + 16\omega^2}, \theta = \tan^{-1}\left(\frac{4\omega}{3}\right)$$

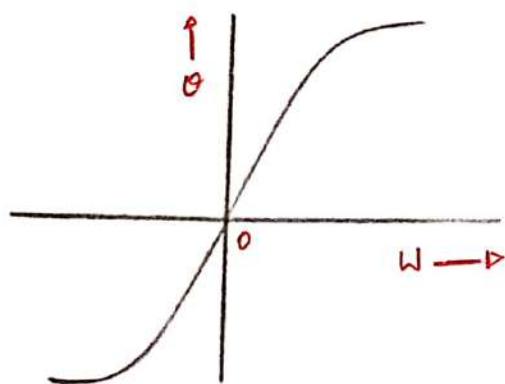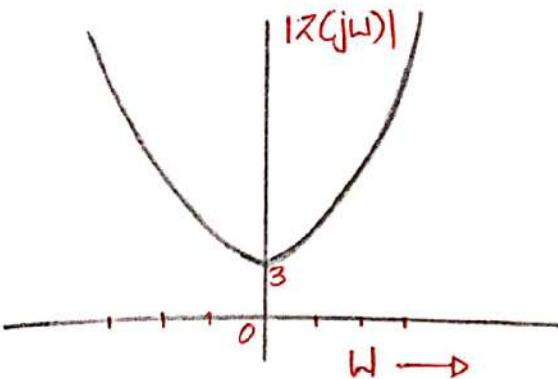

PROBLEMS

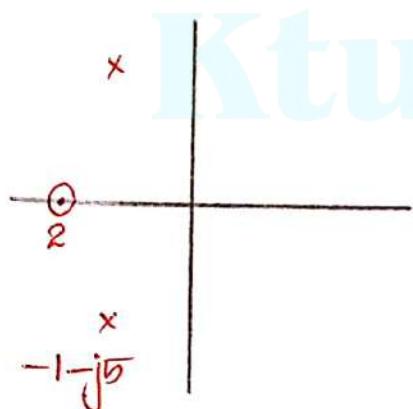1. From the pole zero plot obtain $\chi(s)$. $\chi(0) = 1$




$$\begin{aligned}
 \chi(s) &= k \cdot \frac{s+2}{(s+1-j5)(s+1+j5)} \\
 &= k \cdot \frac{s+2}{(s+1)^2 + 5^2} = k \cdot \frac{s+2}{s^2 + 2s + 1 + 25} \\
 &= k \cdot \frac{s+2}{s^2 + 2s + 26}
 \end{aligned}$$

$$\chi(0) = k \cdot \frac{2}{26} = 1 \Rightarrow k = 13$$

$$\therefore \chi(s) = 13 \cdot \frac{s+2}{s^2 + 2s + 26}$$

2. Pole zero plot of $G(s)$ is shown below. Obtain $G(s)$ in s .

$$G(1) = 4$$

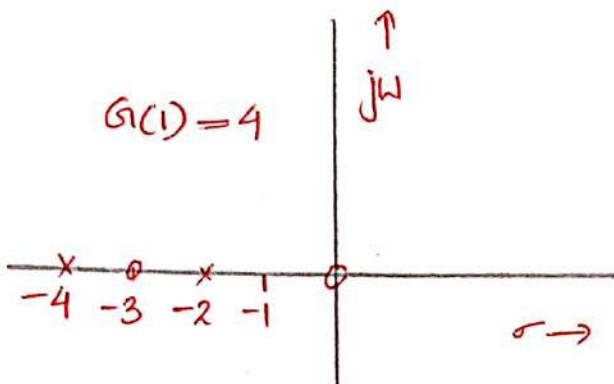

Zeros : 0, -3


Poles : -2, -4

$$G(s) = k \cdot \frac{s(s+3)}{(s+2)(s+4)}$$

$$G(1) = k \cdot \frac{4}{3 \cdot 5} = 4 \Rightarrow k = 15$$

$$\therefore G(s) = \frac{15 \cdot s(s+3)}{s^2 + 6s + 8} = \frac{15s^2 + 45s}{s^2 + 6s + 8}$$

18/11/2020 3) Obtain expression for $G(s)$. $G(0) = 15$ | zeros : -3, -4+j2, -4-j2
Poles : -2+j2, -2-j2

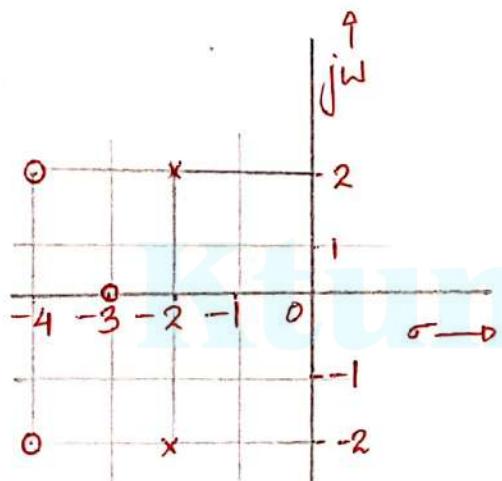

$$\begin{aligned} G(s) &= k \cdot \frac{(s+3)(s+4-j2)(s+4+j2)}{(s+2-j2)(s+2+j2)} \\ &= k \frac{(s+3)((s+4)^2 + 2^2)}{(s+2)^2 + 2^2} \\ &= \frac{k(s+3)(s^2 + 8s + 20)}{(s^2 + 4s + 8)} \end{aligned}$$

$$G(0) = \frac{k \cdot 3 \cdot 20}{8} = 15$$

$$\Rightarrow k = \frac{15 \times 8}{3 \times 20} = 2$$


$$G(s) = \frac{2(s+3)(s^2 + 8s + 20)}{s^2 + 4s + 8}$$

$$= \frac{2[s^3 + 11s^2 + 44s + 60]}{s^2 + 4s + 8}$$

$$= \frac{2s^3 + 22s^2 + 88s + 120}{s^2 + 4s + 8}$$

$$\begin{array}{r} s^2 + 8s + 20 \times \\ \hline s + 3 \\ \hline 3s^2 + 24s + 60 \\ \hline s^3 + 8s^2 + 20s \\ \hline s^3 + 11s^2 + 44s + 60 \end{array}$$

4. obtain $G(s)$. $G(\infty) = 3$

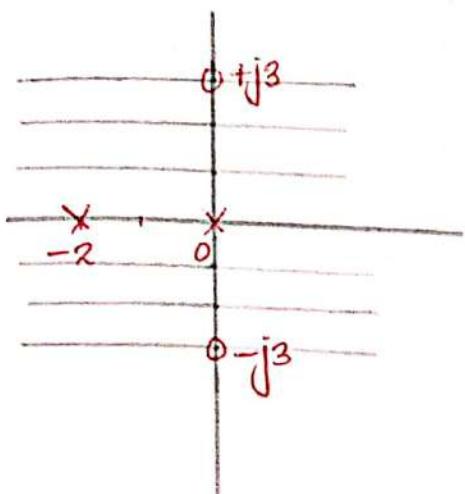

Zeros: $j\sqrt{3}, -j\sqrt{3}$

Poles: $0, -2$

$$G(s) = \frac{k(s-j\sqrt{3})(s+j\sqrt{3})}{s(s+2)}$$

$$= \frac{k(s^2+9)}{s^2+2s} = k \cdot \frac{(1 + \frac{9}{s^2})}{1 + \frac{2}{s}}$$

$$G(\infty) = 3 = \frac{k \cdot 1}{1} \Rightarrow k = 3$$

$$\therefore G(s) = \frac{3(s^2+9)}{s^2+2s} = \underline{\underline{\frac{3s^2+27}{s^2+2s}}}$$


MAGNITUDE AND PHASE RESPONSE

1. Evaluate amplitude and phase of the network function.

$$F(s) = \frac{4s}{s^2+2s+2} \text{ from the pole-zero plot at } s=j^2$$

$$F(s) = \frac{4s}{s^2+2s+1+1} = \frac{4s}{(s+1)^2+1^2} = \frac{4s}{(s+1+j)(s+1-j)}$$

Zero: $s=0$, poles: $-1-j, -1+j$

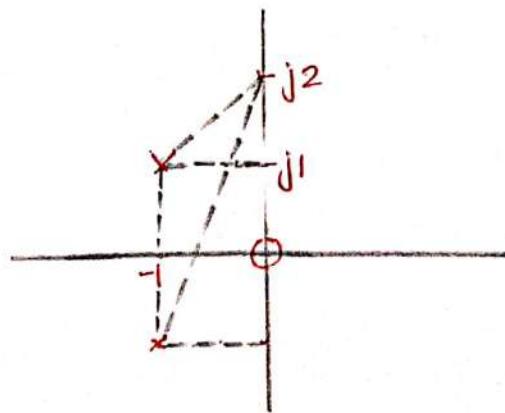

$|F(j2)| = \frac{\text{Product of phasor magnitude from all zeros to } j^2}{\text{Product of phasor magnitude from all poles to } j^2}$

$$= \frac{2}{\sqrt{2} \cdot \sqrt{1+9}} = \frac{2}{\sqrt{20}} = \underline{\underline{0.447}}$$

$$\begin{aligned}\phi(\omega) &= \tan^{-1}\left(\frac{2}{0}\right) - \tan^{-1}\left(\frac{3}{1}\right) - \tan^{-1}\left(\frac{1}{1}\right) \\ &= 90^\circ - 71.56^\circ - 45^\circ \\ &= \underline{\underline{-26.56^\circ}}\end{aligned}$$


2. Using pole zero plot, find magnitude and phase of the function.

$$F(s) = \frac{(s+1)(s+3)}{s(s+2)} \text{ at } s=j^4$$

Zeros: $-1, -3$; poles: $0, -2$

$|F(j4)| = \frac{\text{Product of phasor magnitude from all zeros to } j^4}{\text{Product of phasor magnitude from all poles to } j^4}$
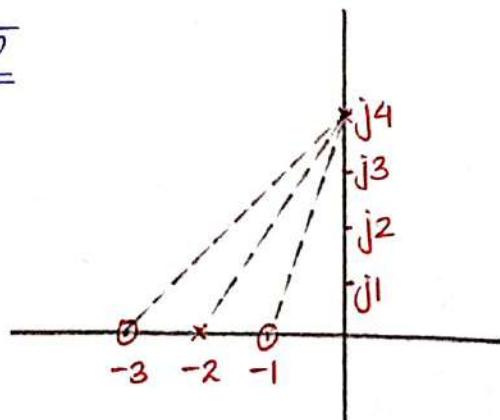
$$= \frac{5\sqrt{17}}{\sqrt{20} \cdot 4} = \underline{\underline{1.15}}$$



$$\begin{aligned}\phi(\omega) &= \tan^{-1}\left(\frac{4}{1}\right) + \tan^{-1}\left(\frac{4}{3}\right) - \tan^{-1}\left(\frac{4}{0}\right) - \tan^{-1}\left(\frac{4}{2}\right) \\ &= 75.96^\circ + 53.13^\circ - 90^\circ - 63.43^\circ \\ &= \underline{\underline{-24.34^\circ}}\end{aligned}$$


3. Plot the amplitude and phase response for

$$F(s) = \frac{s}{s+10}$$

$$F(j\omega) = \frac{j\omega}{j\omega + 10}$$

$$|F(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + 100}}$$


ω	$ F(j\omega) $
0	0
10	0.707
100	0.995
1000	1

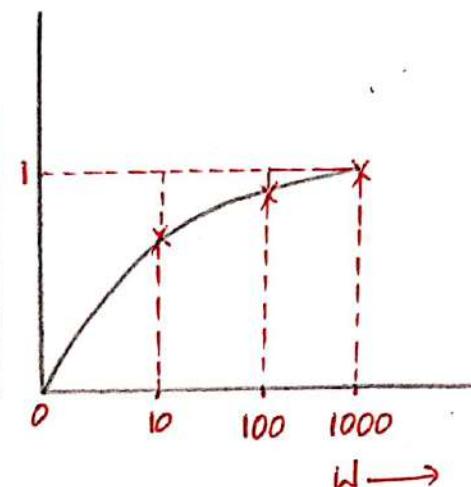

$$\phi(\omega) = \tan^{-1}\left(\frac{\omega}{10}\right) - \tan^{-1}\left(\frac{0}{10}\right)$$

$$= 90^\circ - \tan^{-1}\left(\frac{\omega}{10}\right)$$

ω	$\phi(\omega)$
0	90
10	45
100	5.7
1000	0

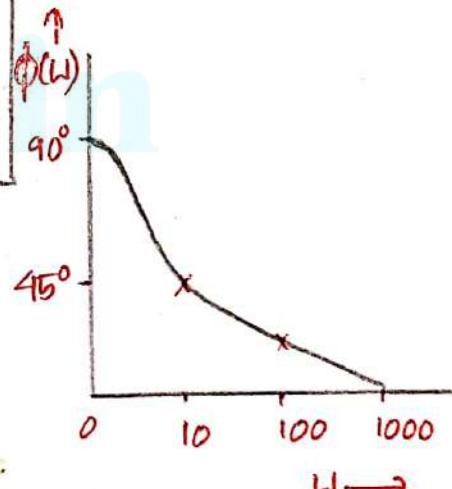


4. Sketch the amplitude and phase response for $F(s) = \frac{s+10}{s-10}$

$$F(j\omega) = \frac{j\omega + 10}{j\omega - 10}$$



$$|F(j\omega)| = \frac{\sqrt{100+\omega^2}}{\sqrt{100+\omega^2}} = 1$$

$$\begin{aligned} \phi(\omega) &= \tan^{-1}\left(\frac{\omega}{10}\right) - \tan^{-1}\left(-\frac{\omega}{10}\right) \\ &= 2\tan^{-1}\left(\frac{\omega}{10}\right) \end{aligned}$$

ω	$\phi(\omega)$
0	0
10	90°
100	168.6°
1000	178.90°

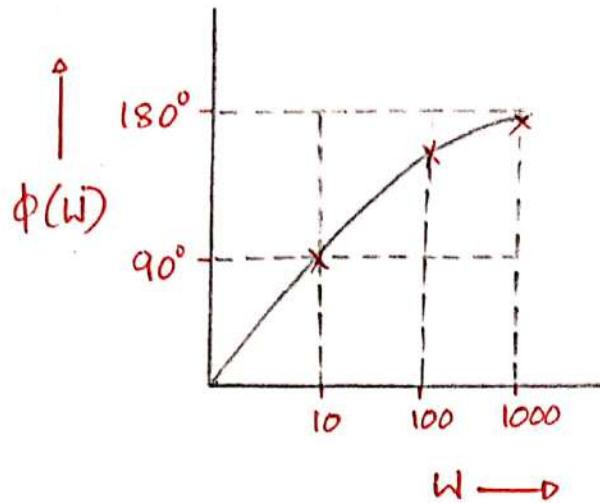

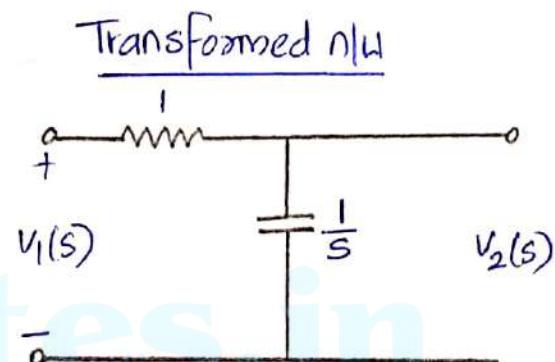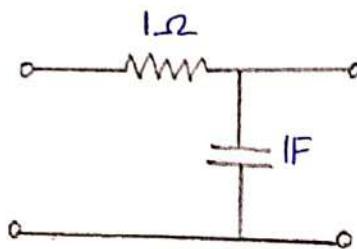5. For the low pass filter (LPF) shown in fig, plot the magnitude and phase response of transfer function for $0 < \omega \leq 10$.




$$H(s) = \frac{V_2(s)}{V_1(s)} = \frac{\frac{1}{s}}{1 + \frac{1}{s}} = \frac{1}{s+1}$$


$$H(j\omega) = \frac{1}{j\omega + 1}$$

$$|H(j\omega)| = \frac{1}{\sqrt{\omega^2 + 1}}, \quad \phi(\omega) = -\tan^{-1}(\omega) = -\tan^{-1}(\omega).$$

ω	$ H(j\omega) $	$\phi(\omega)$
0	1	0
2	0.45	-63.43
4	0.24	-75.96
6	0.16	-80.53
8	0.12	-82.89
10	0.09	-84.29

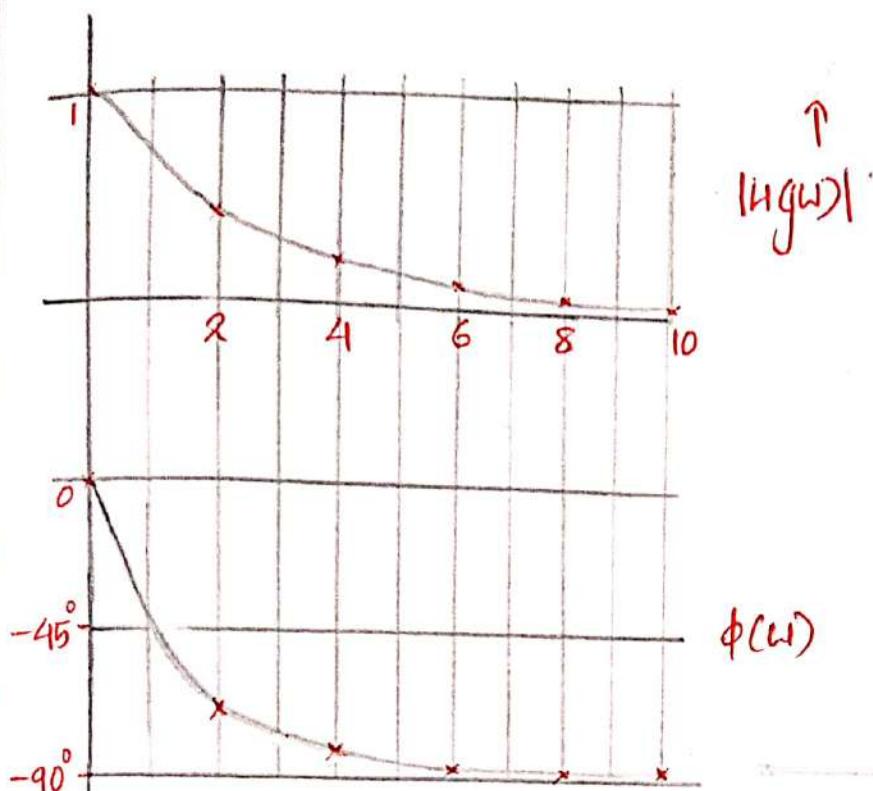

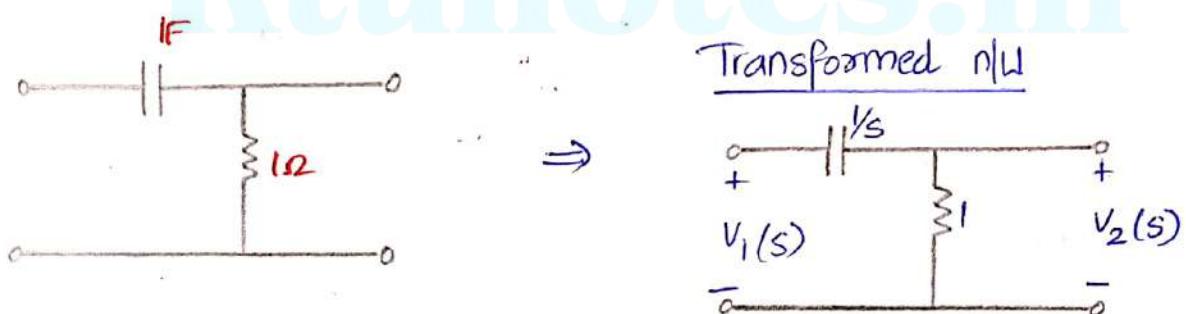6. For the HPF shown below, plot the magnitude and phase response of the transfer function for $0 \leq \omega \leq 10$.



$$H(s) = \frac{1}{1 + \frac{1}{s}} = \frac{s}{s+1}$$

$$H(j\omega) = \frac{j\omega}{j\omega + 1}$$

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + 1}} ; \quad \phi(\omega) = \tan^{-1}\left(\frac{\omega}{1}\right) - \tan^{-1}(\omega) \\ = 90 - \tan^{-1}(\omega)$$

ω	$ H(j\omega) $	$\phi(\omega)$
0	0	90
2	0.89	26.57
4	0.96	14.04
6	0.96	9.47
8	0.96	7.11
10	0.99	5.71

